

Boolean algebra, logic diagrams and truth tables

Kjartan Halvorsen

April 15, 2020

AND and OR

$$a, b \in \{0, 1\}$$


AND

a	b	a AND b, ab
0	0	0
0	1	0
1	0	0
1	1	1





Closed circuit $\Leftrightarrow 1$

Open circuit $\Leftrightarrow 0$

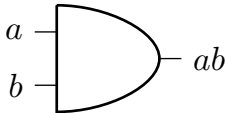

OR

a	b	a OR $b, a + b$
0	0	0
0	1	1
1	0	1
1	1	1

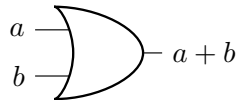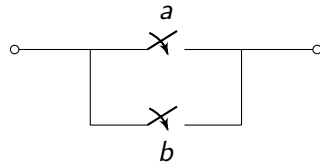


NAND and NOR

$$a, b \in \{0, 1\}$$


NAND

a	b	$a \text{ NAND } b, \overline{a \cdot b}$
0	0	1
0	1	1
1	0	1
1	1	0

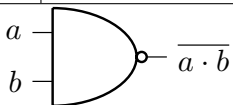

NOR

a	b	$a \text{ NOR } b, \overline{a + b}$
0	0	
0	1	
1	0	
1	1	

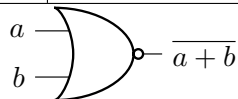

Boolean algebra, contd

$$x, y, z \in \{0, 1\}$$


	Property	Dual
Properties of 0 and 1	$x + 0 = x$ $x + 1 = 1$	$x \cdot 0 = 0$ $x \cdot 1 = x$
Idempotency	$x + x = x$	$x \cdot x = x$
Complementarity	$x + \bar{x} = 1$	$x \cdot \bar{x} = 0$
Involution	$\overline{\bar{x}} = x$	
Commutative	$x + y = y + x$	$x \cdot y = y \cdot x$
Associative	$(x + y) + z = x + (y + z)$	$(xy)z = z(yz)$
Distributive	$x \cdot (y + z) = xy + xz$	$x + yz = (x + y)(x + z)$

Boolean algebra, contd

$$x, y \in \{0, 1\}$$

	Theorem	Dual
Absorption	$x + xy = x(1 + y) = x$	$x(x + y) = x$
Logic adjacency	$xy + x\bar{y} = x(y + \bar{y}) = x$	$(x + y)(x + \bar{y}) = x$
De Morgan's	$\overline{x + y} = \bar{x} \cdot \bar{y}$	$\overline{xy} = \bar{x} + \bar{y}$

DeMorgan's theorem

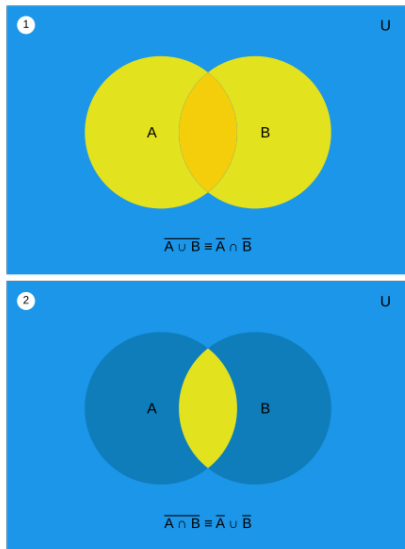

From wikipedia





Simplify functions

1. $f = (a + b)(a + c)$

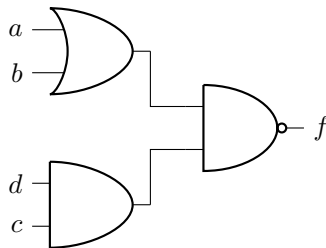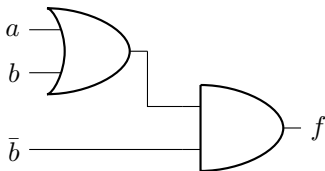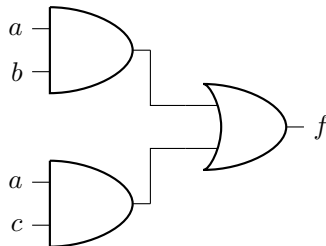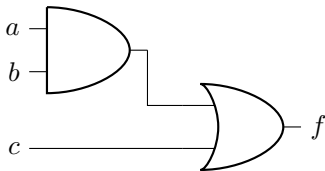2. $f = a + \bar{a}b$

Logic diagram \rightarrow function

Determine the function represented by the logic diagrams



Function \rightarrow logic diagram

Draw the diagram corresponding to the boolean function

1. $f = (a + b)(a + c)$

2. $f = a + \bar{a}b$

Group exercise

1. Enter breakout room
2. One of you downloads and shares this presentation
3. Work together on the problems in the previous three slides
 - 3.1 Simplify functions
 - 3.2 Determine function from logic diagram
 - 3.3 Draw logic diagram from function