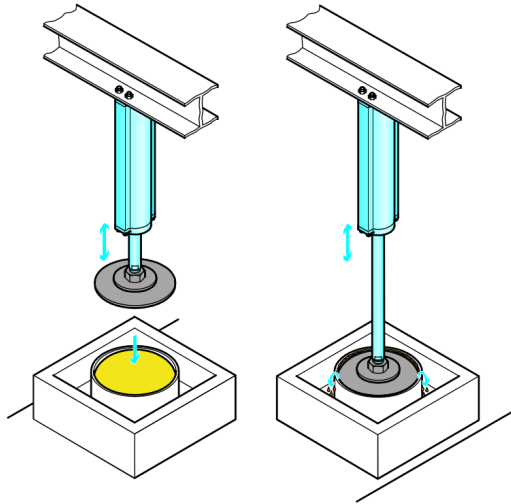


# Logic control of electro-pneumatic systems

Kjartan Halvorsen


October 10, 2022

## Cheese pressing example, sequence A+A-




From FESTO Didactic


# The Relay

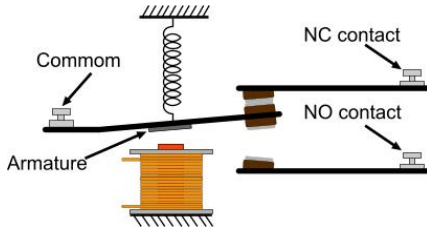

From pcbheaven.com

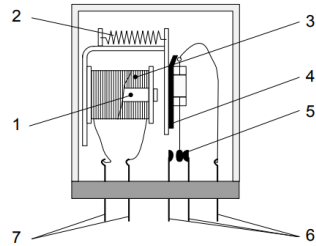

From FESTO didactic

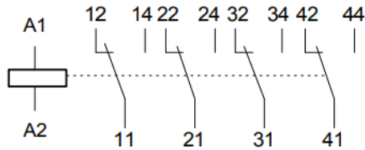

From FESTO didactic




From FESTO didactic


# Other key components

Sources: FESTO didactic, electroschematics.com, automation-insights.blog


## Limit switch

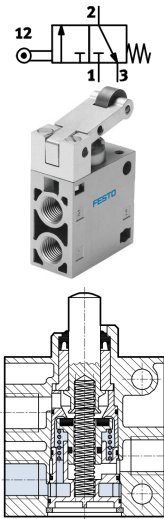

## Solenoid valve

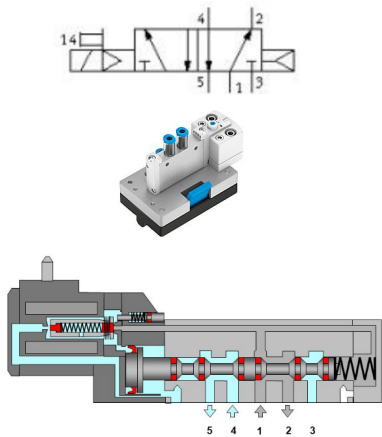


## Proximity sensor

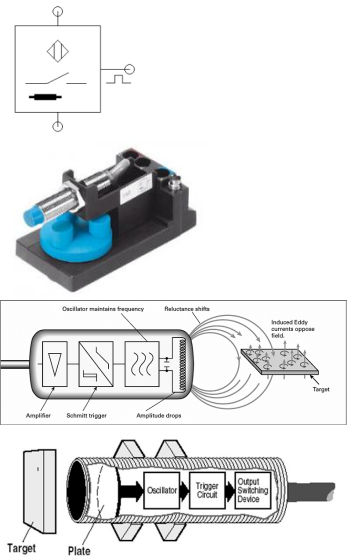

## A logic control loop

controller = logic circuit

plant = pneumatic system

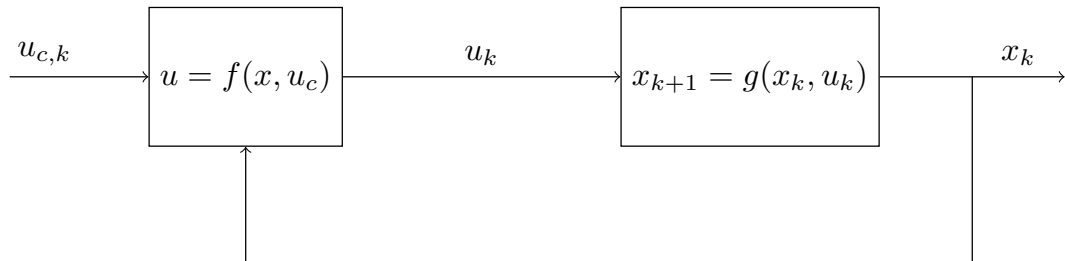

# Cheese pressing example - Variables

## State variables

$$x = \begin{bmatrix} x_R & x_E \end{bmatrix}^T \text{ with}$$

$$x_R = \begin{cases} 1 & \text{Cylinder retracted} \\ 0 & \text{not retracted} \end{cases}$$


$$x_E = \begin{cases} 1 & \text{Cylinder extended} \\ 0 & \text{not extended} \end{cases}$$

## Control signal

$$u = \begin{bmatrix} u_1 & u_2 \end{bmatrix}^T, \text{ with}$$

$$u_1 = \begin{cases} 1 & \text{Activate UA+} \\ 0 & \text{Don't activate UA+} \end{cases}$$
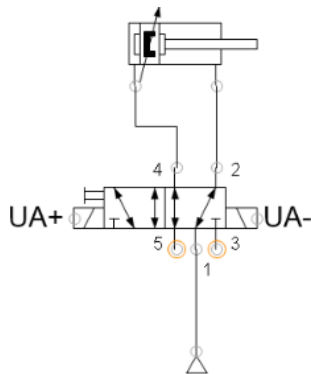
$$u_2 = \begin{cases} 1 & \text{Activate UA-} \\ 0 & \text{Don't activate UA-} \end{cases}$$



Activating solenoid UA+ extends the cylinder, activating UA- retracts the cylinder.

## Command signal

$$u_c = \begin{cases} 0 & \text{Button unpushed} \\ 1 & \text{Button pushed} \end{cases}.$$

## Cheese pressing example - Plant dynamics

Plant dynamics  $x_{k+1} = g(x_k, u_k)$

Input		Current state		Next state	
$u_{1,k}$	$u_{2,k}$	$x_{R,k}$	$x_{E,k}$	$x_{R,k+1}$	$x_{E,k+1}$
0	0	0	1	0	1
0	1	0	1	1	0
1	0	0	1	0	1
(1)	(1)	(0)	(1)	(0)	(1)
0	0	1	0	1	0
0	1	1	0	1	0
1	0	1	0	0	1
(1)	(1)	(1)	(0)	(1)	(0)

## Intermezzo - Maxterms and minterms



## Minterms

A minterm is a boolean expression that is TRUE (=1) for one and only one row in the truth table. For instance  $Y = X_1X_2X_3$  will only be true when  $X_1 = X_2 = X_3 = 1$ , and  $Y = \overline{X_1}X_2\overline{X_3}$  will only be true if  $X_1 = X_3 = 0$  and  $X_2 = 1$ . The combination  $Y = X_1X_2X_3 + \overline{X_1}X_2\overline{X_3}$  will have **only two rows** equal to 1 in the truth table.

Example:

Inputs			Outputs	
$X_1$	$X_2$	$X_3$	$Y_1$	$Y_2$
0	0	0	0	1
0	0	1	0	0
0	1	0	1	0
0	1	1	1	0
1	0	0	0	0
1	0	1	0	0
1	1	0	0	0
1	1	1	0	1

$$Y_1 = m_2 + m_3 = \overline{X_1}X_2\overline{X_3} + \overline{X_1}X_2X_3, \quad Y_2 =$$

# Maxterms

A maxterm is a boolean expression that is FALSE (=0) for one and only one row in the truth table. For instance  $Y = X_1 + X_2 + X_3$  will only be false when  $X_1 = X_2 = X_3 = 0$ , and  $Y = \overline{X_1} + X_2 + \overline{X_3}$  will only be false if  $X_1 = X_3 = 1$  and  $X_2 = 0$ . The combination  $Y = (X_1 + X_2 + X_3)(\overline{X_1} + X_2 + \overline{X_3})$  will have **only two rows** equal to 0 in the truth table.

Example:

Inputs			Outputs	
$X_1$	$X_2$	$X_3$	$Y_1$	$Y_2$
0	0	0	0	1
0	0	1	0	1
0	1	0	1	1
0	1	1	1	1
1	0	0	1	1
1	0	1	1	1
1	1	0	1	0
1	1	1	1	0

$$Y_1 = M_0 M_1 = (X_1 + X_2 + X_3)(X_1 + X_2 + \overline{X_3}), \quad Y_2 =$$

## Cheese pressing example - Control law

The system is operating as long as the start button is pressed ( $u_c = 1$ ). When the button is released, the cylinder should go to the retracted position.

Control law  $u_k = f(x, u_c)$

$x_R$	$x_E$	$u_c$	$u_1$	$u_2$
0	1	0	0	1
1	0	0	0	0
0	1	1	0	1
1	0	1	1	0
0	0	0	0	1
0	0	1	0	0

**Activity:** Write as boolean functions

$$u_1 = f_1(x_R, x_E, u_c) =$$


$$u_2 = f_2(x_R, x_E, u_c) =$$

# Cheese pressing example - implementing the control law

+24V



normally open

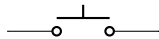


normally open



normally open




$u_1$  0V

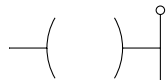

$u_2$



normally closed

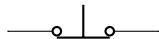


normally closed




normally closed



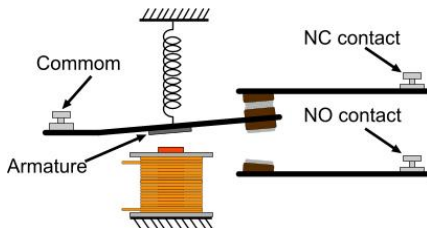
# Intermezzo - An electrical circuit with memory



From pcbheaven.com

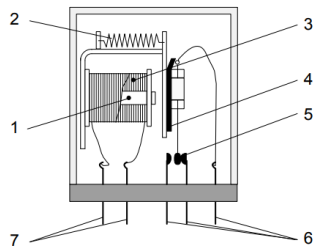

From FESTO didactic

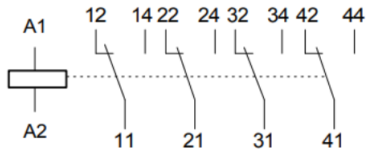


From FESTO didactic



From FESTO didactic

## Intermezzo - An electrical circuit with memory

### Latching circuit

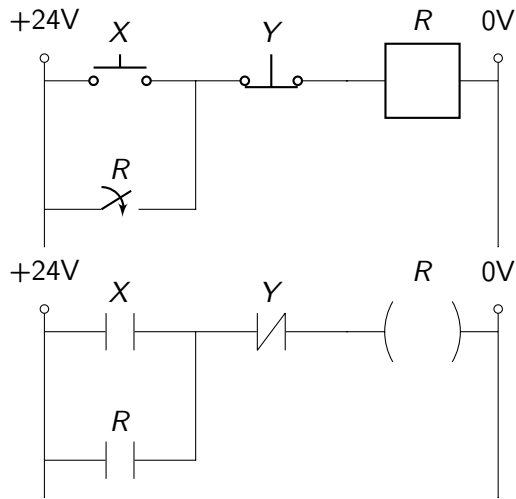

### Truth table

X	Y	$R_k$	$R_{k+1}$
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

**Group activity:** Implement the circuit in FluidSim and verify the truth table.

# Electrical circuits in FluidSim

FluidSIM-P

Archivo Edición Ejecutar Biblioteca Insertar Didáctica Proyecto Ver Opciones Ventana ?

Presentación jerarquizada - Biblioteca de ... FluidSIM Neumática\Diagramas de circuitos\noname.ct

**Interruptores comunes**

Obturator Franqueador Conmutador

**Interruptor de alimentación**

Interruptor d... Interruptor d... Interruptor d... Interruptor d...

**Regulador**

Comparador Regulador... Regulador d...

**Símbolos de diagrama de Ladder**


Conexión el... 0V Conexión al... 24V Pulsador (n... Pulsador (n... Pulsador (o... Contacto no... Contacto no... Solenoide d... Relé (Ladder) Relé con ret... Relé con ret... Indicador lu...

Técnica Digital


24V 0V

Navigation icons: back, forward, search, etc.


# The assignment

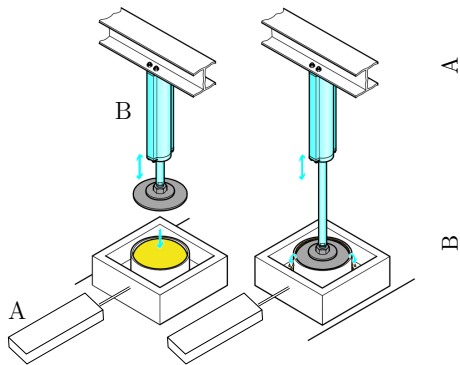

controller = logic circuit

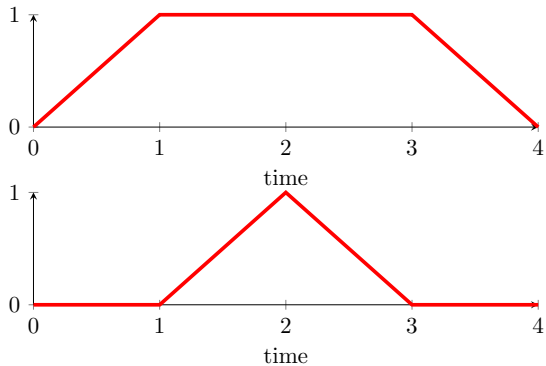


plant = pneumatic system

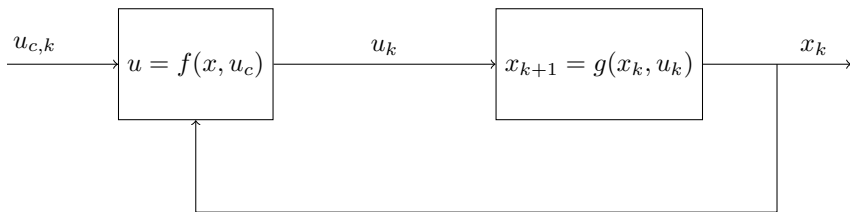




## Implementing the sequence $A+B+B-A-$

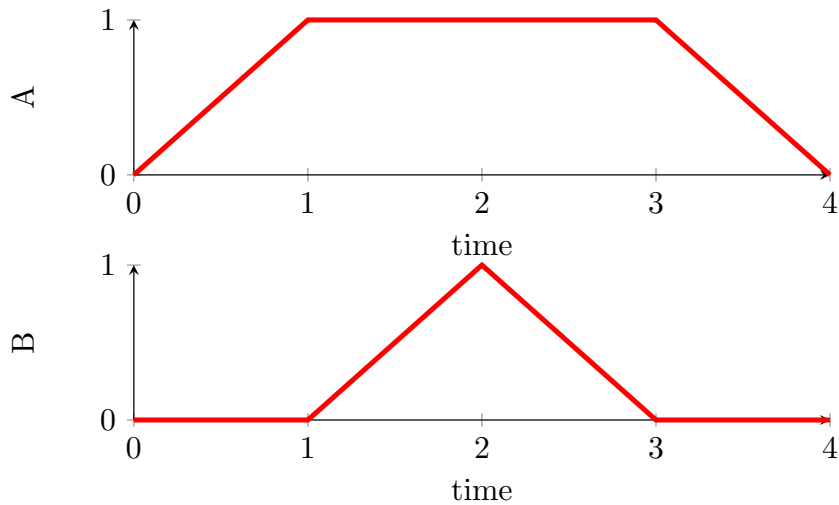
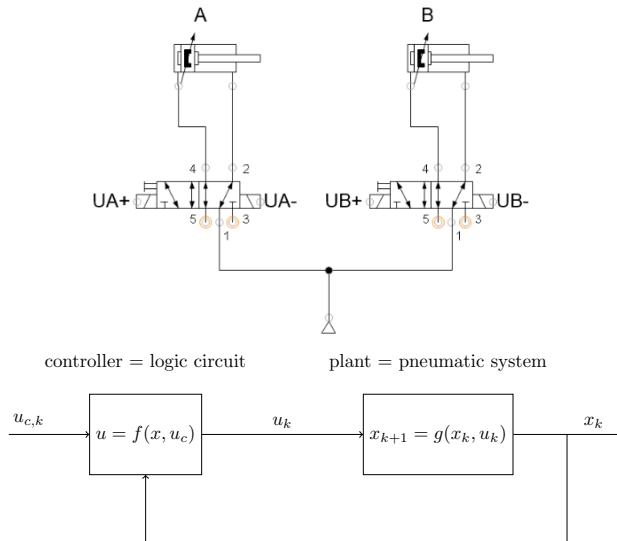
# Implementing the sequence $A+B+B-A-$ , control signal




Control signal

$$u = [u_{A+} \quad u_{A-} \quad u_{B+} \quad u_{B-}]^T,$$

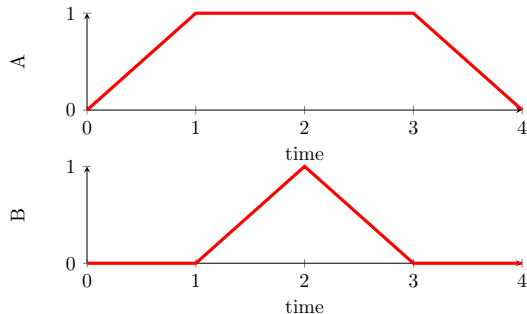
# Implementing the sequence A+B+B-A-, the problem

The correct control signal (action) is not uniquely defined by the position of the cylinders



controller = logic circuit


plant = pneumatic system

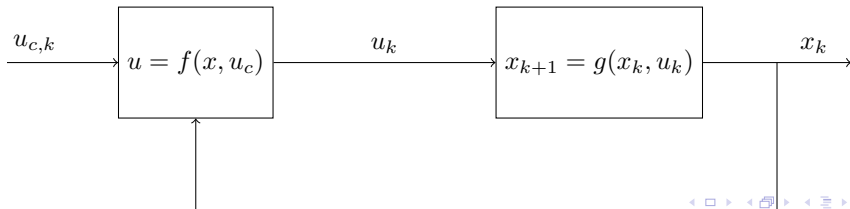

## Implementing the sequence $A+B+|B-A-$

Dividing the sequence into groups (a.k.a. cascade method) Each group contains as many steps as possible without repeating a letter.

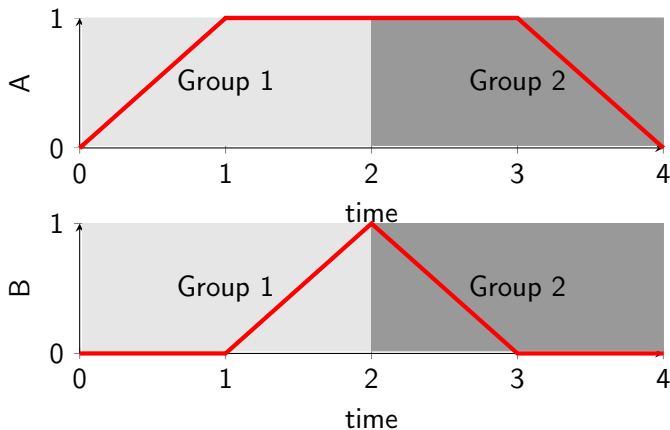
$$\underbrace{A+B+}_{\text{Group 1}} \mid \underbrace{B-A-}_{\text{Group 2}}$$



The cascade method applied to  $A+A^-$
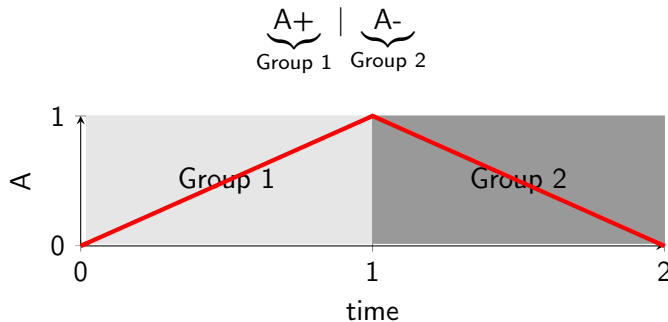
## The cascade method applied to $A+A^-$


Divide the sequence is to groups, where each group is as long as possible without repeating the same letter.


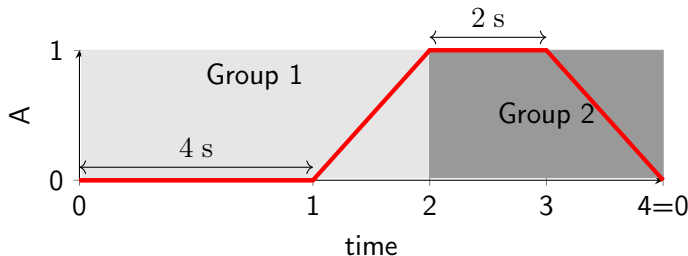
## The cascade method applied to A+A- with delays

Let's add some delays. The process is cyclic and automatic. It takes 4 seconds to replace the mold under the press. The cheese needs to be pressed during 2 seconds before the cylinder retracts.

$$\underbrace{T_{4s} A+}_{\text{Group 1}} \mid \underbrace{T_{2s} A-}_{\text{Group 2}}$$



# State variables

## State variables

$$\mathbf{x} = [x_R \quad x_E \quad x_{G1} \quad x_{G2} \quad x_{T4} \quad x_{T2}]^T,$$

where


$$x_R = \begin{cases} 1 & \text{Cylinder A retracted} \\ 0 & \text{not retracted} \end{cases}$$

$$x_E = \begin{cases} 1 & \text{Cylinder A extended} \\ 0 & \text{not extended} \end{cases}$$

$$x_{Gi} = \begin{cases} 1 & \text{Group } i \text{ active} \\ 0 & \text{Group } i \text{ not active} \end{cases}$$


$$x_{Ti} = \begin{cases} 1 & \text{Timer of } i \text{ s completed} \\ 0 & \text{Timer of } i \text{ s not completed} \end{cases}$$

## State transitions

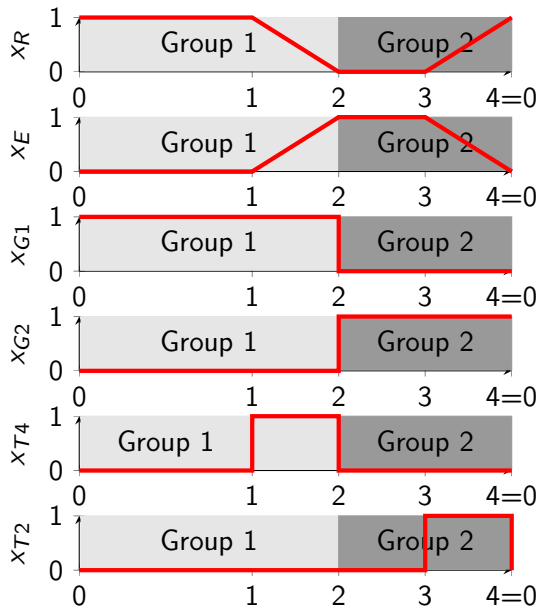





## Group transitions

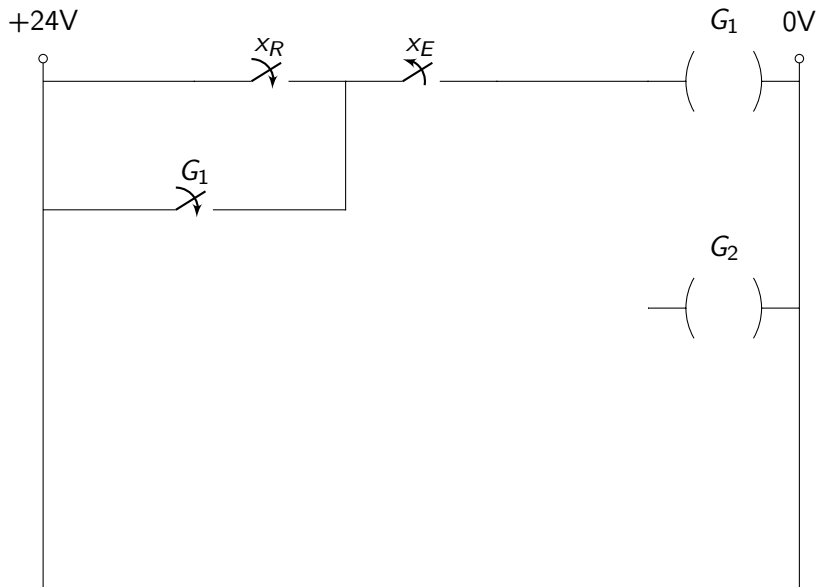


## The timers

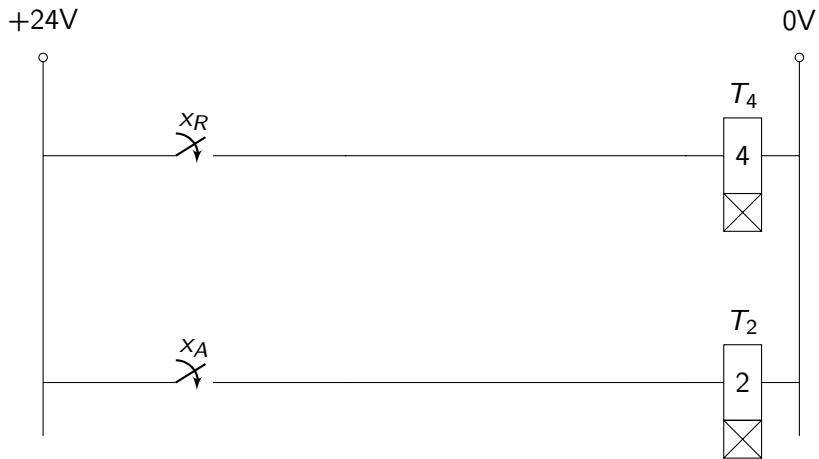


## The control law

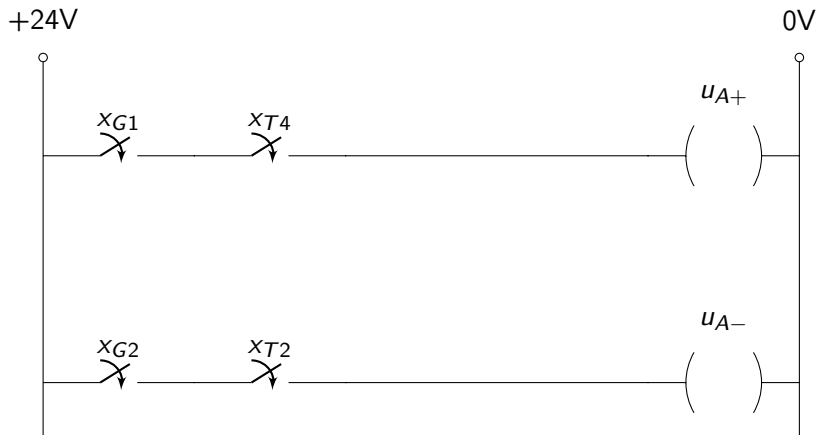


# The lab assignment

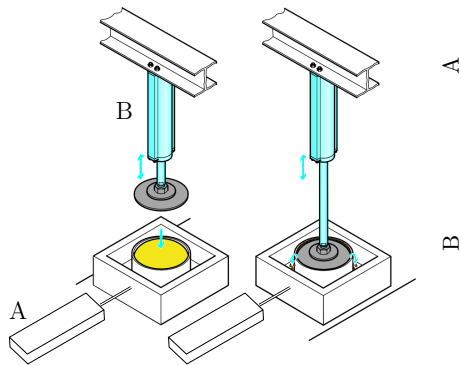

controller = logic circuit

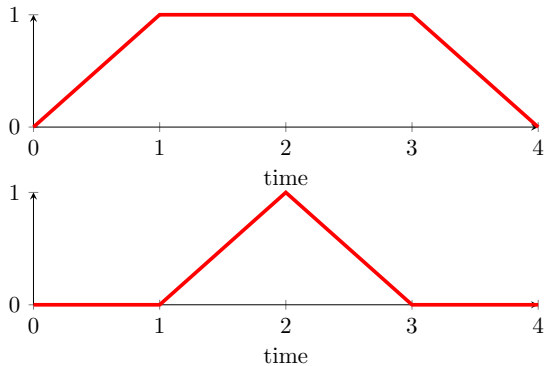

plant = pneumatic system

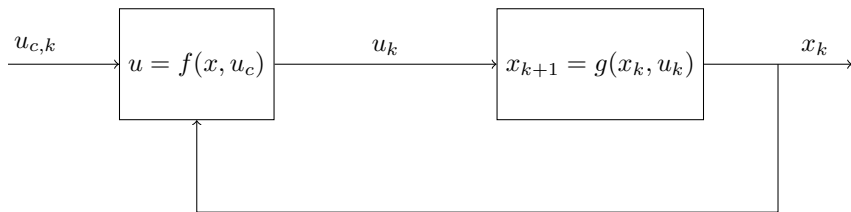

# Implementing the sequence $A+B+|B-A-$ , state variables

## State variables

$$x = [A_R \quad A_E \quad B_R \quad B_E \quad G_1 \quad G_2]^T,$$


with

$$\{A_R, B_R\} = \begin{cases} 1 & \{A,B\} \text{ retracted} \\ 0 & \{A,B\} \text{ not retracted} \end{cases}$$

$$\{A_E, B_E\} = \begin{cases} 1 & \{A,B\} \text{ extended} \\ 0 & \{A,B\} \text{ not extended} \end{cases}$$


$$G_i = \begin{cases} 0 & \text{Group } i \text{ not active} \\ 1 & \text{Group } i \text{ active} \end{cases}$$

## State transitions

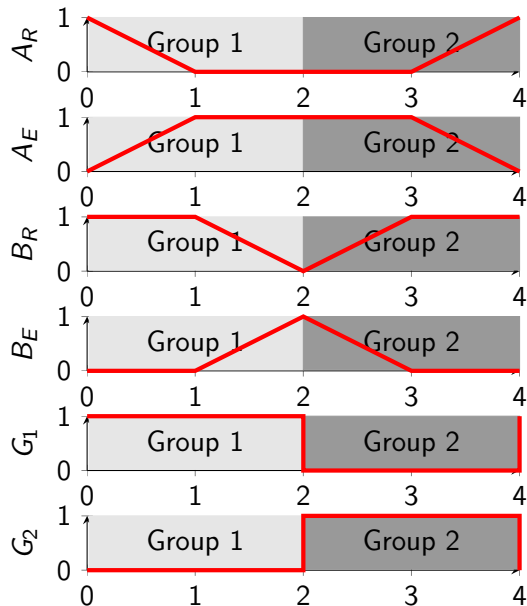

# Implementing the sequence $A+B+|B-A-$ , control law

## State transitions

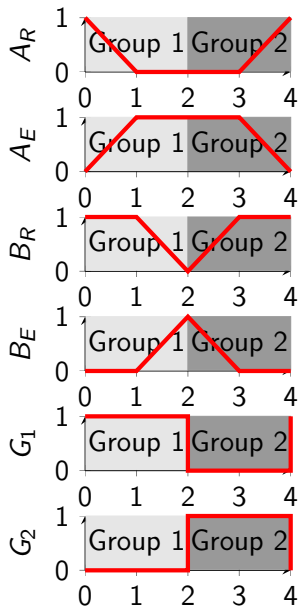

## Control law

$A_R$	$A_E$	$B_R$	$B_E$	$G_1$	$G_2$	$u_{A+}$	$u_{A-}$	$u_{B+}$	$u_{B-}$
1	0	1	0	1	0				
0	1	1	0	1	0				
0	1	0	1	0	1				
0	1	1	0	0	1				

## Implementing the control law


+24V



$u_{A+}$  0V



$u_{A-}$

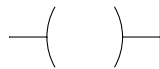



$u_{B+}$



$u_{B-}$



## Implementing the group transitions

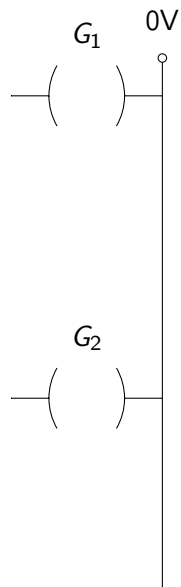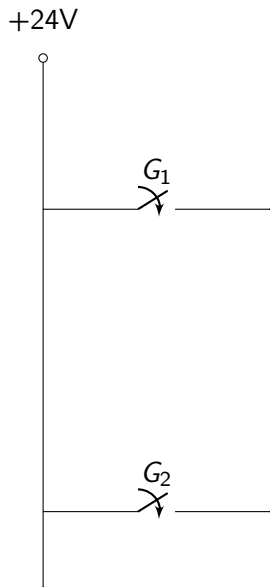



# Implementing the proximity sensor circuit

