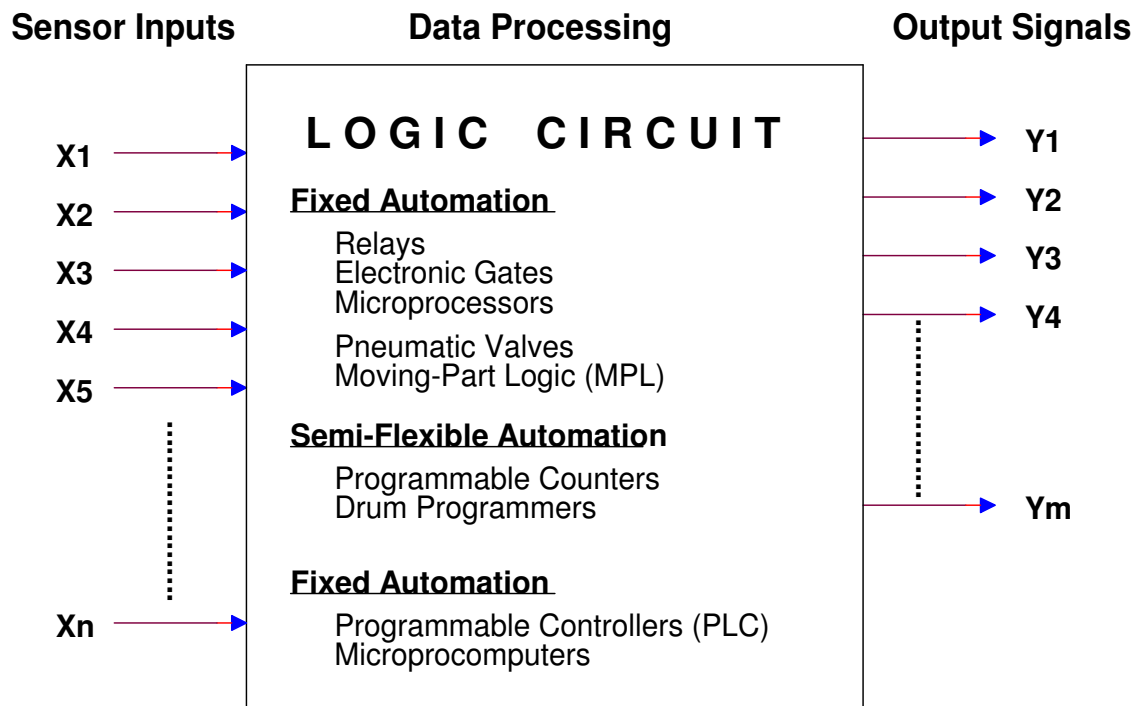


INDUSTRIAL AUTOMATION

SEQUENCE CONTROL



TYPICAL OUTPUT DEVICES

Pneumatic or Hydraulic Cylinders
Pneumatic or Hydraulic Motors
Solenoid Valves
Electric Motors

- Pumps
- Conveyor Belts
- Lifting Devices
- Robot Arms

Heaters
Timers
Lamps
Audible Signals (Bells, Buzzers, Sirens)
Numerical Displays

הפקולטה להנדסת מכונות

הטכניון - מכון טכנולוגי לישראל
אוקטובר 2005

אוטומציה תעשייתית (035008) דף מידע לסטודנט

מרצה הקורס
אסיסטנט/ית הקורס
דן קנושר, טל. 04-8712774 , 0546-484-231

פרק	נושא	מבוא לבקרה	תיעוד קודם
1	אלגברה בוליאנית, פישוט פונקציות בינריות ומימושן, מפות קרנו	14	3
2	בנית דיאגרמת סולם (Ladder Diagram) שיטת הקסקדה למסרים	15	5
3	בקר מתוכנת (PLC - Programmable Controllers)	16	10
4	סוגים שונים של אלמנטים בינריים, טכנולוגיות, שימוש למימוש מערכות שערים אלקטרוניים ממסרים (Relays) שסתומים פניאומטיים אלמנטים לוגיים פניאומטיים עם חלקים נעים (MPL)	14	4
5	שיטת הופמן - מערכות עקיבה בעלות אותות כניסה אקראיים		5,6
6	מערכות פיקוד פניאומטיות שיטת הקסקדה הפניאומטית ניצול שסתומים פניאומטיים כאלמנטים לוגיים שיטות לעצירות חירום של מערכות פניאומטיות (Emergency STOP)	13	7
7	תכן מערכות עקיבה מסוג "קלות-לשינוי" (Hardware Programmable Counters, Step) מפסק תוף צועד (Drum Programmable Counters) מונים מתוכנתים (Counters) טבלת זרימה לבחירת השיטה המועדפת לתכן מערכות עקיבה		9
8	מערכות בינריות שונות קוצבי זמן - טיימרים (Timers), Trigger Flip-Flops מונים בינריים (Binary Counters) רגיסטר הזזה (Shift Register) Schmitt Triggers קודים בינריים (Binary Codes), מצפינים (Encoders)		8
9	מערכות איטרטיביות (Iterative Systems)		8

במדה ויתאפשר, יועברו גם נושאים מתוך הרשימה הבאה (ללא קשר לסדר בו הם רשומים):

פרק	נושאי השלמה	מבוא לבקרה	תיעוד קודם
10	מפות "קרנו" מרובות משתנים		1
11	מערכות פיקוד פניאומטיות - שיטת "טבלת הזרימה" הפניאומטית	13	6
12	מפעילי תנועה (Motion Actuators)	12	10
13	חיישנים חשמליים ופניאומטיים (Sensors)	12	12
14	דיאגרמת GRAFCET		5

חומר עזר

1. ספר: **Industrial Automation, by D. Pessen, John Wiley & Sons, 1989**
 2. ספר: מבוא לבקרה ואוטומציה (כרזע קדם והשלמה חלקית של מספר נושאים), הוצאת "מכלול"
 3. אוסף שקפי ההרצאות: תקליטור שמופץ לסטודנטים בתחילת הסימסטר
 3. תרגילי בית להגשה: תקליטור שמופץ לסטודנטים בתחילת הסימסטר (אותו תקליטור)
 4. כמו כן, אפשר להיעזר בספרים שונים על תורת המיתוג (לפי מספר קטלוגי 621.3.06 בספריית הפקולטה).
- הערה: מומלץ לא להיעזר בתקליטור לא עדכני או בחוברות שנמכרו בסימסטרים קודמים, מאחר וחומר העזר ותרגילי הבית מתעדכן כמעט כל שנה.

סידע מחוץ לשעות ההרצאה

בתחילת הסימסטר יימסרו שעות הקבלה של אסיסטנט/ית הקורס. במידת האפשר הן יותאמו לזמנים הנוחים יותר לסטודנטים. ניתן גם לפנות לייעוץ וקבלת מידע אל המרצה. פרטים מדויקים יימסרו בתחילת הסימסטר.

תרגילי בית

הגשת תרגילי הבית היא חובה.
רשימת התרגילים להגשה תימסר בסיום כל הרצאה. התרגילים יוגשו - בזוגות **קבועים** - שבוע ימים לאחר מכן, בתא המיועד לכך (מסומן "אוטומציה תעשייתית"). במקרים של מניעות חמורות מוצדקות (שירות מילואים, מחלה וכו'), יש להגיש לאסיסטנט/ית אישור מתאים. פרט למקרים אלה – הציון לגבי תרגיל שלא הוגש יהיה 0.
תרגילי הבית ייבדקו בידי האסיסטנט/ית. בכל תרגיל יסומנו השגיאות (במדה ויהיו) וציונו. התרגילים יוחזרו בדר"כ שבוע ימים לאחר הגשתם. בכל מקרה של אי בהירות בנושא התרגילים, יש לפנות אל האסיסטנט/ית בלבד.

ציון תרגילי בית

הציון הממוצע של תרגילי הבית ייקבע על סמך **(n-2)** מתוך **n** התרגילים שיינתנו בסימסטר, עם מתן עדיפות לתרגילים בעלי הציונים הגבוהים ביותר. הגשת פחות מ-**(n-2)** מהתרגילים תפגע בהכרח בציון. במקרים בהם יילקח בחשבון, יהיה לציון התרגילים משקל של 15% בחישוב הציון הסופי (ראה הסבר בסעיף "ציון סופי" למטה).

בחינת הסימסטר

הבחינה הסופית תתקיים ביום _____, (מועד א'), וביום _____ (מועד ב').
בבחינה ניתן להיעזר בחומר פתוח איש.

ציון סופי

ציון תרגילי הבית לא יילקח בחשבון במקרים הבאים:

- תרגילי הבית לא הוגשו עקב מניעות חמורות.
- ציון תרגילי הבית גבוה מציון בחינת הסימסטר בלמעלה מ-25%.

במקרים הללו יהיה לציון הבחינה משקל 100% מהציון הסופי.
במקרים בהם ציון תרגילי הבית יילקח בחשבון (15%), יהיה לציון הבחינה משקל 85% מהציון הסופי.

אתר התייעוד באינטרנט – הנדסת מכונות

Meeng.technion.ac.il



studies



here



דוגמה :

רשימת ערכונים ושנויים מגרסה תשס"ד 2003/4
להלן שמות החוברות שעודכנו/נוספו:

שם החוברת	מחבר	שיוך לקורס	מס' קורס	הערות
1 אוטומציה תעשייתית - שקפי הרצאות	קנושר דן	אוטומציה תעשייתית	035008	גרסה מעודכנת
2 אוטומציה תעשייתית – תרגילים	קנושר דן	אוטומציה תעשייתית	035008	גרסה מעודכנת
3 דינמיקה Dynamics	אלטוס אליעזר, מיילס חבין	דינמיקה	034010	גרסה מעודכנת
4 חינוך ובלאי של חומרים – מאמרים/אנגלית	עציון יצחק	חינוך שימון ובלאי של חומרים	036031	גרסה מעודכנת
5 מבוא לגאומטריה תאורית	בירן אדריאן	שרטוט הנדסי	034004	חוברת חדשה
6 מבוא למכניקת הרצף	מיילס חבין	מבוא למכניקת הרצף	036003	גרסה מעודכנת
7 מכניקת מוצקים 2	ליפשיץ יעקב	מכניקת מוצקים 2	034029	גרסה מעודכנת
8 מערכות הידראוליות ופניומטיות	אשל ראובן	תכן מערכות הידראוליות 1+2	034206+034205	גרסה מעודכנת
9 תרמואלסטיות יישומית	מיילס חבין	תרמואלסטיות יישומית	035029	גרסה מעודכנת

INTRODUCTION

Analog/Digital Differences

Switches and Relays

Pneumatic Switching Valves

Cylinder Control and Sensing

Other Switching Elements

0-1

INDUSTRIAL AUTOMATION

Automation of Mechanical Industrial Production Systems
Control Section
On-Off (Binary) Elements and Information
Various Methodes to Obtain Low-Cost Systems

Fig. 0-1 Subject Definition

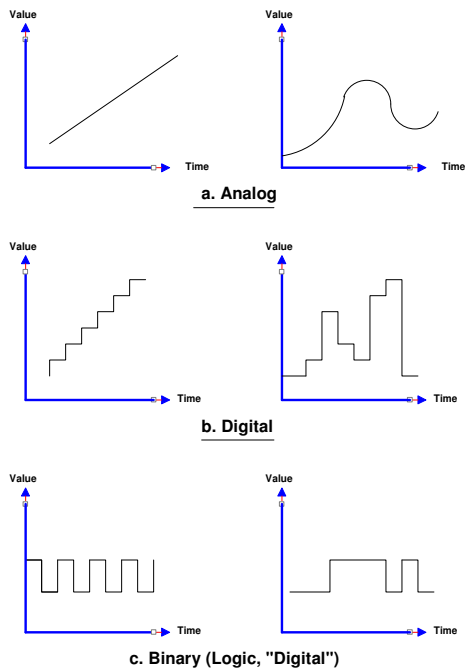


Fig. 0-2 Information Types

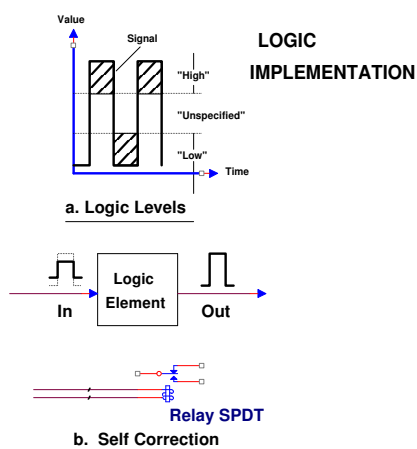



Fig. 0-3 Logic-Levels




a. Electrical Switches




b. Electro-Mechanical Relays

 


c. Electronic Gates

 

d. Pneumatic Valves

 

e. Electrical Limit Switches

 

f. Pneumatic Limit Valves

BINARY SENSORS :

- | | |
|-------------------------------|-----------------------------|
| Flow Switches | Interruptabel-Jet Sensors |
| Temperature Switches | Ultrasonic Sensors |
| Level Switches (Height) | Reed Switches |
| Photoelectric Sensors | Threshold Sensors |
| Pressure Switches | Magnetic Proximity Sensors |
| Back-Pressure Sensors | Inductive Proximity Sensors |
| Annular Back-Pressure Sensors | Inductive Proximity Sensors |

g. Various Elements

Fig. 0-4 Binary (Switching) Elements

CHAPTER 1

BOOLEAN ALGEBRA

Binary Basic

Basic Boolean Operations

Truth Table

De-Morgan Functions

Algebraic Minimization

Karnaugh Map Minimization

BOOLEAN ALGEBRA

1-1

Logic Theory Implementation in Switching
George Boole
False and True replaced by 0 and 1
Binary Items and Variables
Logic , Boolean , Binary , Digital
Switch or Relay ON/OFF Position :
Contacts : Open / Closed
Net : Connected / Not-connected
Binary sensors (Temperature, Pressure, etc)
Representations :
"0" / "1"
"ON" / "OFF"
"HIGH" / "LOW"

a. Basic Definitions

AND	OR	NOT
0.0 = 0	0+0 = 0	0' = 1
0.1 = 0	0+1 = 1	1' = 0
1.0 = 0	1+0 = 1	
1.1 = 1	1+1 = 1 { }	

b. Basic Operators

X.0 = 0	X+0 = X
X.1 = X	X+1 = 1
X.X = X	X+X = X
X.X' = 0	X+X' = 1
X.X.Y = X	
X.X'.Y = X.Y	
X(Y+Z) = XY+XZ	
(X+Y).(X+Z) = X+YZ	
XY+X'Z+YZ = XY+X'Z	

c. Basic Relations

XY+X'Z+YZ = XY+X'Z					
F1 = XY+X'Z+YZ			F2 = XY+X'Z		
X	Y	Z	F1	F2	
0	0	0	0	0	
0	0	1	1	1	
0	1	0	0	0	
0	1	1	1	1	
1	0	0	0	0	
1	0	1	0	0	
1	1	0	1	1	
1	1	1	1	1	

d. Minimization - Truth Table

$XY+X'Z+YZ = XY+X'Z$	
$F1 = XY+X'Z+YZ$	$F2 = XY+X'Z$
If $Z=0$ then :	
$F1 = XY+X'.0+Y.0 = XY$	$F2 = XY+X'.0 = XY$
If $Z=1$ then :	
$F1 = XY+X'.1+Y.1 = XY+X'+Y = X'+Y$	$F2 = XY+X'.1 = X'+XY = X'+Y$

e. Minimization - Math Operations

NAND (NOT AND) :	X nand Y = (X.Y)'
NOR (NOT OR) :	X nor Y = (X+Y)'
XOR (Exclusive OR)	X xor Y = X'Y+XY'
INHIBITION	X.Y'
IMPLICATION	X+Y'

f. More Useful Operators

(A.B)' = A'+B'
(A+B)' = A'.B'
Implementations :
(A.B+A'.C)' = (A'+B').(A+C)
(AB(C'+DE))' = A'+B'+C(D'+E)

g. DeMorgan Theorem

AND , OR , NOT	
AND , NOT	A+B = (A'.B')'
OR , NOT	A.B = (A'+B')'
NAND	A' = (A.A)' = (A NAND A) A+B = (A'.B')' = ((A.A)'.(B.B))' = = (A NAND A) NAND (B NAND B)
NOR	A' = (A+A)' = (A NOR A) A.B = (A'+B')' = ((A+A)'+(B+B))' = = (A NOR A) NOR (B NOR B)

h. Universal Systems

A	B	C	D	F
0	0	0	0	0
0	0	0	1	0
0	0	1	0	1
0	0	1	1	1
0	1	0	0	1
0	1	0	1	1
0	1	1	0	0
0	1	1	1	1
1	0	0	0	0
1	0	0	1	0
1	0	1	0	1
1	0	1	1	1
1	1	0	0	0
1	1	0	1	0
1	1	1	0	1
1	1	1	1	1

1. Universal Sum-of-Products :
2. Universal Products of Sum :
3. Minimal Sum-of-Products :
4. Minimal Products of Sum :

1. Universal Sum-of-Products :
f(A,B,C,D) = A'B'CD'+A'B'CD+A'BC'D'+A'BCD+
+ AB'CD'+AB'CD+ABCD'+ABCD
2. Universal Products of Sum :
f'(A,B,C,D) = A'B'C'D' + A'B'C'D + A'BCD' + AB'CD' +
+ AB'C'D + ABC'D' + ABC'D
3. Minimal Sum-of-Products :
f(A,B,C,D) = (A+B+C+D)(A+B+C+D')(A+B'+C+D)(A'+B+C+D).
(A'+B+C+D')(A'+B'+C+D)(A'+B'+C+D')
4. Minimal Products of Sum :
f(A,B,C,D) = (A'+C)(B+C)(A+B'+C'+D)

i. Functions Basic Representations

Fig. 1-1 : Boolean Algebra Concepts

1-2

INSURANCE COMPANY REQUIREMENTS

AN INSURANCE COMPANY SELECTS CLIENTS ACCORDING TO THE FOLLOWING
CRITERIA : NATIONALITY, GENDER, AGE AND HAVING DRIVING-LICENSE.
CLIENT MUST SATISFY AT LEAST ONE OF THE FOLLOWING CONDITIONS :

and/or ISRAELI
and/or NON-ISRAELI UNDER 50 WITH DRIVING LICENSE
and/or NON-ISRAELI MALE 50 OR ABOVE
and/or NON-ISRAELI UNDER 50 WITHOUT DRIVING LICENSE

FIND THE MINIMAL REQUIRED CONDITIONS

a. System Definition

CRITERIA	VARIABLE	1	0
NATIONALITY	A	ISRAELI	NON-ISRAELI
GENDER	B	MALE	FEMALE
AGE	C	50 OR ABOVE	UNDER 50
LICENSE	D	HAS LICENSE	DOESN'T HAVE LICENSE

b. Boolean Variables Assignment

$$T = A + A'C'D + A'BC + A'C'D' = A + A'(C'D + BC + C'D')$$

$$= A + C'D + BC + C'D' = A + C'(D + D') + BC = A + C' + CB = A + B + C'$$

c. Direct Minimization

$$T = A + A'B'C'D + A'B'C'D + A'BC'D + A'BC'D + A'BCD + A'BCD$$

$$= A + A'(B'C'D + B'C'D + BC'D + BC'D + BCD + BCD) =$$

$$= A + B'C'D + B'C'D + BC'D + BC'D + BCD + BCD =$$

$$= A + B'C'(D + D) + BC'(D + D) + BC(D + D) =$$

$$= A + B'C' + BC = A + B'C' + B(C + C) =$$

$$= A + B'C' + B$$

$$= A + C' + B$$

e. Truth Table Minimization

SIMPLIFIED RESULT :

and/or ISRAELI
and/or UNDER 50
and/or MALE

A	B	C	D	T
0	0	0	0	1
0	0	0	1	1
0	0	1	0	0
0	0	1	1	0
0	1	0	0	1
0	1	0	1	1
0	1	1	0	1
0	1	1	1	1
1	0	0	0	1
1	0	0	1	1
1	0	1	0	1
1	0	1	1	1
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	1

d. Truth Table

f. Minimal Requirements

Fig. 1-2 : Algebraic Minimization (1)

AN OCTAL NUMBER IS DEFINED BY THE BINARY COMBINATION X_2, X_1, X_0

WHERE $N(X_2, X_1, X_0) = 4.X_2 + 2.X_1 + 1.X_0$

A COMBINATIONAL SYSTEM DETECTS IF THE NUMBER IS DIVIDABLE
BY EITHER 2 OR 3

a. System Definition

X2	X1	X0	T
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0



b. Block Diagram

$$T = X_2'X_1'X_0' + X_2'X_1.X_0' + X_2'X_1.X_0 +$$

$$+ X_2.X_1'X_0' + X_2.X_1.X_0'$$

$$= X_0'(X_2'X_1' + X_2'X_1 + X_2X_1' + X_2X_1) + X_2'X_1X_0 =$$

$$= X_0'(X_2'(X_1' + X_1) + X_2(X_1' + X_1)) + X_2'X_1X_0 =$$

$$= X_0'(X_2' + X_2) + X_2'X_1X_0 =$$

$$= X_0' + X_2'X_1X_0 =$$

$$= X_0' + X_2'X_1$$

d. Minimization Steps


c. Truth-Table

Fig. 1-3 : Algebraic Minimization (2)


Karnaugh Maps

- * Visual method for boolean functions minimization
- * Each variable occupies half map
- * n variables split map into 2^n basic cells, named map Elements
- * Each element is represented by a n-variable boolean product, named "Minterm"
- * Any two adjacent elements are represented by two "Adjacent" minterms
- * Merging two adjacent elements produces a 2-elements cell, represented by a product of (n-1) variables
- * Two adjacent 2-element cells may be merged into a 4-elements cell, represented by a product of n-2 variables, and so on


a. Map Concepts and Basic Properties

 

b. 2-Variables Map Representations

 

c. 3-Variables Map Representations

 

d. 4-Variables Map Representations

Fig. 1-4 : Karnaugh Maps Concept

GROUPS SELECTION - ESSENTIAL AND NON-ESSENTIAL CANDIDATES

An international company has to hire employees that will be available, as a group, to support the following 6 languages :

Hebrew , English , Russian , Arabic , Rumanian , French

Of course, the company target is to hire the minimal number of employees, and get the required support.

5 candidates look for that job. Next table specifies the language knowledge of each candidate :

Candidate A	Candidate B	Candidate C	Candidate D	Candidate E
Hebrew English Russian Arabic	Hebrew English Romanian	Russian Arabic	Hebrew French	Arabic Russian

There are many available combinations, but we can make the selection easier :

1. Check if there are ESSENTIAL candidates, that is to say candidate that support at least a single language, that none of the others does. These candidates are called ESSENTIAL, since are non-replacable by any of the other candidates.
2. Since all ESSENTIAL candidates (if there are any) must be a part of any selection option, we first identify them and select them.
3. NON_ESSENTIAL candidates doesn't mean that they will not be selected. NON_ESSENTIAL. Since any of them may be replaced by others, no one can decide - on first glance - which of them must be selected, or not.
4. Actually, some (or all) NON_ESSENTIAL will have to be selected in case that the ESSENTIAL candidates do support all required languages.
5. We can see easily that French is supported by candidate D only, and Romanian is supported by candidate B only. This makes D and B ESSENTIAL. Each of all other languages is supported by at least 2 candidates, so all those candidates are NON_ESSENTIAL.
6. Selection of candidates B and D (ESSENTIAL) cover more than the 2 mentioned languages; they also support Hebrew and English, so we don't have to worry about support of these 4 languages.
7. Selecting all ESSENTIAL candidates, don't cover the left languages Arabic and Russian. So, we must look for the minimal additional candidates that will complete the selection. This selection is simpler.
8. In this case, either A or C complete the required support, so the minimal selected group contains 3 candidates (2 ESSENTIAL and 1 NON_ESSENTIAL).
9. There is no other option to support Arabic and Russian by a single candidate, so there are two minimal available selections :
 - a. { A , B , D }
 - b. { B , C , D }
10. Principally, both selections are minimal. On the other hand candidate A has higher priority than C since he supports 4 languages and may be more helpful, and a backup to the other languages that had been covered by the ESSENTIAL candidates.
11. This means that first minimal selection (a) is preferable, which leaves a single minimal solution.

Fig 11-5 : ESSENTIAL and NON_ESSENTIAL concept

Fig. 1-6 : Example 1

Essential cells : 3
Non-Essential cells : 0
Minimal solutions : 1
 $F = AD + C'D + A'CD'$


 


Fig. 1-7 : Example 2

 Essential cells : 4
Non-Essential cells : 1
Minimal solutions : 1
 $F = A'C'D + ACD + A'BC + ABC'$



Maps Definitions

- I Function "Area"
- II All (Maximal) Cells
- III Minimal Solution 1
- IV Minimal Solution 2
- V Minimal Solution 4

Fig. 1-8: Example 3

Essential cells : 2
Non-Essential cells : 2
Minimal solutions : 2
 $F_1 = BC + B'C'D + A'BD$
 $F_2 = BC + B'C'D + A'CD$

 


Fig. 1-9 : Example 4

Essential cells : 3
Non-Essential cells : 2
Minimal solutions : 1
 $F = AC + B'C + A'BC' + CD$

 


Fig. 1-10 : Example 5

Essential cells : 2
Non-Essential cells : 4
Minimal solutions : 4
 $F_1 = A'C' + AC + ABD + AB'D'$
 $F_2 = A'C' + AC + ABD + B'C'D'$
 $F_3 = A'C' + AC + BC'D + AB'D'$
 $F_4 = A'C' + AC + BC'D + B'C'D'$

 


Fig. 1-11 : Example 6

Essential cells : 0
Non-Essential cells : 6
Minimal solutions : 2
 $F_1 = ABC + BC'D + A'BD'$
 $F_2 = BCD' + ABD + A'BC'$


 


Fig. 1-12 : Example 7

 

Maps Definitions

- I Function "Area"
- II All (Maximal) Cells
- III Minimal Solution 1
- IV Minimal Solution 2
- V Minimal Solution 4

Essential cells : 0
Non-Essential cells : 12
Minimal solutions : 6
 $F1 = A'C' + B'D' + AB + CD$
 $F2 = BD + AC + A'B' + C'D'$
 $F3 = AD + BC + CD + A'B'$
 $F4 = A'D + B'C + AB + C'D'$
 $F5 =$
 $F6 =$

Fig. 1-13 : Example 7.1

Essential cells : 2
Non-Essential cells : 0
Minimal solutions : 1
 $F' = A'BCD' + AB'C'D$
 $F = (A + B' + C' + D)(A' + B + C + D')$

 


Fig. 1-14 : Example 8

Essential cells : 2
Non-Essential cells : 1 (+2)
Selected Don't Cares : All
Minimal solutions : 1
 $F = AD' + A'B' + BCD$


 


Fig. 1-15 : Example 8.1

 Essential cells : 0
Non-Essential cells : 8
Selected Don't Cares : None
Minimal solutions : 1
 $F' = AB'D + A'BD' + BCD$
 $F = (A' + B + D')(A + B + D)(B + C + D)$



1-5

Fig. 1-16 : Example 9

Essential cells : 0
Non-Essential cells : 3 (+5)
Selected Don't Cares : None
Minimal solutions : 1
 $F = AC' + C'D + A'CD'$

 


Fig. 1-17 : Example 10

Essential cells : 2
Non-Essential cells : 1
Selected Don't Cares : Partial
Minimal solutions : 1
 $F = AD + A'D'$


 


Fig. 1-18 : Example 11

 
Essential cells : 1
Non-Essential cells : 5
Selected Don't Cares : Partial
Minimal solutions : 2
 $F1 = ACD + AB + A'C'$
 $F2 = ACD + AB + A'D'$
Note : F1 and F2 are equivalent but not identical



1-6

X	Y	Z	M
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

a. Truth-Table



 


b. Karnaugh-Map

Fig. 1-19 : Majority Function

X	Y	Z	A	B	C
0	0	0	0	0	0
0	0	1	1	0	0
0	1	0	1	0	0
0	1	1	1	1	0
1	0	0	1	0	0
1	0	1	1	1	0
1	1	0	1	1	0
1	1	1	1	1	1

a. Truth-Table

   

b. Karnaugh-Maps

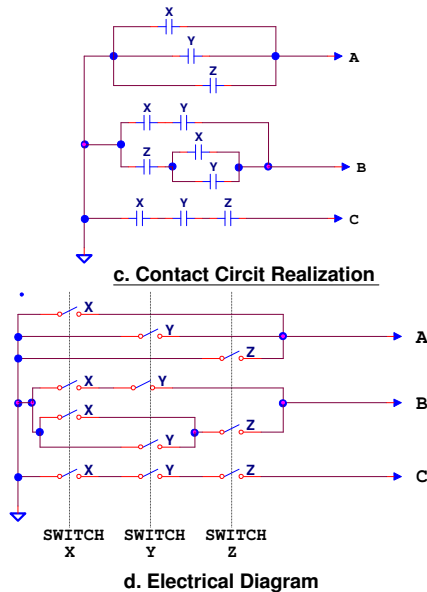


Fig. 1-20 : Motor Operation Control
(Exer 1-7)

BCD to 7-SEGMENTS CONVERTER

Design a combinational circuit that gets a BCD input, and converts it to 7-Segment display.


BCD is short form of Binary-Coded-Decimal. It Represents 10 decimal digits (0-9) in 4-bit binary code (0000-1001).

Binary combinations 1010-1111 (above decimal 9) may not appear as inputs, and are referred as don't-care.

a. System Definition

0 1 2 3 4 5 6 7 8 9


b. 7-Sgments Arrangement

 


c. Block Diagram

D3	D2	D1	D0	A	B	C	D	E	F	G
0	0	0	0	0	1	1	1	1	1	0
0	0	0	1	0	1	1	1	1	0	1
0	0	1	0	1	1	1	0	1	1	1
0	0	1	1	1	1	0	1	1	1	1
0	1	0	0	1	1	0	1	1	1	0
0	1	0	1	1	1	0	1	1	1	0
0	1	1	0	1	1	0	1	1	1	0
0	1	1	1	1	1	0	1	1	1	0
1	0	0	0	1	1	1	1	1	1	1
1	0	0	1	1	1	1	1	1	1	1
1	0	1	0	-	-	-	-	-	-	-
1	0	1	1	-	-	-	-	-	-	-
1	1	0	0	-	-	-	-	-	-	-
1	1	0	1	-	-	-	-	-	-	-
1	1	1	0	-	-	-	-	-	-	-
1	1	1	1	-	-	-	-	-	-	-

d. Truth-Table (Partial)

 

e. Karnaugh Map of "E"

 

f. Karnaugh Map of "A"

Fig. 1-21 : BCD to 7-Segments

1-7


 



Fig. 1-22 : Various Switches and Relays Types

$$T = AB + AC + BC = AB + (A + B)C$$


a. Majority Boolean Function

 


b. Switches-Operated Circuit

 

c. Contacts Circuit

 


 d. Switches Remote Operation
9 Long Lines, Carrying High Current




e. Relays Remote Operation
3 Long Lines, Carrying Low Current


Fig. 1-23 : "MAJORITY" Function Circuit

 

a. Block-Diagram

 


b. Switches-Operated Circuit

 

Long lines, high power dissipation

c. Contacts Circuit

 

d. Relays-Operated Circuit

Fig 1-24 : 3-TO-8 DECODER CIRCUIT

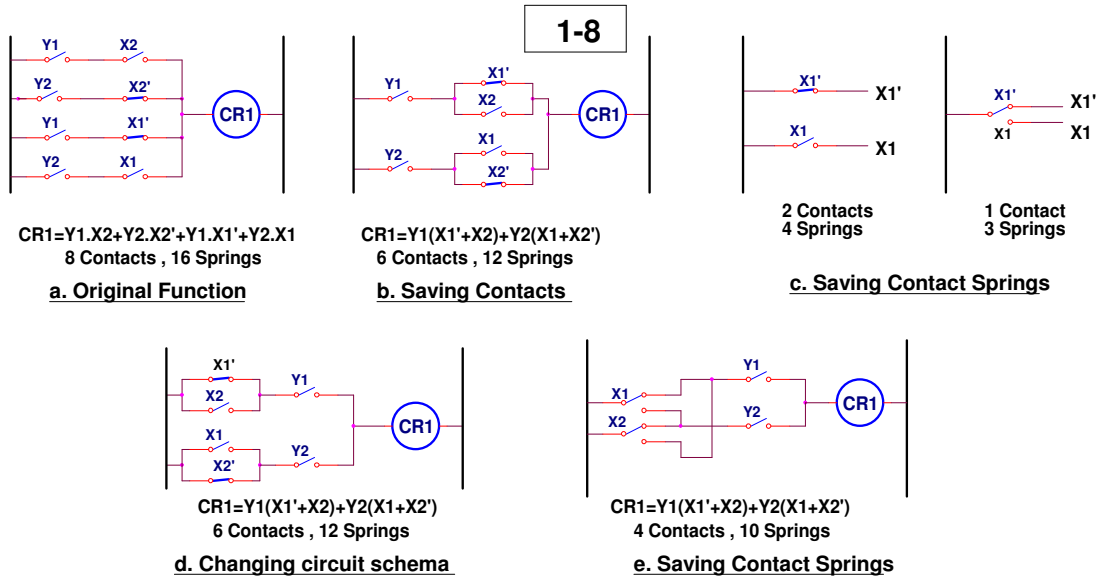


Fig. 1-25 : Saving Contacts and Contacts Springs

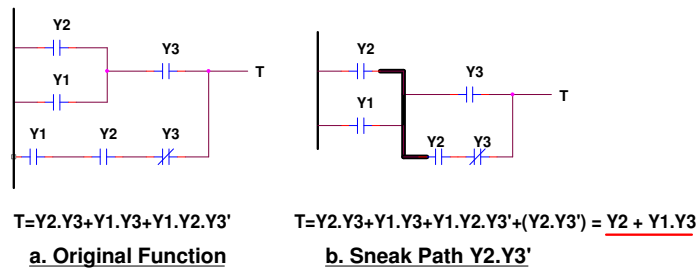


Fig.1-26 : Sneak Path Creation

 


Fig. 1-27 : Devices Outputs (fan-out)

	NOT	AND	OR	EXCLUSIVE OR	NOR	NAND	INHIBITION	FLIP-FLOP
Old European Symbols								
Old USA Symbols								
New Symbols Recommended by ISO								


Fig. 1-28 : Logic Gate Symbols

1-9




$$T = BC' + A'C'D = C'(B + A'D)$$

a. Prime Cells Selection

 


b. Gates Implementation of (a) - 5 Gates

 


$$T = BC'D + A'C'D = (B + A')C'D$$

c. Non-Prime Cells Selection

 


d. Gates Implementation of (c) - 4 Gates

Fig. 1-29 : Minimize by Selecting Non-Prime Cells

 


a. General Case

 

b. Specific Case

Fig. 3-30 : Multiple Output System

 


$$T1 = AC' + BCD$$

(Instead of $A'C + BD$)

a. Function T1

$$T2 = A'B + BCD$$

b. Function T2

 

c. Gates Implementation

Fig. 1-31 : Minimize by Selecting Non-Prime Cells, in Multiple-Output System

CHAPTER 2

RELAYS CASCADE SYSTEMS

Ladder Diagram

Relays, Cylinders, Valves Symbols

Sequential Sequences

Relays Cascade Implementation

Huffman Method

Flow Diagram


Primitive and Merged Flow

Tables

State Assignment


Output and Excitation Functions

2-1

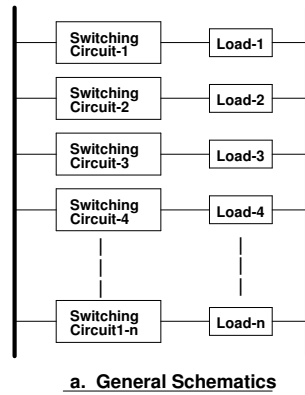


a. General Schematics

Fig. 2-1 : Ladder Diagram

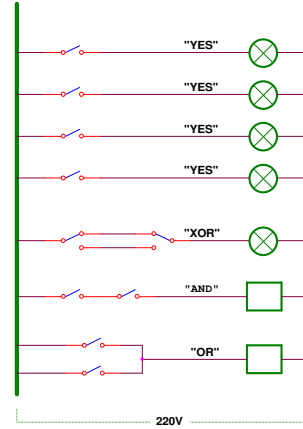

 
b. Example - Home Electric Ladder Network



a. Basic Circuit




b. Basic Contacts Circuit

 


c. General Circuit

Fig. 2-2 : Set-Reset Relay Flip-Flop

 


a. Example - Schematic Circuit

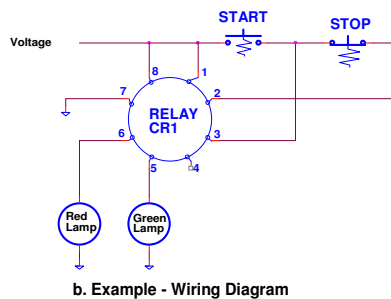

b. Example - Wiring Diagram


Fig. 2-3 : Flip-Flop Implementation Example

 

a. Valve Without Return Spring


b. Valve With Return Spring

Fig. 2-4 : Cylinder Actuation Valves

 


a. Position "-"

b. Position "Moving"

 

c. Position "+"

Fig. 2-5 : Positions of Cylinder Limit Switches

 


a. Normally Open



b. Normally Closed

Fig. 2-6 : Graphic Symbols of Limit Switches

 A Sequence of Drilling Two Holes in a Wooden Plate



Cylinder "A" fastens/releases the wooden plate.
Cylinder "B" lowers and lifts a driller..

a. Process Mechanical Representation


Process starts by pressing START pushbutton

1. Cylinder "A" fastens the wooden plate
2. Cylinder "B" lowers the driller thus performing drilling action
3. Cylinder "B" lifts the driller thus disconnecting it from the plate
4. Cylinder "C" shifts the driller to next hole location.
5. Cylinder "B" lowers the driller thus performing drilling action
6. Cylinder "B" lifts the driller thus disconnecting it from the plate
7. Cylinder "C" returns the driller to its initial position, and cylinder "A" releases the wooden plate.

b. Sequence Description


START , A+ ,B+ ,B- , C+ ,B- , (A- , C-)

c. Sequence Short Representation

 


d. Cylinders Sequence Process Chart


Fig. 2-7 : Process Sequence Representations

 

A. Cylinders Position Chart

 

B. Cylinders Position Chart & Contacts

 

C. Cylinders Position Chart, Contacts & Valves Position

Fig. 2-8 : Sequence Chart Diagram

2-3


START,A+,A-,B+,10 Sec delay,B-

(STEPS 1 2 3 4 5)


a. Process Sequence (No Return Springs)




b. Step 1 : Actuate A+

 


c. Step 2 : Actuate A-

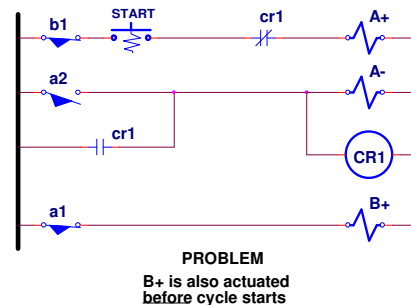

d. Step 3 : Correct and Actuate B+

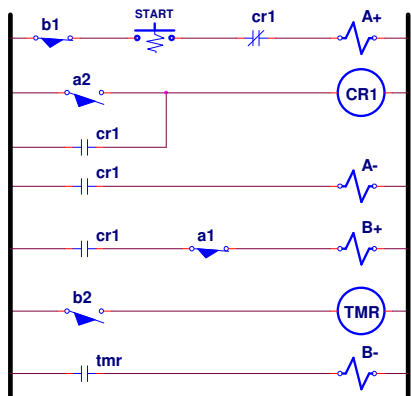


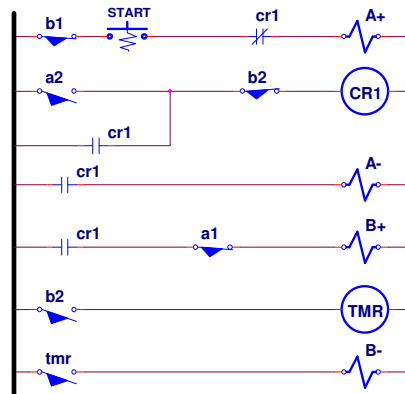e. Steps 4-5 : Correct and Actuate TMR and B-



Add reset (b2') to CR1

f. Correct problems of (e)

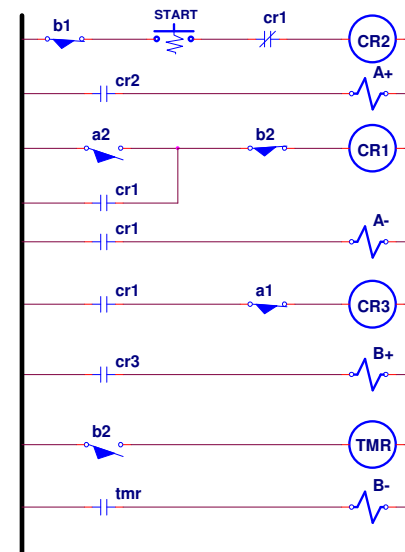

g. Isolate Limit Swithes from Solenoids Current

Fig. 2-9 : "Intuitive" Design Problems


RELAYS CASCADE SYSTEMS

- * Avoid conflicting actuation of a cylinder
- * Distinguish between situations where a cylinder performs more than a single cycle
- * Maximal size groups (to obtain minimum number of group relays)
- * Same "Letter" may appear no more than once in a group (to avoid conflicted commands to a cylinder)
- * Except for specific cases, groups Partitioning doesn't depend on having or not having valves return springs

Fig. 2-10 : Cascade Method Target & Rules

START , A+ , A- , B+ , C+ , $\begin{bmatrix} C- \\ A+ \end{bmatrix}$, A- , B-

a. Sequence List Representation

 

b. Sequence Chart Representation

Fig. 2-11 : Typical Process Definition

 


Fig. 2-12 : Typical Groups Partitioning


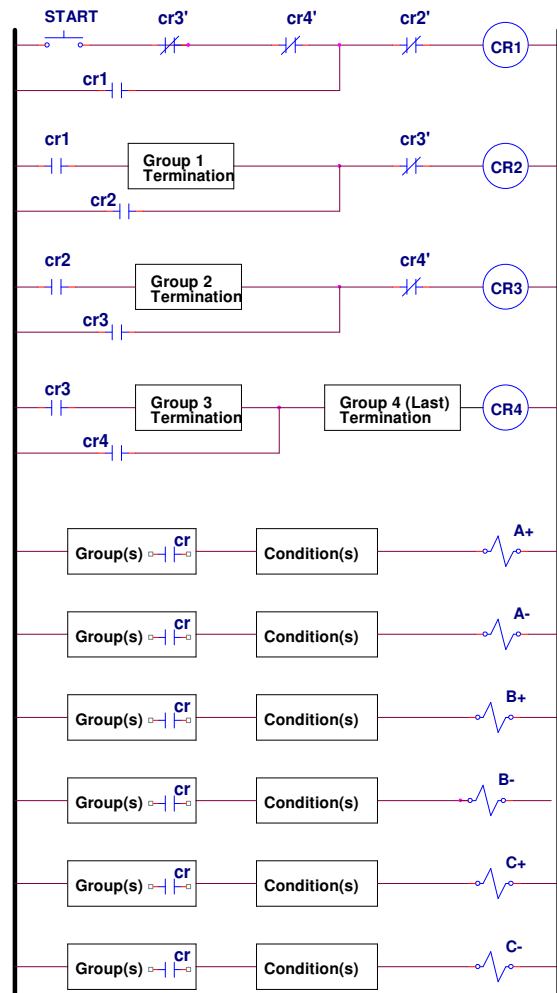



Fig. 2-13 : Typical Initial Cascade Circuit,
of 3-Cylinder / 4-Groups Process

 


START, A+, B+, C+, C-, A-, D+, A+, D-, B-, A-,

1. Cylinders are actuated by 5/2 valves with return springs.
2. Valves are actuated electrically (solenoids).

a. Process Sequence Information

 

b. Groups Partition

 

d. Complete Circuit

c. Total Initial Circuit


Notes : CR4 been canceled (useless).
Rset CR3 been corrected
Contact a1 been added to Set CR1

Fig. 2-17 : Relay Cascade Design Process 2
(With Return Springs)


START, A+, B+, C+, C-, A-, D+, A+, D-, B-, A-,

1. Cylinders are actuated by 5/2 valves without return springs.
2. Valves are actuated electrically (solenoids).

a. Process Sequence Information

 

b. Groups Partition

 

c. Total Initial Circuit

d. Complete Circuit

Fig. 2-16 : Relay Cascade Design Process 2
(Without Return Springs)


"ON-DELAY" TIMER DEFINITION

As long as input is "0", output is also "0".

When input changes from "0" to "1", output change to "1" is delayed by T sec.

When input changes from "1" to "0", output changes to "0" immediately, and time count resets t

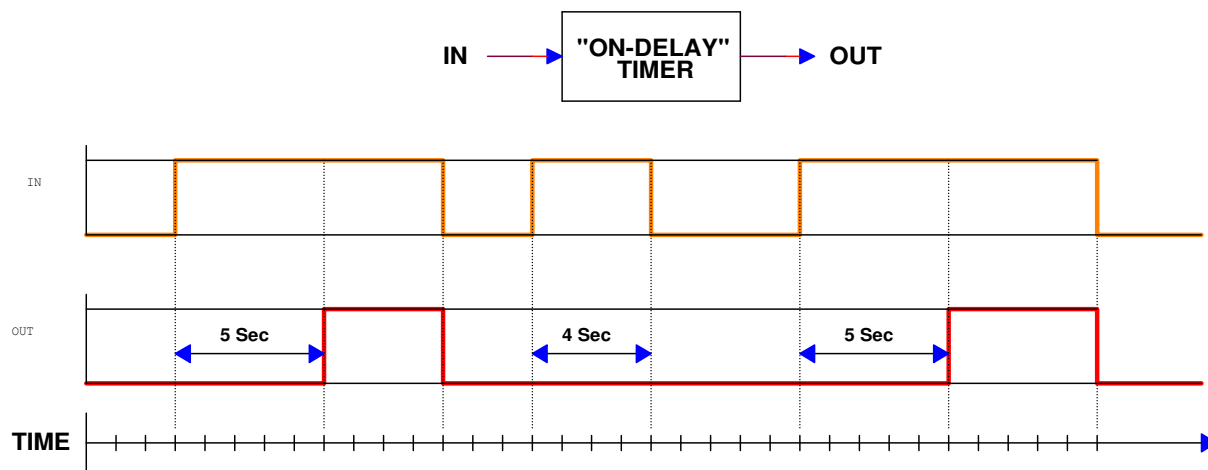Note : Element behaves as a slow activated relay : it changes to active state only T sec after been energized, but returns to rest state as soon as energizing terminates.



Timing chart of a 5-Sec delay timer (example)

Fig. 2-17 : "On-Delay" Timer Definition

CHAPTER 3

PLC

(Programmable Logic Controller)

PLC Definition

PLC Hardware Control System

PLC Programming

Programming LIFO Stack

Implementation

Timers and Counters

Modified Programming Commands


Standard I/O

PLC - Programmable Logic Controller

3-1

Micro-computer for controlling industrial processes
First applied at 60th-70th
Implement binary and analog signals, PID
Eliminate need to implement relays and its wiring
Cost economical, requires small space
Contains timer' counters and more
Perfect reliability
Solution to the design of complex systems
Easy to program and easy to change it
Input/output are adapted to high voltage/current devices
Reliable operation under industrial conditions
Built in self diagnostics
May be controlled and monitored by central computer
Not economic for small control processes
Slow but OK for industrial timing

a. General

 

b. Block Diagram of PLC

3-1. Programmable Controller (PLC) Representation

Limit Switches
Proximity Switches
Photoelectric Switches
Sensor Switches (Level, Pressure, Temperature etc)
Push-Button Switches
Selector Switches
Relay Contacts

a. Discrete Input Devices to PLC

Contact Relay Coils
Valve Solenoids
Pneumatic or Hydraulic Cylinders and Motors
Lights
Audible Alarms (Bells, Buzzers, Sirens)
Fans
Heaters
Motor Starters

b. Discrete Output Devices Actuated by PLC

12, 24, 48, 120, 230 Volt AC
12, 24, 48, 120, 230 Volt DC
5V DC (TTL Level)
Contact Relay Output

c. Standard Discrete I/O Interface Modules

3-2. PLC Interfaces

Field signal may not be connected directly to PLC
Converts field signals to logic level, and vica versa
Adapted to implement DC and AC signals
Contains protection from voltage transients and noise
Contains protection from opposite polarity connections
Electrical common isolation
Expensive
Adapted to work in industrial conditions

3-3 Input/Output Modules

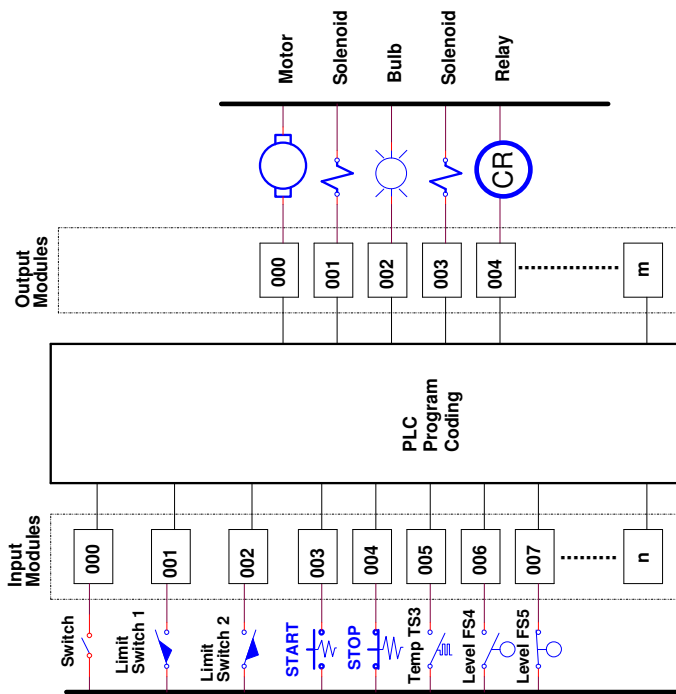


Fig. 3-4 : General I/O Connection Diagram



 


Fig. 3-5 : Different I/O Connection Location

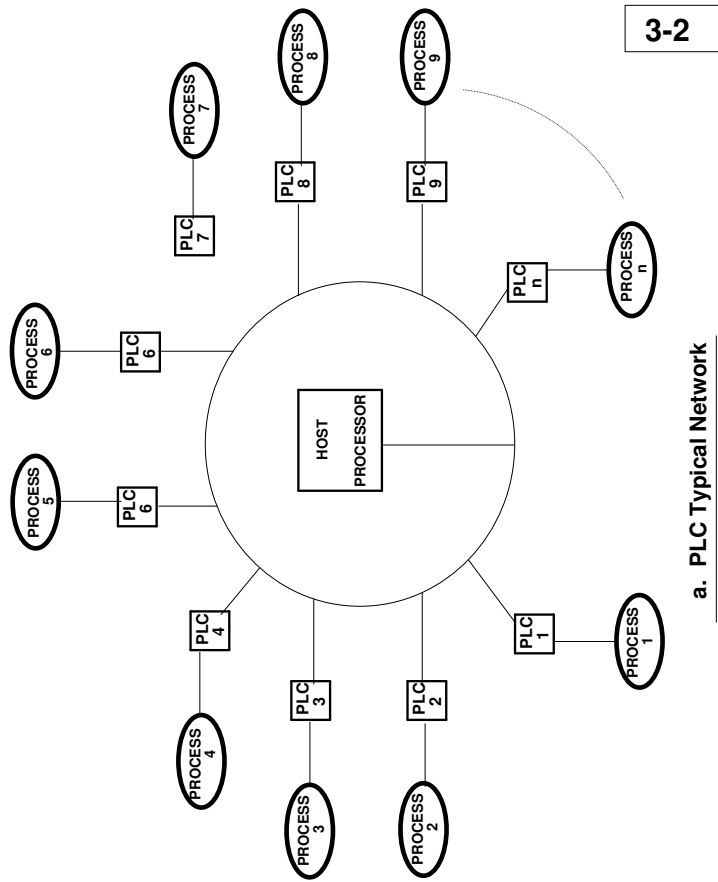

a. PLC Typical Network

 

b. Several Possible LAN Topologies

Fig. 3-6: PLC Macro Networks

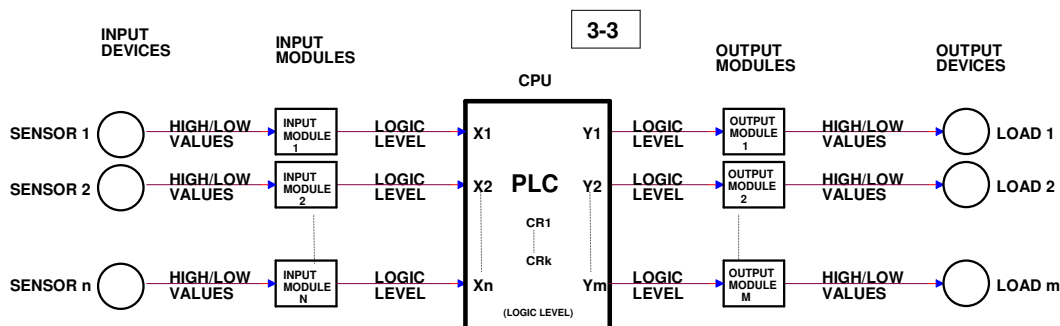


Fig. 3-7 : PLC General Configuration

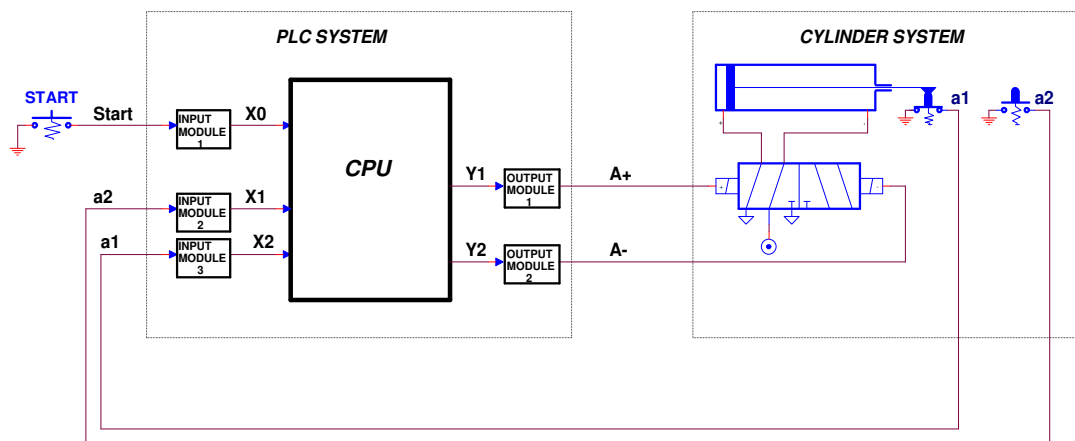


Fig. 3-8 : Typical PLC Control System Example


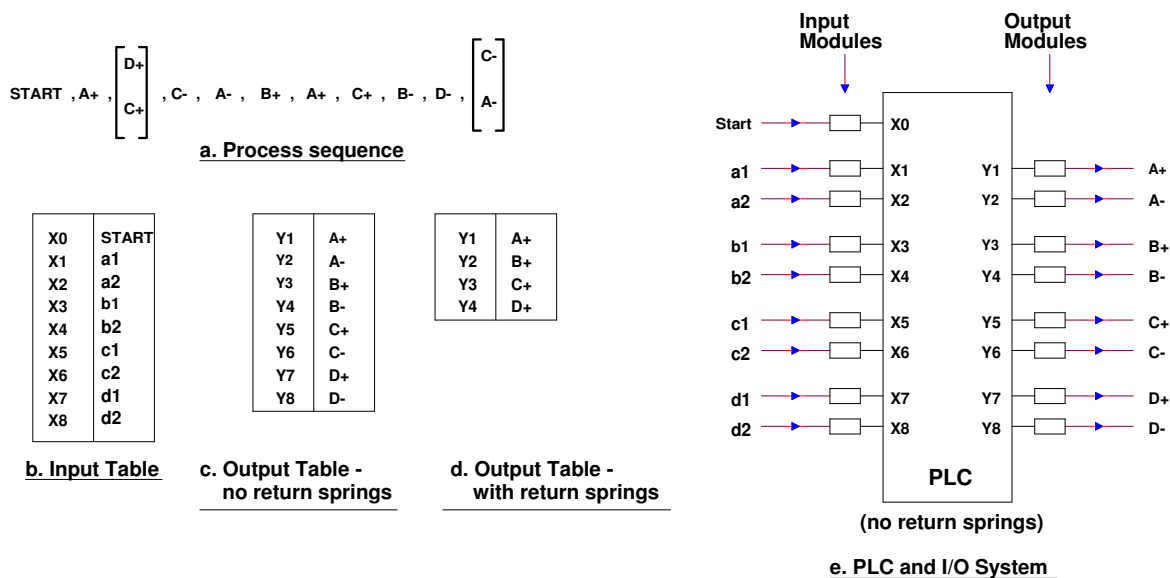


Fig. 3-9 PLC I-O Variables Assignment

3-4

 

Typical air-condition system is operated by two push-button switched :

START button that operates the system


STOP button that deactivate the system

System is turned-on by pressing STARTbutton, and remains activated after releasing the button

System is tuened-off by pressing STOP button, and remains de-activated after releasing the button


A red LED is illuminated as long as the system in on

 In addition, control circuit is also equipped with a temperature sensor, that protects the system from over-heat (by turns it off)




b. Block Diagram

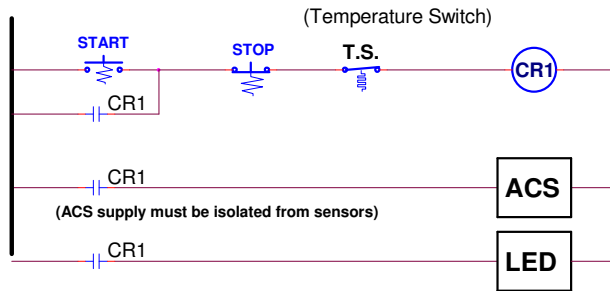a. Air-Condition System (ACS) representation




c. Relay Ladder Diagram for ACS

 


e. PLC "Internal" Ladder Diagram

	INPUT MODULE	OUTPUT MODULE
Start	X17	
Stop	X18	
T.S.	X19	
ACS		Y13
LED		Y15

d. I/O Assignment Table

 

f. Simplified Ladder Diagram

 

d. PLC Ladder Diagram

STORE	X17
OR	Y13
AND NOT	X18
AND NOT	X19
OUT	Y13
OUT	Y15

g. PLC Program

Fig. 3-10 PLC Control for Air-Condition System (ACS)

3-5


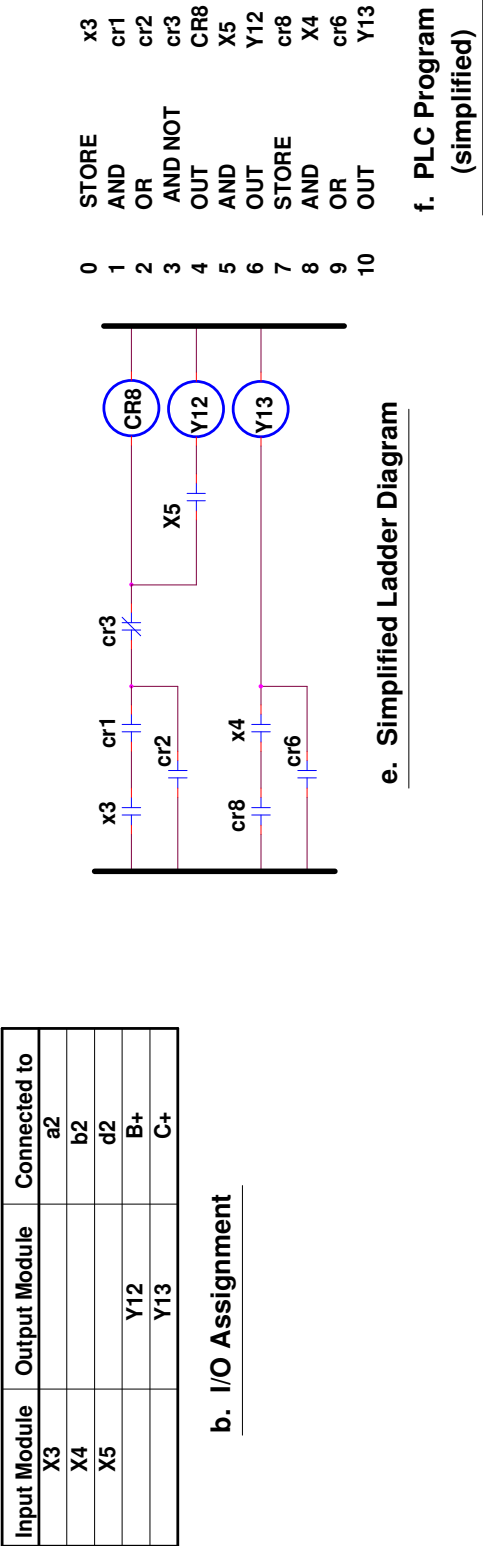
 


Fig. 3-11 : Simplification of PLC Ladder Diagram


3-6

Command STORE first stores current value in a stack, while "pushing down" previous stack elements, and then clears latest calculated value. Action is similar to loading weapon stack.

 Commands that refer to stack - such as "AND STORE", "OR STORE" etc - perform operation on current "upper" stack element (the one that been last entered), and deletes that element from stack, while "Pushing up" previous elements. Action is similar to unloading a weapon stack, or shooting.




3-12 PLC LIFO Stack concepts

 

a. Ladder Diagram

0	STORE NOT	X2
1	AND	CR10
2	STORE NOT	X4
3	AND	CR11
4	OR	STORE
5	OUT	Y5

b. PLC Programming of (a)

 


a. Ladder Diagram

STORE NOT	X1
AND	CR5
STORE NOT	X2
AND NOT	CR6
OR	STORE
STORE NOT	CR10
AND NOT	CR11
STORE	CR2
AND NOT	CR3
OR	STORE
AND	STORE
OUT	CR1

b. PLC Programming of (a)

Fig. 3-13 : Use of LIFO Memory Stack

Fig. 3-14 : Multiple Use of LIFO Stack

 

a. Ladder Diagram

0	STORE NOT	X2
1	AND	CR10
2	STORE NOT	X4
3	AND	CR11
4	OR	STORE
5	STORE NOT	X1
6	AND	X3
7	OR	STORE
8	OUT	Y4

b. PLC Programming Option 1


0	STORE NOT	X2
1	AND	CR10
2	STORE NOT	X4
3	AND	CR11
4	STORE NOT	X1
5	AND	X3
6	OR	STORE
7	OR	STORE
8	OUT	Y4

c. PLC Programming Option 2


3-15 : LIFO Use Options

STORE	x0	STORE	x0
AND NOT	cr3	AND NOT	cr3
AND NOT	cr4	AND NOT	cr4
OR	cr1	OR	cr1
AND NOT	cr2	AND NOT	cr2
OUT	CR1	OUT	CR1
AND	x6	AND	x6
OR	cr2	OR	cr2
AND NOT	cr3	AND NOT	cr3
OUT	CR2	OUT	CR2
AND	x5	AND	x5
OR	cr3	OR	cr3
AND NOT	cr4	AND NOT	cr4
OUT	CR3	OUT	CR3
AND	x6	AND	x6
OR	cr4	OR	cr4
STORE NOT	x3	STORE NOT	x3
OR NOT	x5	OR NOT	x5
AND	STORE	AND	STORE
OUT	CR4	OUT	CR4
STORE	cr1	STORE	cr1
OUT	Y1	OUT	Y1
STORE	cr2	STORE	cr2
OUT	Y2	OUT	Y2
STORE	cr1	STORE	cr1
OUT	Y3	OUT	Y3
STORE	cr4	STORE	cr4
OUT	Y4	OUT	Y4
STORE	cr1	STORE	cr1
AND	x2	AND	x2
AND	x4	AND	x4
OR	cr3	OR	cr3
OUT	Y5	OUT	Y5
STORE	cr2	STORE	cr2
AND	x1	AND	x1
OR	cr4	OR	cr4
OUT	Y6	OUT	Y6

e. PLC Program

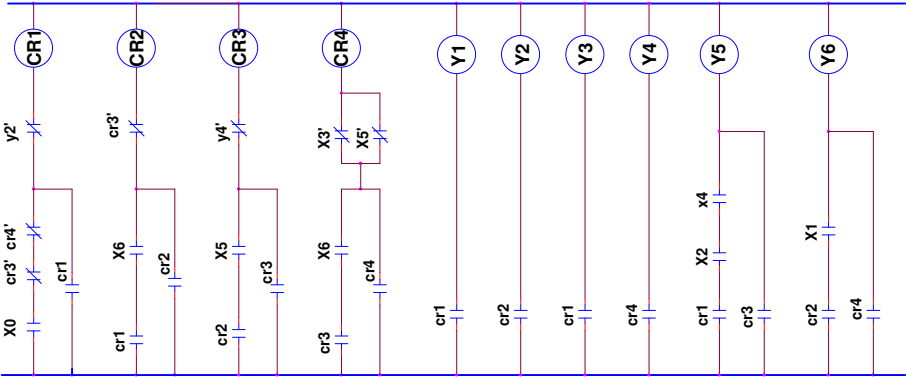


d. PLC Cascade Circuit

 

START	x0
a1	x1
a2	x2
b1	x3
b2	x4
c1	x5
c2	x6
A+	Y1
A-	Y2
B+	Y3
B-	Y4
C+	Y5
C-	Y6

c. PLC Variables Assignment

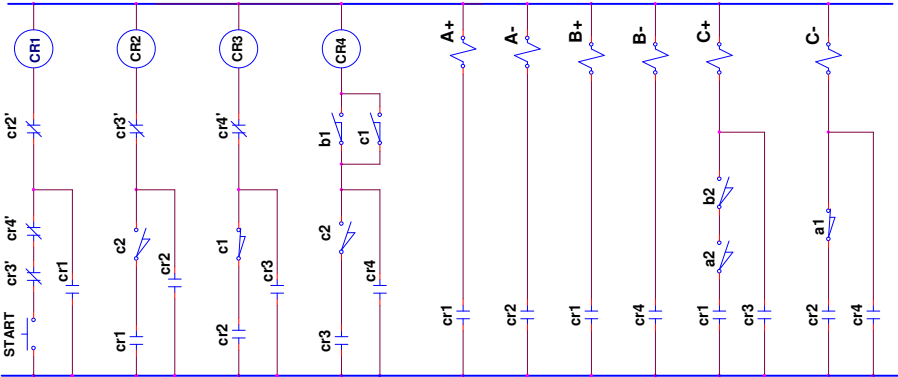

b. Relays Cascade Circuit

Fig. 3-16 : PLC Cascade System Design

 


Fig. 3-17 : PLC Simplified Cascade of Fig. 3-16

3-9

1. Read & store status of all external inputs (Xi)
2. Run program commands in its written order
3. Wait until end of scan time (*)
4. Return to (1) and start new cycle

1. Input variables (Xi) status cannot be changed by program commands, and remains unchanged until next cycle

2. Output variables (Yi) and internal variables (CRi) status are controlled by PLC program. They are updated once during each cycle

3. Program commands refer to latest update of the variables.


a. PLC Scan Cycle Order

b. Variables Status During Scan Cycle


I/O Update at Beginning of Scan	Variables States	
	This Scan	Next Scan
y7	Y7=0 , CR2=0	Y7=1 , CR2=1
cr4	CR4=0 , CR6=0	CR4=1 , CR6=1
x4	X4=1 , Y7=1	
x4	X4=1 , CR4=1	
y7	Y7=1 , CR5=1	
cr6	CR6=0 , Y8=0	CR6=1 , Y8=1

c. Effect of Scanning Action on Relay States

Fig. 3-18 : Effect of Scanning Action in PLC

 



a. Proper Rung Order

 



b. Improper Rung Order

Fig. 3-19: Importance of Proper Rung Order (Pulse Shaper)

3-10

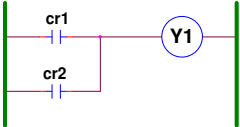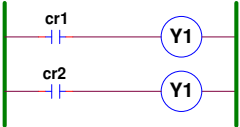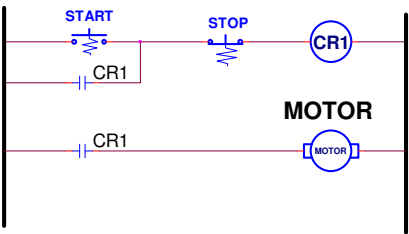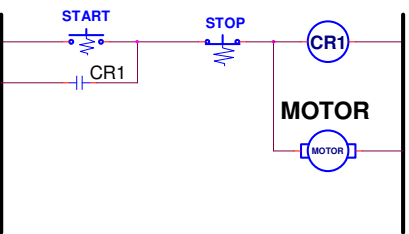RIGHT	WRONG	
		SCHEMATIC DRAWING
<pre> STORE cr1 OR cr2 OUT Y1 </pre>	<pre> STORE cr1 OUT Y1 STORE cr2 OUT Y1 </pre>	PLC PROGRAM
<p>CR1=1 CR2=0</p> <div> <pre> STORE cr1 1 OR cr2 1+0=1 OUT Y1 Y=1 </pre> </div>	<p>CR1=1 CR2=0</p> <div> <pre> STORE cr1 1 OUT Y1 Y=1 STORE cr2 0 OUT Y1 Y=0 </pre> </div>	SPECIFIC CASE
<div> <pre> STORE cr1 1 OR cr2 1+0=1 OUT Y1 Y=1 </pre> </div>	<div> <pre> STORE cr1 1 OUT Y1 Y=1 STORE cr2 0 OUT Y1 Y=0 </pre> </div>	PROGRAM FLOW
Y=1	Y=0	END-LOOP RESULT


a. NEVER SPLIT OUTPUT FUNCTION INTO 2 (OR MORE) OUTPUT SUB-FUNCTIONS

RIGHT	WRONG
	
<p>Motor current flows through separate contact, thus isolated from input sensors</p>	<p>Motor current flows through sensors)</p>

b. LOAD MUST BE ISOLATED FROM SENSORS

Fig. 3-20 : Right/Wrong Cases

3-11

 


STORE	X1
STORE	X2
STORE	X3
AND	X4
OR	STORE
AND	STORE
OUT	CR1
STORE	cr1
AND	X2

STORE	X3
AND	X4
OR	X2
AND	X1
OUT	CR1
STORE	cr1
AND	X2

a. Original Circuit

b. Programmable Simplified Circuit

 

c. Ladder Sub-Circuit

STORE	X3
AND	X4
OR	X2
AND	X1
OUT	CR1
STORE	cr1
AND	X2

d. PLC Program

STORE	X3
AND	X4
OR	X2
AND	X1
OUT	CR1
AND	X2

e. Simplified Program

Fig. 3-21 : PLC Program Simplification

TIMERS AND COUNTERS


The following implement PLC timers and counters of two companies :

General Electrinc (GE)

Texas Instruments (TI)

Note : Examples refer to specific PLCs. Actually there exist a lot of different timers and counters.

Fig. 3-22 : PLC Timer And Counter Models

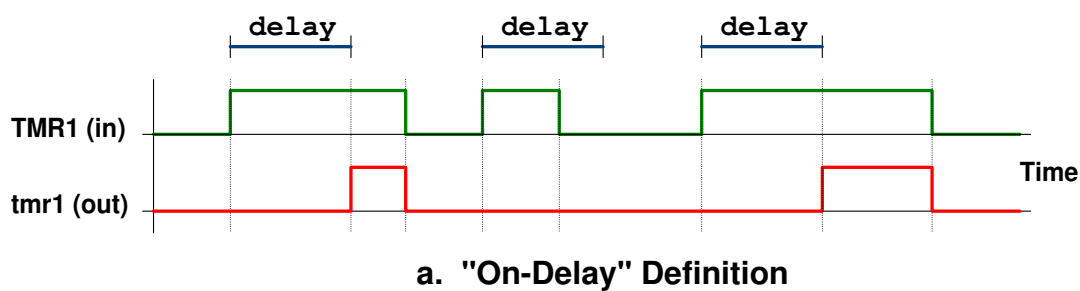

X1=1 Timer Enabled and counting time

X1=0 Timer is Reset

b. Specific Case

c. General Case


Fig. 3-23 : PLC "On-Delay" Timer Model (GE)

3-13




 a. Flash Block Diagram


Flash light is actuated while switch is on



b. Flash Timing Diagram

 

c. PLC Ladder Diagram

 

d. Detailed Timing Diagram

Fig. 3-24 : Design Flash-Light system using "On-Delay" time

 


Fig. 3-25 : 2-Input PLC Timer (TI - Texas Instruments)

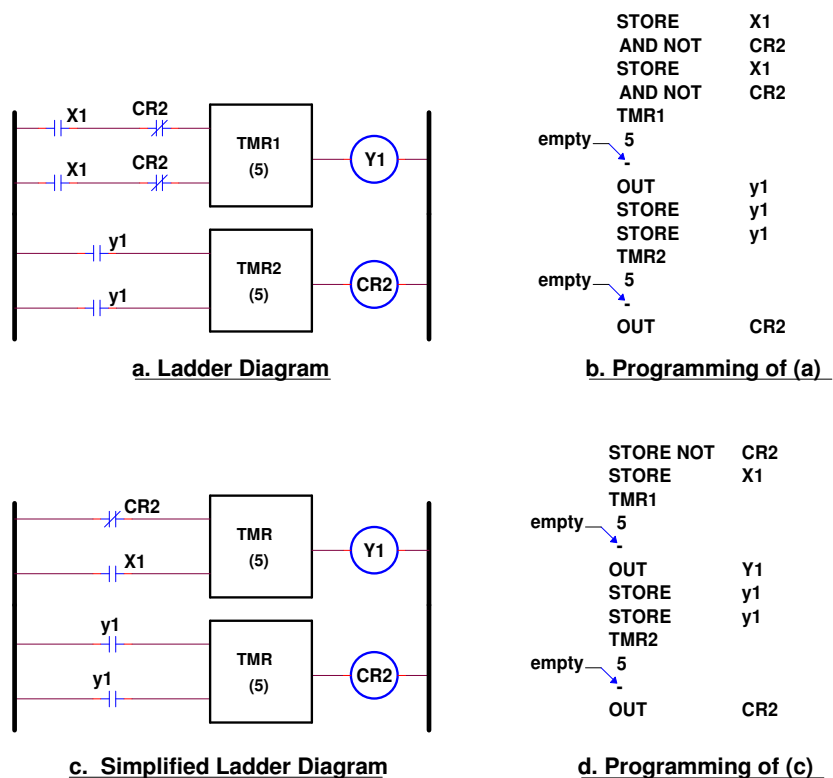


Fig. 3-26 : Design Flash-Light system using TI timers

A security lock is to be opened only on confirmation of two managers, simultaneously. Each manager confirms by turning on a personal switch (A and B).

In order to make sure that a single manager will not be able to turn on both switches, the switches been located far from each other, and lock is to be opened only if the two switches are turned on within 0.5 Sec.

If one switch is turned on at least 0.5 Sec before second switch is turned on, the security lock is disabled, and may later be open after releasing the pressed switch and repeat the process.

After being opened, the lock is closed as soon as any of the switches is turned off.

a. Security Lock Specifications


Switch A	X1
Switch B	X2
Lock	Y1

b. PLC I/O table




Y=1 when both switches are operated
Missing timing dependence

c. Solution Step 1

 

Y=1 when both switches are operated, and
timer output tmr1 is off
Missing timer actuation


d. Solution Step 2

 

Timer is actuated by either of the two
switches. If timeout occurs before
second switch been turned, lock is
disabled

Timer output always is set to "1" after
0.5 Sec. This disables lock even if it
had been opened correctly.

e. Solution Step 3

 


If Y1 been set to "1", it keeps be
connected by by-passing cr1 contact
(acts as flip-flop).

f. Solution Step 3 - Complete Solution

Fig. 3-27 : Two-Hands Circuit Using PLC

3-16

 


STORE X1
STORE X2
CTR1
25
OUT CR1

empty

c. Programming of (a)

Fig. 3-28 : PLC Two-Input UP Counter (TI)

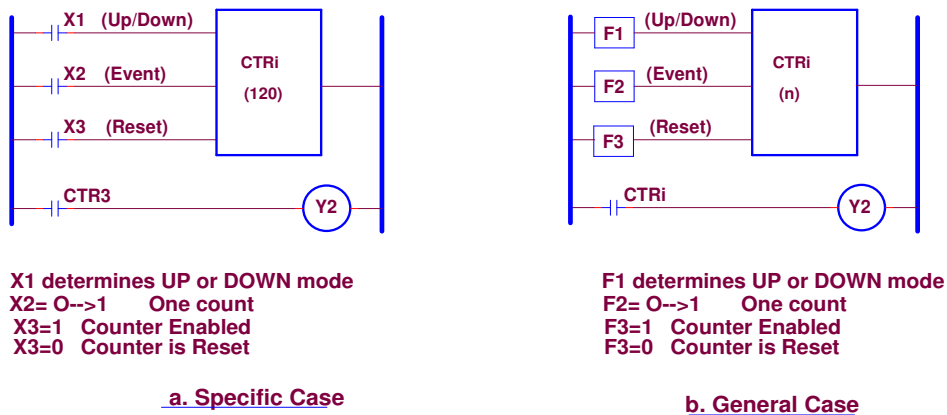

LOAD NOT X1
LOAD NOT X2
LOAD NOT X3
OUT CTR3
120
LOAD CTR3
OUT Y1


c. Programming of (a)

Fig. 3-29 : 3-Input UP/DOWN Counter (GE)

3-17

START,(D+,D-) repeat 6 times,D+,10 Sec DELAY,D-


a. Required Sequence

 


Input Modules	Output Modules	Connected to
X0		START
X1		d1
X2		d2
	Y1	D+
	Y2	D-

b. Cylinder Type

c. PLC I/O Table

 


d. Solution Step 1

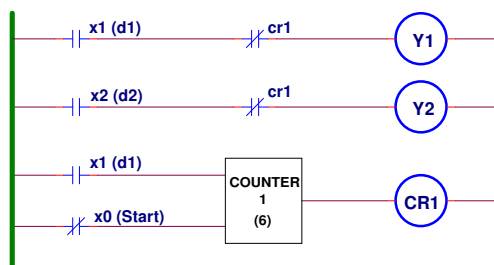

Circuit performs 6+1/2 Cycles, and stops

e. Solution Step 2

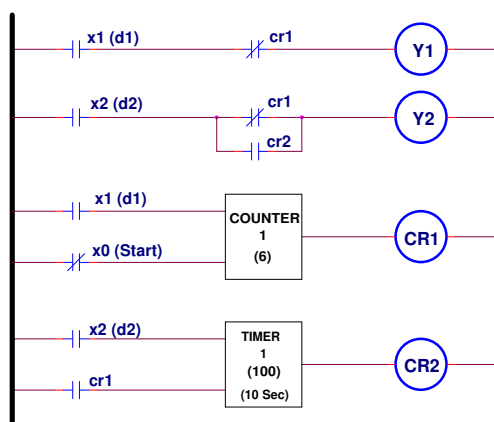

f. Solution Step 3 - Complete Circuit

```

STORE      x1
AND NOT    cr1
OUT         Y1

STORE NOT   cr1
OR          cr2
AND         x2
OUT         Y2

STORE      x1
STORE NOT   x0
CTR1
6
(NOT USED)
OUT         CR1
STORE NOT   x2
STORE      cr6
TMR1
100
(NOT USED)
OUT         CR2
    
```

g. PLC Programm

Fig. 3-30 : Step-By-Step Design of Sequence
START,(D+,D-) repeat 6 times,D+,10 Sec DELAY,D-


3-18

An elevator exists in a 5-floor building.


Elevator runs automatically (without human control), from 1st floor to 5th floor, and vica versa, while stopping for 10 seconds in each floor.

Each floor is equipped WITH a unique contact, that is closed when the elevator reaches that floor. These contacts are implemented as input sensores for PLC control system.

a. System Description

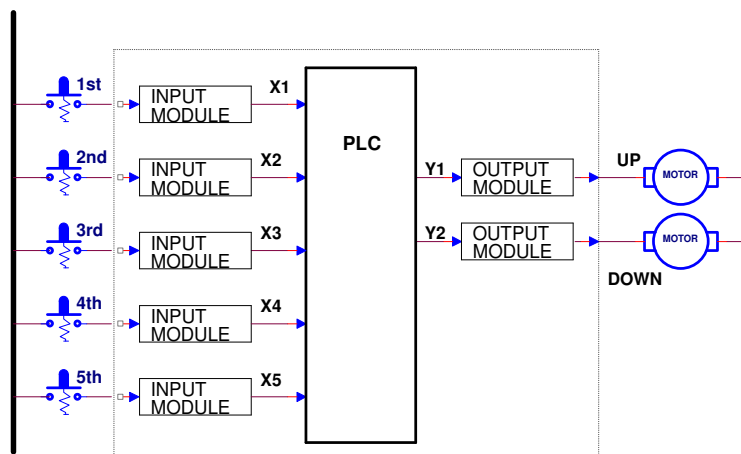

b. PLC System Configuration

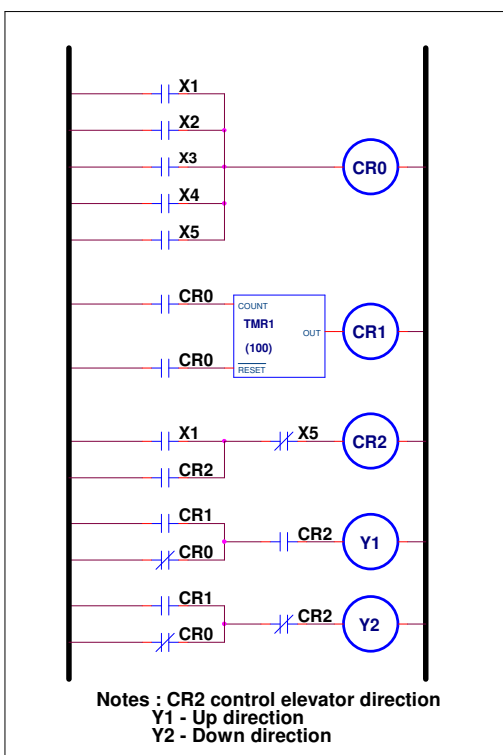

c. PLC Ladder Diagram

STORE	X1
OR	X2
OR	X3
OR	X4
OR	X5
OUT	CR0
AND	CR0
TMR1	
100	
(NOT USED)	
OUT	CR1
STORE	X1
OR	CR2
AND NOT	X5
OUT	CR2
STORE	CR1
OR NOT	CR0
AND	CR2
OUT	Y1
STORE	CR1
OR NOT	CR0
AND NOT	CR2
OUT	Y2

d. PLC Program

Fig. 3-31 : "Saturday" Elevator

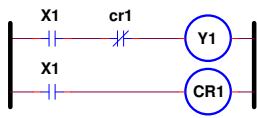
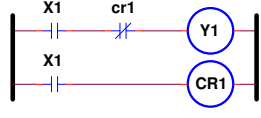
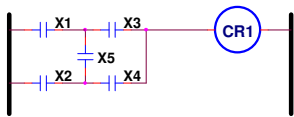
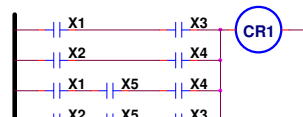
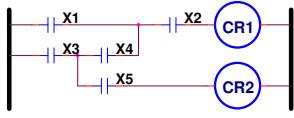
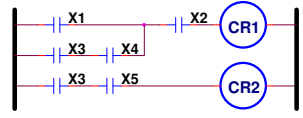
Property	Relays System	PLC System
a. Signal Flow	Parallel	Serial
b. Number of Contacts	Limited	Unlimited
c. Adding Relay	Expensive	NO cost
d. Timers / Counters	Expensive	NO cost
e. Reliability	Limited	Almost unlimited
f. Support	Required	Almost not required
g. Races	 <p>Possible</p>	 <p>Impossible</p>
h. Non Serial Parallel	 <p>Possible</p> <p>$(CR1 = X1.X3 + X2.X4 + X1.X5.X4 + X2.X5.X3)$</p>	 <p>Impossible</p>
i. Sneak Path	 <p>Possible</p> <p>$CR1 = X1.X2 + X3.X4.X2$ $CR2 = X3.X5 + X1.X4.X5$</p>	 <p>Impossible</p> <p>$CR1 = X1.X2 + X3.X4.X2$ $CR2 = X3.X5$</p>

Fig. 3-32 :Differences Between Relay and PLC Ladder Diagram

Byte/Word format (binary groups)
Digital to/from Binary
Mathematical Operations
Matrix Operations
Digital/Analog conversion
More

Fig. 3-33 : Support Other Data Types

 


Fig. 3-34 : Master Control Relay (MCR) Command

 


Fig. 3-35: Jump (JMP) Command

ENHANCED LADDER DIAGRAM INSTRUCTIONS

Enhanced ladder diagram instructions are handled very differently in different PLC models. Therefore, only a few typical examples are shown here.

LATCH (UNLATCH)
GOTO
ADD
SUBTRACT
MULTIPLICATION
DIVISION
SQUARE ROOT
COMPARE

Fig. 3-36 : Arithmetic Instruction

 


Fig. 3-37 : Typical "ADD" Instruction Block

 


Fig. 3-38 : Typical "COMPARE" Instruction Block

AND
OR
XOR
NAND
NOR
NOT

Fig. 3-39 : Logic Operations
(or corresponding bits of two specified registers)

These change the contents of a specified register.

Typical Conversions :
BCD to Binary
Binary to BCD
Absolute Value
Complement (multiplied by -1)
Invert (inverts all bits)

3-40 Data Conversion Instructions

Logical Shifts : Moves all bits of a register to right or left
Data Transfer Instructions :
There are many such instructions, used to move data within the PLC

Fig. 3-41 : Data Commands

MICRO-AUTOMATION versus MACRO-AUTOMATION

Micro-Automation : Automation of a single machine, or a small group of machines, also called an "Automation Island".

Macro-Automation : Automation of a large plant, consisting of many individual automation islands. Uses a large computer or a large PLC, that coordinates the operation of the individual automation islands. Each automation island is usually controlled by its own control system, such as a small or medium-scale PLC ("Distributed Control").


Macro-automation makes use of a LAN (Local-Area-Network), which links the various stations or automation islands with the central supervising computer or PLC. The use of a LAN provides :

1. Distributed Control
2. Centralized Data Acquisition

The LAN can be organized according to any one of a several possible LAN Topologies (arrangements), such as "Common Bus", "Star" or "Ring".

THIS COURSE REFERS TO MICRO-AUTOMATIC ONLY


Fig. 3-42 : PLC Micro/Macro Systems Definition

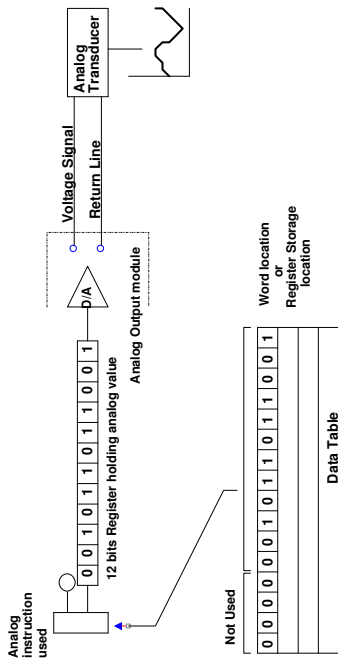

d. Transferring a Word to Analog Output Module

ANALOG OUTPUT	
Rack	4
Slot	05
Number of channels	4
Source register	300
(Octal code 300 = 192)	

 e. Typical "Analog Out" Instruction Block




f. Typical "PID Controller" Instruction Block

In some PLC's, the PID Controller is implemented by a special output module, i.e. by hardware. In others, it is programmed using a special Instruction Block, such as shown here.

- 4 - 20 mA
- 10 - 50 mA
- 0 - 5 volt DC
- 0 - 10 volt DC
- +/- 5 volt DC
- +/- 10 volt DC
- PID Controller

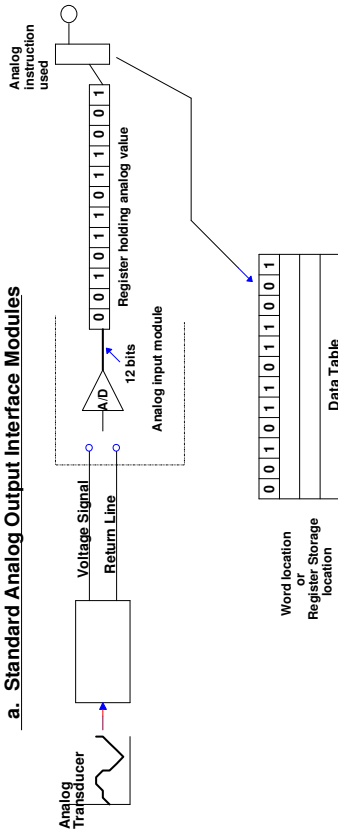a. Standard Analog Output Interface Modules



Since A/D converters are expensive, they are often shared by several 4 to 8 channels. One channel is read and stored on every scan.

b. Storing an Analog Input

ANALOG IN	
Rack	0
Slot	03
Number of channels	8
Destination register	200
(Octal code 200 = 128)	

(Since there are 8 channels, the 8 slots would be assigned the Destination Register 200 to 207)

c.. Typical "analog In" block Instruction


Fig. 43 : Support Analog Data

CHAPTER 4


INDUSTRIAL SWITCHING ELEMENTS

Electronic Gates
Gates Implementation
Input/Output Module
Electric Relays
Pneumatic Valve “Gates”
Moving Parts Logic (MPL)
Design Considerations
Switching Elements Properties


4-1

 


a. Quad 2-Input NAND Gate

 


b. Quad 2-Input OR Gate

 


c. Tripple 3-Input NAND Gate

 


d. Dual 4-Input NAND Gate

 


e. Hex INVERTER

 

f. Dual J-K FLIP-FLOP

 

g. Chip Configuration

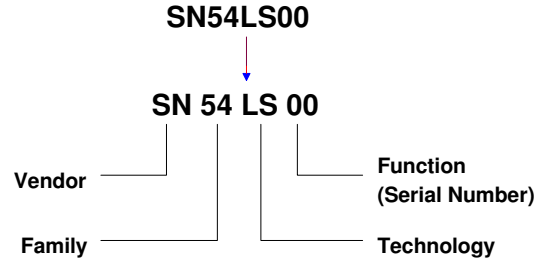

h. Chip Name "Code"

74 : Commercial Family

54 : Military Family

Difference : Temperature Range

Many More Families

i. Families

High / Low Speed


High / Low Power Dissipation

High / Low Power Drive (Fan-Out)

High / Low Power Supply Voltage

And Many More

j. Technologies Characteristics

 

k. Grid-Array Package
(not SSI)

Fig. 4-1 : Typical Simple Gates Packages (SSI - Small Scale Integrated)

4-2

 


Fig. 4-2 : Equivalent Circuits for Function $AB+CD+EF$

 


Fig.4- 3 : Equivalent Circuits for Function $AB+A'C$ (Save Packages)

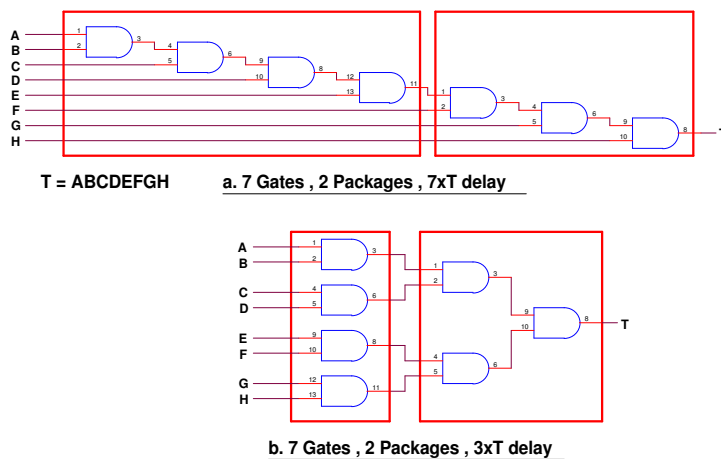


Fig. 4-4 : Equivalent Circuits for Function $ABCDEFGH$

(Increase Speed)

 


Fig. 4-6 : Switch Bounce Elimination

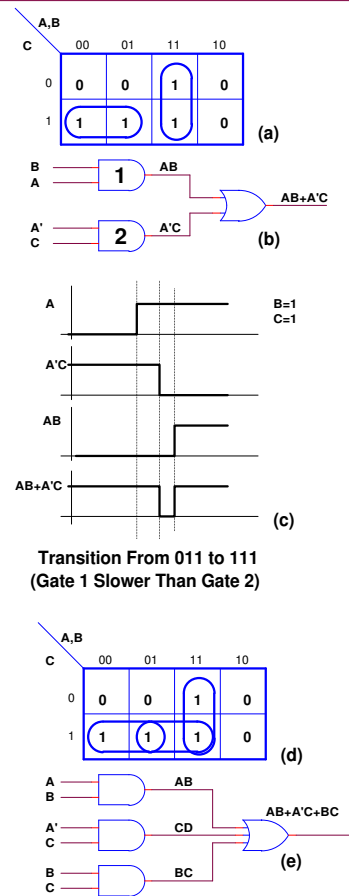


Fig. 4-5 : Hazard Elimination

4-3



 



Fig. 4-7 : Typical Opto-Isolated Input Module

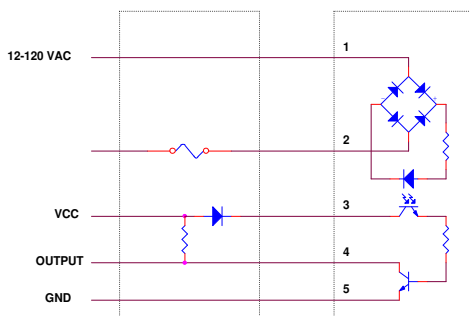


a. AC Input Module (IAC)

 

DC Input Module (IDC)

 

b. AC Output Module (IAC)

 

DC Output Module (IDC)

Fig. 4-8 : AC Input and Output Modules for Electronic Gates

Fig. 4-9 : DC Input and Output Modules for Electronic Gates

 


Fig. 4-10 : Relay Construction

 


Fig. 4-11 : Typical Relay Package



 


Fig. 4-12 : Typical Relay Contacts


4-4

 


a. YES Gate

 


b. NOT Gate

 


c. AND Gate

 


d. OR Gate

 


e. INHIBITION Gate

 


f. IMPLICATION Gate

 


g. SELECTOR Gate

 


h. YES/NOT Gate

 


i. AND/OR Gate

 


j. INHIBITION/IMPLICATION Gate

 

k. Non-Valve "OR" Element

 

 l. Almost equal HOT/COLD pressure - No Flow



m. COLD Pressure Less Than HOT - HOT Flows Into COLD

Fig. 4-13: Pneumatic Valve Gates

 
 


Fig. 4-14 : Operation of 5/2 Spool Valve

 


Fig. 4-16 : Pneumatic Universal Gate (MPL)
(Samsomatic, W. Germany)

 


Fig. 4-17 : Pneumatic Universal Gate (MPL)
(Dreloea, E. Germany)

 


Fig. 4-15 : Shuttle Valve
(OR Gate)

 


Fig. 4-18 : Pneumatic OR Gates

 


Fig. 4-19 : Pneumatic AND Gate

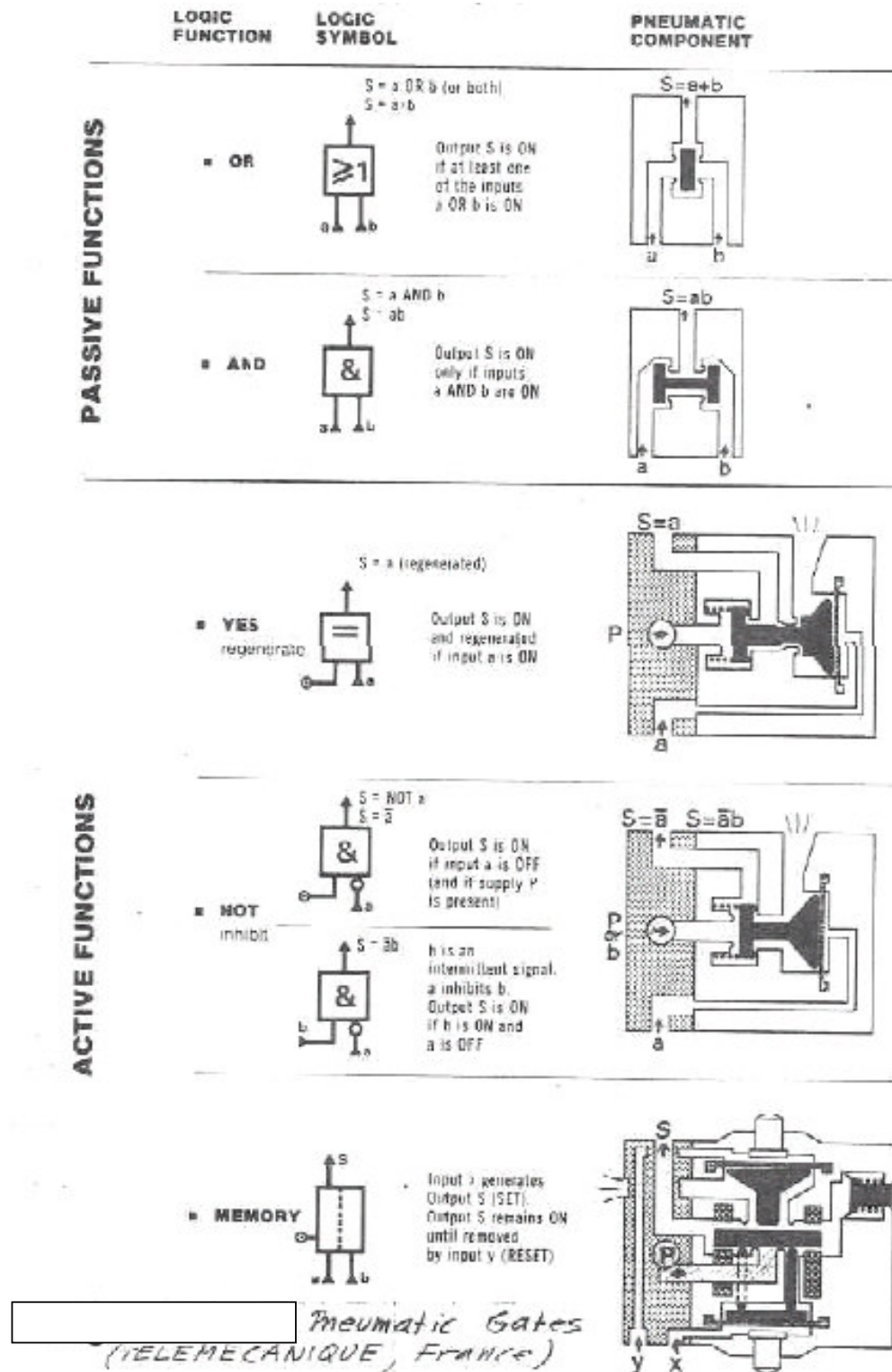


Fig. 4-20 : Pneumatic Gates (TELEMECHANIQUE, France)

 


Fig. 4-21 : Fluid Flip-Flop (Wall Attachment Principle)

 


Fig. 4-22 : Fluid OR-NOR Gate $Q1 = C1 + C3$, $Q1 = (C1 + C3)'$

 


Fig. 4-23 : Fluid NOR Gate (Impact Modulator, AIR Logic, USA)
 $T = (C1 + C2 + C3 + C4)'$

 


Fig. 4.33. On and Off states of a diaphragm amplifier. (Courtesy of Air Logic Div., Fred Knapp Eng. Co.)

Fig. 4-24 : Pneumatic Binary Amplifier (Single Stage, AIR LOGIC, USA)

 


Fig. 4-25 : Pneumatic Binary Amplifier (Two Stage, CLIPPARD, USA)



Fig. 4-26 : Comparison Between Switching Methods

Fluidies	Moving-Part Logic	Pneumatic Valves	Relays	Electronics	
1-2 mSec	5-10 mSec	10-20 mSec	10-25 mSec	5-10 mSec	זמן תגובה
בינוני	בינוני	גדול	גדול	קטן	גודל יחסית של המערכת
בלתי מוגבל	10E7-10E8 מחזוריים	10E7-10E8 מחזוריים	10E5-10E6 מחזוריים	בלתי מוגבל	אמינות (משך חיים)
עם אוויר נקי				בתנאים מתאימים	
טוב מאוד	טוב	טוב	בינוני	גרוע	הגישות לטמפרטורה
גרוע	טוב	טוב	בינוני	בינוני	הגישות לכלוך וקורוזיה
טוב מאוד	בינוני	טוב מאוד	גרוע	בינוני	הגישות להתנודות והלם
טוב מאוד	טוב מאוד	טוב מאוד	טוב	גרוע	הגישות לרעש חשמלי
					וקרינה
טוב מאוד	טוב מאוד	טוב מאוד	גרוע	בינוני	סכנה עם חומר מתלקח
2-4	2-3	2	>20	2-8	Fan-In
4-6	בלתי מוגבל	בלתי מוגבל	>20	5-10	Fan-Out
נמוך	בינוני - גבוה	גבוה	-	-	לחץ אוויר
גבוהה	נמוכה	נמוכה	-	-	תצרוכת אוויר
	פניאומטיים	טוב לחישינים	חשמליים	טוב לחישינים	Input Interface
זורש הגברה	פניאומטי	טוב לצידוד	חשמלי	טוב לצידוד	Output Interface

Fig. 4-27 : Comparison Between Switching Elements

CHAPTER 5

HUFFMAN METODE

Feedback Memory Concept
Typical Block Diagram
Primitive Flow Diagram
Primitive Flow Table
Merge diagram
Merged Flow Table
States Assignment
Excitation and Output Functions
Ladder Circuit Realization
PLC Program
Random Inputs Systems

Huffman/PLC Combination

5-1

Huffman method is very effective in reducing the number of group relay flip-flops. It is also effective for design of systems with random inputs.

Design process by Huffman method may become very complex, from "State Assignment" step, and on. Furthermore, it is based on Karnaugh maps, which eliminate the number of involved variables.

When system realization is based on PLC or on electronic gates, number of "relay" flip-flops doesn't actually effect system cost (or effect is minor)


The Huffman-PLC method :

- * implements flip-flop for each state
- * eliminates the complexity of Huffman method,
- * enables to implement large Karnaugh maps and Pseudo Karnaugh maps.

Fig. 5-1 : Huffman Method - Basic

 
Example - A system detects cylinder piston movement direction : forward (toward A+ position), or backwards (toward A- position).

System reads limit switches a1 and a2 and outputs signals to green or red bulbs. During forward movement (input=00), green bulb must be illuminated, and during backwards movement (same input) red bulb must be illuminated,




Note : Assume that piston changes direction only after reaching cylinder edge.


a. System Definition

 

 
b. Same Input Generates Different Outputs (Impossible in a combinational system)



 
c. Adding External State Input (y) May Eliminate Problem



d. Internal Generated State Signal

 

e. Sequential System General Diagram

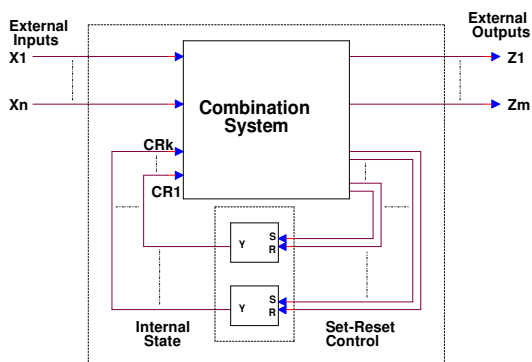

f. Multiple Internal Generated State Signals

Fig. 5-2 : Sequential System Concepts


RESTRICTION : DUE TO TRANSIENT HAZARDS, ASYNCHRONOUS SYSTEM CANNOT HANDLE CHANGE OF SEVERAL INPUT SIGNALS SIMULTANEOUSLY (EXCEPT FOR SPECIFIC CASES).

Change of an external input may cause a change of state variable, which is fed to system input. Result may cause simultaneous change of two input signals (external and internal).


In order to avoid it, simultaneous changes are replaced by sequential changes. This result is achieved due to memory (flip-flop) delay.

a. Essential Restriction Rule


b. Hazard Problem and Its Elimination

 

c. Circuit Example

 

e. Transition Timing

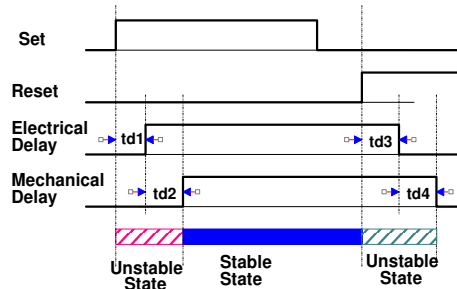

Each transition from state to state is combined of unstable state followed - after delay- by stable state.

d. Relay Flip-Flop Transition Response


Fig. 5-3 : States Transition Process

- | | |
|---|--|
| Step 1 : System requirements definition | Step 7 : States assignment |
| Step 2 : Primitive flow diagram | Step 8 : Output table |
| Step 3 : Primitive flow table | Step 9 : Flip-flops excitation expressions |
| Step 4 : Merge options Diagram | Step 10 : Outputs expressions |
| Step 5 : Merge groups selection | Step 11 : System Logic Circuit |
| Step 6 : Merged flow table | |

Fig. 5-4 : Huffman Design Steps

When input changes from "0" to "1", output is delayed T sec
When input changes from "1" to "0", output is changed immediately, and time count is reset

a. Definition

 

b. Example of Timing Diagram (5 Sec Delay)

Fig. 5-5 : "On-Delay" Timer


HUFFMAN DESIGN METHOD

5-3


START, A+, A-, A+, A-

With Return Spring


a. Sequence

 

b. Sequence Chart

 


c. Cylinder Type

 

d. Basic Block Diagram

State	Cylinder State	Action	Output Command
1	Cylinder at A- (Start)	Start moving towards A+	A+
2	Moving towards position +	Keep moving towards A+	A+
3	Cylinder at A+	Start moving back (towards A-)	None (A-)
4	Cylinder moves towards A-	Keep moving back	None (A-)
5	Cylinder at A-	Start moving towards A+	A+
6	Cylinder moves towards A+	Keep moving towards A+	A+
7	Cylinder at A+	Start moving back (towards A-)	None (A-)
8	Cylinder moves towards A-	Keep moving back	None (A-)


e. States Definitions

 

f. Primitive Flow-diagram

a1,a2	10	00	01	11
1	2	-	-	-
2	3	-	-	-
3	4	-	-	-
4	5	-	-	-
5	6	-	-	-
6	7	-	-	-
7	8	-	-	-
8	1	-	-	-

g. Primitive Flow-table

 

h. Merge Diagram

(refer to 5-5 for Merging rules)

a1,a2	10	00	01	11
1	2	-	-	-
2	3	-	-	-
3	4	-	-	-
4	5	-	-	-
5	6	-	-	-
6	7	-	-	-
7	8	-	-	-
8	1	-	-	-

j. Merged Flow-table

{1,2}, {3,4}, {5,6}, {7,8}

i. Selected Groups

a1,a2	10	00	01	11
cr1	1	2	3	-
cr2	5	4	3	-
cr3	5	6	7	-
cr4	1	6	7	-

k. States Assignment


a1,a2	10	00	01	11
cr1	1	1	-	-
cr2	-	0	0	-
cr3	1	1	-	-
cr4	-	0	0	-

l. Output Table

$$\begin{aligned}
 S1 &= cr4.a1 & R1 &= cr2.a2 & R1' &= cr2' + a2' \\
 S2 &= cr1.a2 & R2 &= cr3.a1 & R2' &= cr3' + a1' \\
 S3 &= cr2.a1 & R3 &= cr4.a2 & R3' &= cr4' + a2' \\
 S4 &= cr3.a2 & R4 &= cr1.a1 & R4' &= cr1' + a1' \\
 S1 &= a1(cr2+cr3)' = a1.cr2'.cr3' & & & & \\
 A+ &= cr1 + cr3 & & & & \\
 A- &= START.cr1.a1 + cr1.a1' + cr3 & & & &
 \end{aligned}$$

m. Exitation and Output Functions

 (refer to 5-5 for Initialization and Output Rules)




n. Relays Ladder Diagram

INPUTS	
Start	X0
Limit contact a1	X1
Limit contact a2	X2

OUTPUTS	
Solenoid A+	Y1

o. PLC I/O Tables

 

p. Relays Ladder Diagram

STORE	x1
AND NOT	cr2
AND NOT	cr3
OR	cr1
STORE NOT	cr2
OR NOT	x2
AND	STORE
OUT	CR1
AND	x2
OR	cr2
STORE NOT	cr3
OR NOT	x1
AND	STORE
OUT	CR2
AND	x1
OR	cr3
STORE NOT	cr4
OR NOT	x2
AND	STORE
OUT	CR3
AND	x2
OR	cr4
STORE NOT	cr1
OR NOT	x1
AND	STORE
OUT	CR4
STORE	x0
AND	cr1
AND	x1
STORE	cr1
AND NOT	x1
OR	STORE
OUT	cr3
Y1	

q. PLC Circuit & Program


Fig. 5-6 : Sequence A+,A-,A+,A-, Huffman Method
(With Returned Springs)

HUFFMAN DESIGN METHOD


START , A+ , A- , A+ , A-

Without Return Spring


a. Sequence

 

b. Sequence Chart

 


c. Cylinder Type

 


d. Basic Block Diagram

State	Cylinder State	Action	Output Commands	
			A+	A-
1	Position - (initial)	Start moving towards A+	1	0
2	Moving towards position +	No action required	-	0
3	A+	Start moving back (towards A-)	0	1
4	Cylinder moves towards A-	No action required	0	-
5	Cylinder at A-	Start moving towards A+	1	0
6	Cylinder moves towards A+	No action required	-	0
7	Cylinder at A+	Start moving back (towards A-)	0	1
8	Cylinder moves towards A-	No action required	0	-

e. States Definitions

 

f. Primitive Flow-diagram

 

h. Merge Diagram

(See page 5-9 for Merging rules)

i. Selected Groups

{1;2} , {3;4} , {5;6} , {7;8}

a1,a2	10	00	01	11	A+	A-
cr1	1	2	-	-	1	0
cr2	-	2	3	-	-	0
cr3	-	4	3	-	0	1
cr4	5	4	-	-	0	-
cr5	6	-	-	-	1	0
cr6	-	6	7	-	-	0
cr7	-	8	7	-	0	1
cr8	1	8	-	-	0	-

g. Primitive Flow-table

a1,a2	10	00	01	11
cr1	1	2	3	-
cr2	5	4	3	-
cr3	6	7	-	-
cr4	1	8	7	-

j. Merged Flow-table

a1,a2	10	00	01	11
cr1	1	2	3	-
cr2	5	4	3	-
cr3	6	7	-	-
cr4	1	8	7	-

k. States Assignment


a1,a2	10	00	01	11
cr1	1	-	-	-
cr2	-	0	0	-
cr3	1	-	-	-
cr4	-	0	0	-

l. Output Tables

$$\begin{aligned}
 S1 &= cr4.a1 & R1 &= cr2.a2 & R1' &= cr2' + a2' \\
 S2 &= cr1.a2 & R2 &= cr3.a1 & R2' &= cr3' + a1' \\
 S3 &= cr2.a1 & R3 &= cr4.a2 & R3' &= cr4' + a2' \\
 S4 &= cr3.a2 & R4 &= cr1.a1 & R4' &= cr1' + a1' \\
 S1 &= a1(cr2+cr3)' = a1.cr2'.cr3' \\
 A+ &= cr1 + cr3 \\
 A+ &= START.cr1 + cr3 \\
 A- &= a2
 \end{aligned}$$

m. Exitation and Output Functions

 (refer to 5-5 for Initialization and Output Rules)



n. Relays Ladder Diagram


INPUTS

Start	X0
Limit contact a1	X1
Limit contact a2	X2

OUTPUTS

Solenoid A+	Y1
Solenoid A-	Y2

o. PLC I/O Tables

 

p. PLC Ladder Diagram

STORE	x1
AND NOT	cr2
AND NOT	cr3
OR	cr1
STORE NOT	cr2
OR NOT	x2
AND	STORE
OUT	CR1
AND	x2
OR	cr2
STORE NOT	cr3
OR NOT	x1
AND	STORE
OUT	CR2
AND	x1
OR	cr3
STORE NOT	cr4
OR NOT	x2
AND	STORE
OUT	CR3
AND	x2
OR	cr4
STORE NOT	cr1
AND	STORE
OUT	CR4
STORE	x0
AND	cr1
OR	cr3
OUT	Y1
STORE	x2
OUT	Y2

q. PLC Circuit & Program

Fig. 5-7 : Sequence A+,A-,A+,A- , Huffman Method
(Without Returned Springs)

 


Fig. 5-8: Merge Flow Rows Rules

Tran	Current State	Next State	Set	Reset
0 --> 1	0	1	1	0
1 --> 0	1	0	0	1
0 --> 0	0	0	0	-
1 --> 1	1	1	-	0

a. Flip-Flop Transition Cases

Fig. 5-9: FF Excitation Rules

On system reset (or power on), all state variables are "0", meaning :

$$CR1=CR2=CR3=...CRi=...=CRn = 0$$

This state is not part of the flow table, and and therefor is not taking care of. As a result, if we refere only to the flow table, we can't force the initial state CR to become "1".

Most (or all) set/reset functions are product of state-variable (or more), but since all of them are 0, all functions are inhibited.

Therefor, driving the system to its expected initial state, must be done by a function that doesn't depend on any operated CRi, but only on non-operated CRi' .

This is acheived by writing the initial function in its negative conditions, and negate it (similar to implementing the "0" Karnaught table).

So, instead of writing the CR states where the transition to that state must be carried on, we write the states where the transition is forbidden, as a function of CR or several CRs, and then negate it.

Negating this expression, using De-Morgan rules, bring to a function that depends on CRi, and this may be carried on.

System Initialization

In most cases, only steady-state output is specified.

But transition between steady states is done by pathing through a non-steady state : transients. If we don't take care of transition states, say define it as don't care, system output may be wrong during those transients.

Usually, transient time is very short with respect to steady states duration.

In some cases, we may ignore the need to define transitions output, usually when output inertion is high. For example, standard 220 valve is actuated by AC current, meaning that during each cycle its current is 0 twice, but it illuminates as required. This a simple case where due to high enersion, transient outputs do not affect the expected output.

Generally, if there is not enough information about the importance of transient outputs, the following rules are used :

Rule 1 : If outputs of 2 steady states are same, the output of the transition between them must be equal to the steady-state

Output: If outputs of 2 steady states are different from each other, the output of the transition between them may be defined as don't care.

Transient Outputs


 


Fig. 5-10 : States Grouping Examples


A mixing system requires filling a tank with liquid, mix it for a specific time period and then drain the liquid out.

An automatic process is represented as follows :

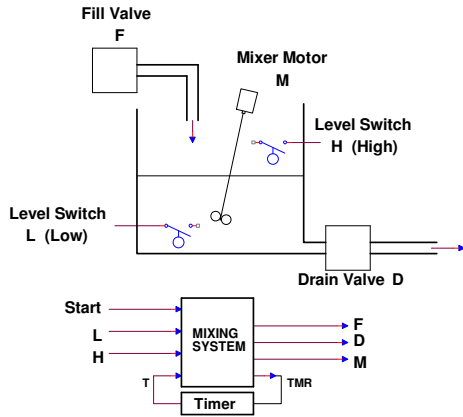
1. Sequence starts by pressing START button. This opens FILL valve.
2. Liquid fills tank until HIGH level sensor is operated.
3. At that time FILL valve is closed, mixing motor is turned on, and a timer is activated
4. On timeout, motor is turned off, and DRAIN valve is opened.
5. When tank is empty, LOW level sensor contacts open, and DRAIN valve is closed.



 
a. Process presentation and requirements definitions



b. Process Sequence

 

c. Groups Partition

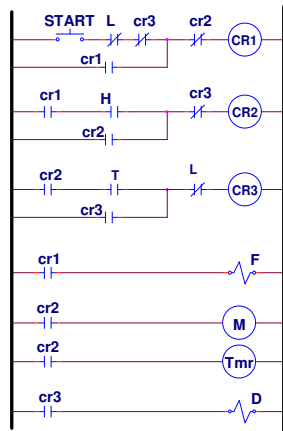

d. Cascade Contacts Circuit

Fig. 5-11 : Automatic Mixing System
Cascade Method


5-7

Process is same as defined at Fig. 6-25/a .

a. Process definitions

LHT	000	100	110	111	101	F	D	M	Ymr
1	2	-	-	-	-	1	0	0	0
-	2	3	-	-	-	1	0	0	0
-	-	3	4	-	-	0	0	1	1
-	-	-	4	5	-	0	1	-	1
-	6	-	-	5	-	0	1	0	0
1	6	-	-	-	-	0	1	0	0

b. Primitive Flow Table

 

c. Merge Diagram

{1, 2, 3}, {4, 5, 6}

e. Selected Groups Partition

- {1, 2, 3}, {4, 5, 6}
- {1, 2, 3, 4}, {5, 6}
- {1, 2}, {3, 4, 5, 6}

d. Minimized Groups Partition

LHT	000	100	110	111	101
CR	1	2	3	4	-
1	1	2	3	4	-
0	1	6	-	4	5

f. Merged Flow Table

LH	00	10	11	01
cr1,T	1	6	-	-
00	-	5	4	-
01	-	-	4	-
11	-	-	4	-
10	1	2	3	-

g. "Path" Map

LH	00	10	11	01
cr1,T	10	0-	-	-
00	-	0-	0-	-
01	-	-	01	-
11	-	-	01	-
10	-0	-0	-0	-

h. Exitation Map (SR)

LH	00	10	11	01
cr1,T	0	0	-	-
00	-	0	0	-
01	-	0	0	-
11	-	-	(0)	-
10	1	1	0	-

F

LH	00	10	11	01
cr1,T	0	1	-	-
00	-	1	1	-
01	-	1	1	-
11	-	-	-	-
10	0	0	0	-

D

LH	00	10	11	01
cr1,T	(0)	0	-	-
00	-	0	-	-
01	-	0	-	-
11	-	-	-	-
10	0	0	1	-

M

LH	00	10	11	01
cr1,T	(0)	0	-	-
00	-	0	-	-
01	-	0	1	-
11	-	-	(1)	-
10	0	0	1	-

TMR

i. Output Tables


S = L'.START F = H'.cr1 M = H
R = tmr D = L.cr1' TMR = H

j. System Functions

Fig. 5-12 : Automatic Mixing System
Huffman Method

5-8

 1. Different size elements are transferred on a conveyor belt.
2. All elements that are below specific height limit must be rejected.
3. Reject is performed by opening a reject door - $Z=1$.
4. Photocells X1 and X2 are placed in specific locations.
5. X2 is covered by all sizes. X1 is covered by elements over the defined specific height limit.




a. System Definition



b. System Block Diagram

- State 1 : Check area empty (00)
 State 2 : High element enters area (10)
 State 3 : High element in check area (11)
 State 4 : High element starts leaving area (01)
 State 5 : Low element in inside check area (01). Pushed out


c. States Definitions

 

d. Primitive Flow Diagram

X1,X2	00	10	11	01	Z
1	1	2	-	5	0
2	-	2	3	-	0
3	-	-	3	4	0
4	1	-	-	4	0
5	1	-	-	5	1

e. Primitive Flow Table

 

f. Merge Diagram

{1,2,5},{3,4}

{1,5},{2,3,4}

g. Merge Options

{1,5},{2,3,4}

h. Selected Options

X1,X2	00	10	11	01
1	1	2	-	5
2	1	2	3	4

i. Merged Flow Table

X1,X2	00	10	11	01
cr1	0	1	2	-
1	1	2	3	4

j. State Assignment

X1,X2	00	10	11	01
cr1	0	0	(0)	-
1	(0)	0	0	0

k. Output Table


$$\begin{aligned}
 S1 &= X1 & (S1 &= X1.X2') \\
 R1 &= X1'.X2' & (R1 &= X1'.X2'.cr1) \\
 Z &= X2.cr1' & (Z &= X1'.X2.cr1')
 \end{aligned}$$

l. System Functions

Fig. 5-13 : Height Detector System Design

5-9

 1. Different size elements are transferred on a conveyor belt.
2. All elements that are below specific height limit must be rejected.
3. Reject is performed by opening a reject door - Z=1.
4. Photocells X1 and X2 are placed in specific locations.
5. X2 is covered by all sizes. X1 is covered by elements over the defined specific height limit.



INPUTS

Photo-cell X1	X1
Photo-cell X2	X2

OUTPUTS

Cylinder Z	Y1
------------	----

d. PLC I/O List




$$\begin{aligned} S1 &= X1 & (S1 &= X1.X2') \\ R1 &= X1'.X2' & (R1 &= X1'.X2'.cr1) \\ Z &= X2.cr1' & (Z &= X1'.X2.cr1') \end{aligned}$$

a. Summary of Fig. 5-13

STORE	x1
OR	cr1
STORE	x1
OR	x2
AND	STORE
OUT	CR1


STORE NOT	cr1
AND	x2
OUT	Y1

e. PLC Program

 


 b. Relays Implementation

$$\begin{aligned} CR1 &= (X1 + cr1).(X1 + X2) = \\ &= X1.X1 + X1.X2 + cr1.X1 + cr1.X2 = \\ &= X1 + cr1.X2 \end{aligned}$$



c. Gates Implementation

 

f. cr1 Function Simplification


Fig. 5-14 : Realiation of Fig. 5-13

5-10


A red light signal is placed in the junction of road and railway. Its task is warning cars not to cross the junction. Another red light signal is placed far from the junction. Its task is warning other trains not to enter junction area. Train must operate red light as soon as it enters "junction path area", far from the junction, and turn it off as soon as last waggon leaves the junction, near junction.

Trains may go in two direction, but the following assumption are known :

 - * Only a single train crosses the junction path area, at a time.
- * Train doesn't changes direction within the junction path area.



 One of the tracks is connected to common node (Ground), while the other track is splitted - within the junction path area - into 3 sections, that are physically joined, but electrically isolated from the grounded track, and from tracks outside junction path area. Mid-section is also isolated from the other two, as seen in the drawing.




When the junction path area is empty (no trains inside) all 3 sections are disconnected from common track, thus providing "0" signal on each section.

When the train crosses a track section, it connects it electrically to the common track, thus changing its signal into "1". Signal returns to "0" as soon as last waggon leaves the appropriate track section.

Signaling control system senses A and B signals, and turns red lights on or off, accordingly.


a. System description

 

b. Basic Block Diagram

State	Position	AB	LW
1	Junction area empty	00	00
2	Train enters area	01	11
3	Train over central area	11	11
4	Train leaving central area	01	01
5	"Short" train on central area	10	11


c. States Definitions

 

d. Flow-diagram (primitive)

AB	00	01	11	10	L	W
00	①	2	-	-	0	0
01	-	②	3	-	1	1
11	-	4	③	5	1	1
10	1	④	-	-	0	1
00	-	-	3	⑤	1	1

e. Primitive Flow-table

 

f. Merge Diagram

{1,2,5}, {3,4}

{3,4,5}, {1,2}

g. Merge Options

{1,2,5}, {3,4}

h. Selected Groups

AB	00	01	11	10
00	①	②	3	⑤
01	1	④	③	5

i. Merged Flow-table

AB	00	01	11	10
0	①	②	3	⑤
1	1	④	③	5

j. States Assignment

AB	00	01	11	10
0	00	11	(11)	11
1	(0-)	01	11	(11)

LW


k. Output Table

S1 = AB
R1 = B' (R1' = B)
L = A + cr1'.B
W = A + B

l. System Functions

Fig. 5-15 : Traffic-Light Control System Design


5-11

 


a. Basic Block Diagram

$$\begin{aligned} S1 &= AB \\ R1 &= B' \quad (R1' = B) \\ L &= A + cr1'.B \\ W &= A + B \end{aligned}$$

b. System Functions

 


c. Relays SYstem Realization

 

 d. Gates Implementation

$$\begin{aligned} CR1 &= (A.B + cr1)B = \\ &= A.B.B + cr1.B = \\ &= A.B + cr1.B = B(a + cr1) \end{aligned}$$



h. CR1 Function Simplification


INPUTS

A	X1
B	X2

OUTPUTS

Light L	Y1
Warning W	Y2

e. PLC I/O Tables

 

f. PLC Circuit

STORE	x1
AND	x2
OR	cr1
AND	x2
OUT	CR1

STORE NOT	cr1
AND	x2
OR	x1
OUT	Y1

STORE	x1
OR	x2
OUT	Y2

g. PLC Program

Fig. 5-16 : Realization of Fig. 5-15

5-12

1. System FAIL status is expressed by an external signal F=1.
It must activate siren S, until operator confirmation
2. Operator confirms by pressing C button. This de-activates siren.
3. If FAIL signal still exists, confirmation turns on flash light L=1.
4. After confirmation, flash is turned off as soon as fail terminates.




a. System Definition

b. System Block Diagram

(0) -

State	Position	Error Status	Key Status	Alarm Status	Warning Status	FC AL
1	Idle State	NO	OFF	NO	NO	00 00
2	Error exists. Not yet confirmed	YES	OFF	YES	NO	10 10
3	Error exists and is being confirmed (Error exists and operator presses key)	YES	ON	NO	YES	11 01
4	Error exists and been confirmed (Error exists and operator releases key)	YES	OFF	NO	YES	11 01
5	Confirmed key depressed while no error occurs	NO	ON	NO	NO	01 00
6	Error terminated but not yet confirmed (Error exists and operator releases key)	NO	OFF	YES	NO	00 10

c. States Definitions

 

d. Primitive Flow Diagram

{3,4,5} {2,6} {1}

{1,5} {2,6} {3,4}

g. Merge Options

	00	10	11	01
cr1	1	2	3	5
cr2	6	2	3	5
cr3	1	4	3	5


{1,5} {2,6} {3,4}

h. Selected Options

i. Merged Flow Table & States Assignment

FC	00	10	11	01	S	L
	1	2	-	5	0	0
	6	2	3	-	1	0
	-	4	3	5	0	1
	1	4	3	-	0	1
	1	-	3	5	0	0
	6	2	-	5	1	0

e. Primitive Flow Table

 

f. Merge Diagram

FC	00	10	11	01
cr1	0	-	(0)	0
cr2	1	1	-	-
cr3	(0)	0	0	(0)

j. Output Table of S

FC	00	10	11	01
cr1	0	(0)	-	0
cr2	0	0	-	(0)
cr3	-	1	1	-

k. Output Table of L

$$S1 = F'.C'.cr2' + F'.C = F'(C + cr2')$$

$$S2 = cr1.F.C'$$

$$S3 = F.C$$

$$R1 = cr2.F.C' + F.C = F(C + Ccr2)$$

$$R2 = F'.C + F.C = C$$

$$R3 = cr1.F'.C' + cr1.F'.C = cr1.F' (*)$$

$$S = cr2$$

$$L = cr3$$

(*) Non-minimal cell selection enables function minimization

l. Excitation & Output Functions

Fig. 5-17: Alarm System Design

5-13

$$S1 = F'C'.cr2' + F'.C = F'(C + cr2')$$

$$S2 = cr1.F.C'$$

$$S3 = F.C$$

$$R1 = cr2.F.C' + F.C = F(C + cr2)$$

$$R1' = F' + (C'.cr2')$$

$$R2 = F'.C + F.C = C$$

$$R2' = C'$$


$$R3 = cr1.F'.C' + cr1.F'.C = cr1.F'$$

$$R3' = cr1' + F$$


$$A = cr2$$

$$L = cr3$$

a. Excitation & Output Functions

 

b. Typical Relay Flip-Flop

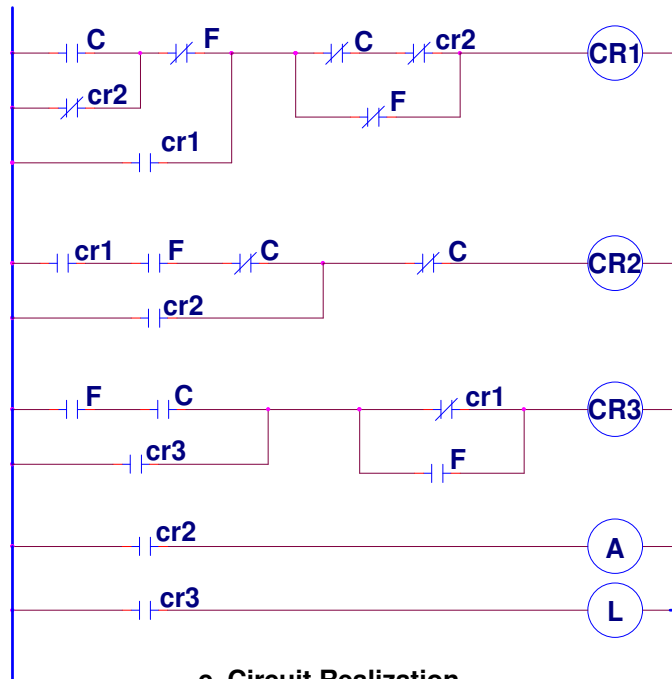

c. Circuit Realization

Fig. 5-18: Realization of Fig. 5-17 by Relays System

5-14

$$\begin{aligned} S1 &= F'C'.cr2' + F'.C = F'(C + cr2') \\ S2 &= cr1.F.C' \\ S3 &= F.C \\ R1 &= cr2.F.C' + F.C = F(C + cr2) \\ R1' &= F' + (C'.cr2') \\ R2 &= F'.C + F.C = C \\ R2' &= C' \\ R3 &= cr1.F'.C' + cr1.F.C = cr1.F' \\ R3' &= cr1' + F \end{aligned}$$

$$A = cr2 \quad L = cr3$$

a. Excitation & Output Functions

INPUTS

F	X1
C	X2

OUTPUTS


Alarm A	Y1
Flash L	Y2

b. PLC I/O Tables

Y1 → CR2

Y2 → CR3

c. CR Equivalence

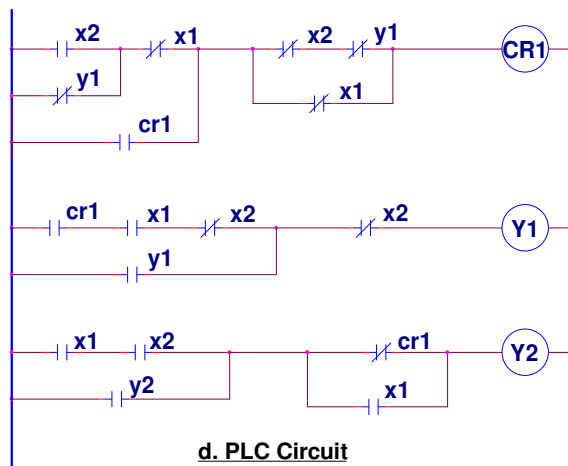

STORE	x2
OR NOT	y1
AND NOT	x1
OR	cr1
STORE NOT	x2
AND NOT	y1
OR NOT	x1
AND	STORE
OUT	CR1
AND	x1
AND NOT	x2
OR	y1
AND NOT	x2
OUT	Y1
STORE	x1
AND	x2
OR	y2
STORE NOT	cr1
OR	x1
AND	STORE
OUT	Y2

e. PLC Program

Fig. 5-19: Realization of Fig. 5-17 by PLC



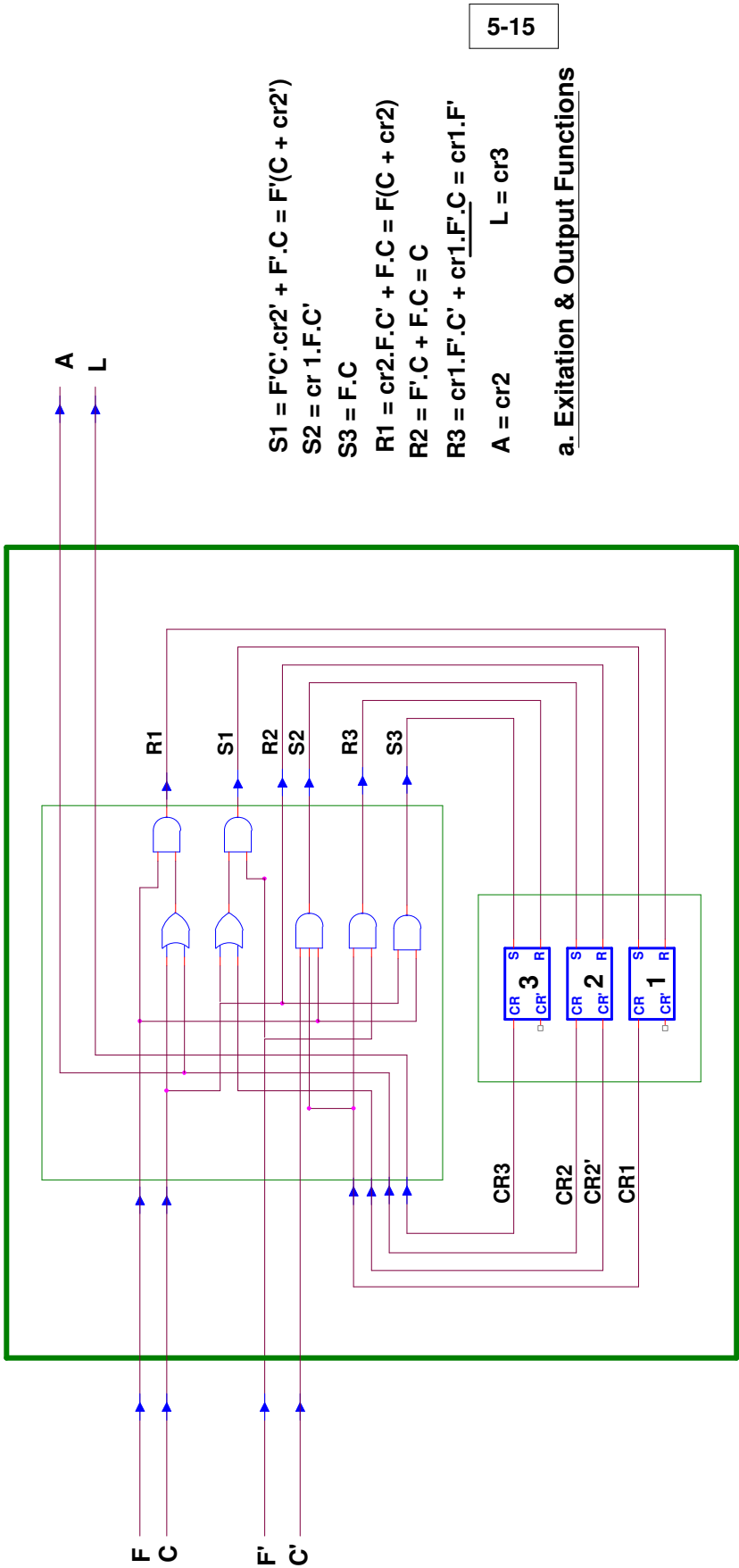
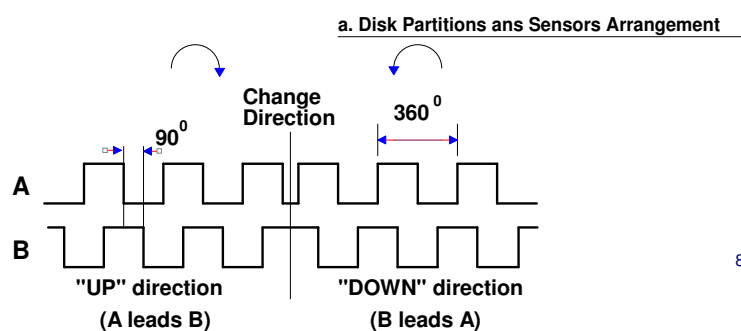


Fig. 5-20: Realization of Fig. 5-17 by Electronic Gates System

5-16

 

 b. Encoder Code Waveforms for Both Directions




d. Primitive Flow-diagram

AB

00	01	11	10	D
1	5	-	2	0
6	-	3	2	0
-	4	3	7	0
1	4	8	-	0
1	5	8	-	1
6	5	-	2	1
6	-	3	7	1
-	4	8	7	1

e. Primitive Flow-table

 

f. Merge Diagram

g. Merged Flow-table & State Assignment

AB	D			
	00	01	11	10
cr1	1	5	8	2
cr2	6	5	3	2
cr3	6	4	3	7
cr4	1	4	8	7

g. Merged Flow-table & State Assignment

AB		D			
		00	01	11	10
cr1	0	1	(1)	(0)	
cr2	1	(1)	(0)	0	
cr3	(1)	(0)	0	1	
cr4	(0)	0	1	(1)	

h. Output Table

$$S1 = cr2.A'B + cr4.A'B'$$

$$S2 = cr1.AB' + cr3.A'B'$$

$$S3 = cr2.A.B + cr4.A.B'$$

$$S4 = cr1.A.B + cr3.A'B$$

$$R1 = cr2.A.B' + cr4.A.B$$

$$R2 = cr1.A'B + cr3.AB$$

$$R3 = cr2.A'B' + cr4.A'B$$

$$R4 = cr1.A'B' + cr3.AB'$$

$$D = cr1.B + cr2.A' + cr3.B' + cr4.A$$

i. Excitation and Output Functions

Initially, while A=B=0, and all Flip-flops are in reset state (CRI=0).

At that state, Flip-flop 1 must be set, with no conflict later, that is to say, while CR2 and CR3 are not set.

$$S1 = cr2.A'B + cr2'.cr3'.A'B'$$

j. Corrected System Initialization

Fig. 5-21 : Motor Direction Detection System Design

5-17

$$S1 = A'(cr2.B + cr2'.cr3'.B')$$

$$S2 = B'(cr1.A + cr3.A')$$

$$S3 = A(cr2.B + cr4.B')$$

$$S4 = B(cr1.A + cr3.A')$$

$$R1 = A(cr2.B' + cr4.B)$$

$$R2 = B(cr1.A' + cr3.A)$$

$$R3 = A'(cr2.B' + cr4.B)$$

$$R4 = B'(cr1.A' + cr3.A)$$

$$R1' = A' + (cr2' + B).(cr4' + B')$$


$$R2' = B' + (cr1' + A).(cr3' + A')$$

$$R3' = A + (cr2' + B).(cr4' + B')$$

$$R4' = B + (cr1' + A).(cr3' + A')$$

$$D = cr1.B + cr2.A' + cr3.B' + cr4.A$$

a. Excitation and Output Functions

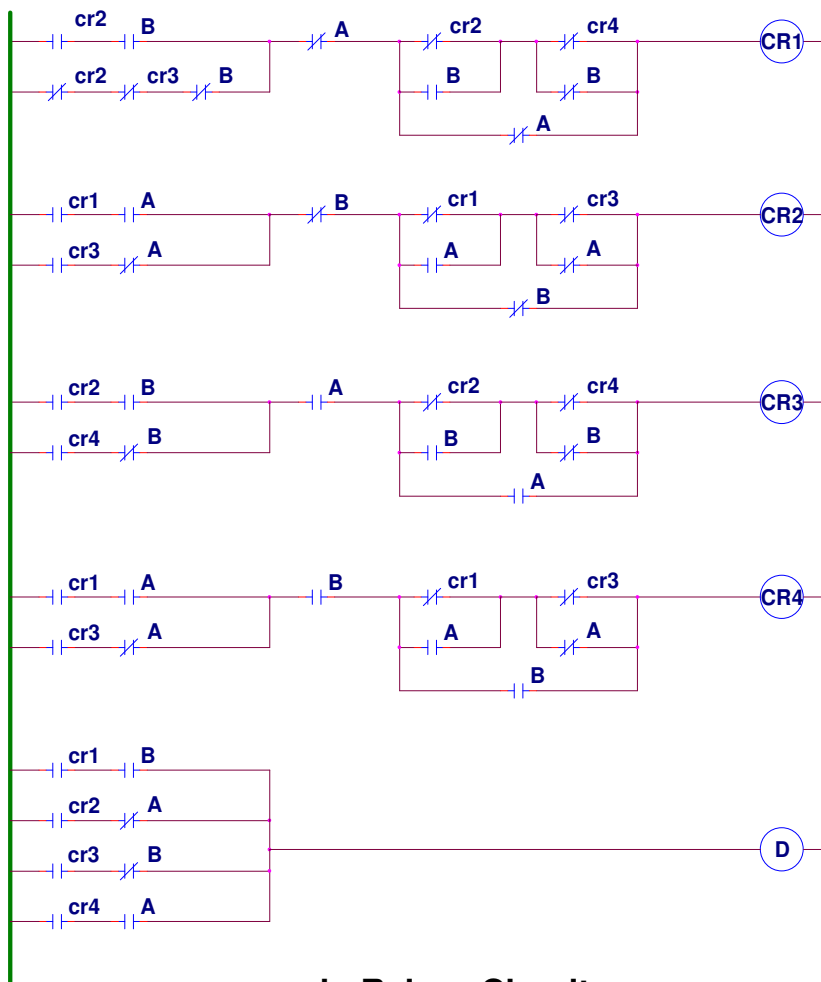

b. Relays Circuit

Fig. 5-22: Realization of Fig. 5-21 by Relay System

5-18

$$S1 = A'(cr2B + cr2'.cr3'.B')$$

$$S2 = B'(cr1.A + cr3.A')$$

$$S3 = A(cr2.B + cr4.B')$$

$$S4 = B(cr1.A + cr3.A')$$

$$R1 = A(cr2.B' + cr4.B)$$

$$R2 = B(cr1.A' + cr3.A)$$

$$R3 = A'(cr2.B' + cr4.B)$$

$$R4 = B'(cr1.A' + cr3.A)$$

$$R1' = A' + (cr2' + B).(cr4' + B')$$

$$R2' = B' + (cr1' + A).(cr3' + A')$$

$$R3' = A + (cr2' + B).(cr4' + B')$$

$$R4' = B + (cr1' + A).(cr3' + A')$$

$$D = cr1.B + cr2.A' + cr3.B' + cr4.A$$

a. Exitation and Output Functions


INPUTS

A	X1
B	X2

OUTPUTS

Direction D	Y1
-------------	----

b. PLC I/O Tables

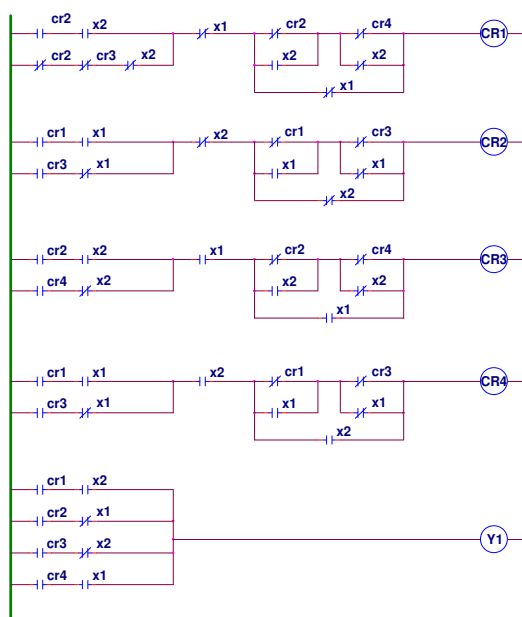

c. PLC Circuit

```
STORE cr2
AND x2
STORE NOT cr2
AND NOT cr3
AND NOT x2
OR STORE
AND NOT x1
STORE NOT cr2
OR x2
STORE NOT cr4
OR NOT x2
AND STORE
OR NOT x1
AND STORE
OUT CR1
```

```
AND x1
STORE cr3
AND NOT x1
OR STORE
AND NOT x2
STORE NOT cr1
OR x1
STORE NOT cr3
OR NOT x1
AND STORE
OR NOT x2
AND STORE
OUT CR2
```

```
AND x2
STORE cr4
AND NOT x2
OR STORE
AND NOT x1
STORE NOT cr2
OR x2
STORE NOT cr4
OR NOT x2
AND STORE
OR NOT x1
AND STORE
OUT CR3
```

```
STORE cr1
AND x1
STORE cr3
AND NOT x1
OR STORE
AND x2
STORE NOT cr1
OR x1
STORE NOT cr3
OR NOT x1
AND STORE
OR NOT x2
AND STORE
OUT CR4
```

```
STORE cr1
AND x2
STORE cr2
AND NOT x1
OR STORE
STORE cr3
AND NOT x2
OR STORE
STORE cr4
AND x1
OR STORE
OUT Y1
```

d. PLC Program

Fig. 5-23: Realization of Fig. 5-21 by PLC

5-19

1. A security door is controlled by two input switches : X1 and X2 .
2. The door is opened and closed, by entering the following sequence :

$X1, X2 = 00, 10, 11, 10, 11, \dots, 00$


Open (T=1) Close (T=0)

Actually, door is opened when latest 5 inputs satisfy the sequence 00, 10, 11, 10, 11, and closed as soon as both inputs become 0 ($X1X2=00$).


a. System Definition



b. System Block Diagram

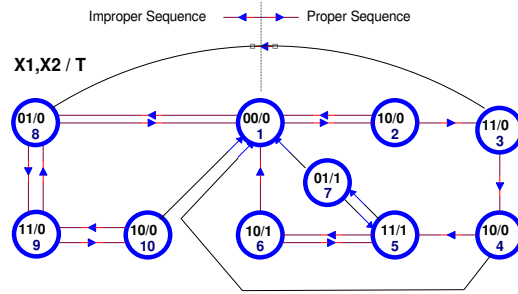

c. Primitive Flow Diagram

 

e. Merge Diagram

X1,X2	00	01	11	10	T
00	1	8	-	2	0
01	1	-	3	2	0
11	-	8	3	4	0
10	1	-	5	4	0
00	-	7	5	6	1
01	1	-	5	6	1
11	1	7	5	-	1
10	1	8	9	-	0
00	-	8	9	10	0
01	1	-	9	10	0

d. Primitive Flow Table

X1,X2	00	01	11	10
cr1	1	8	3	2
cr2	-	8	3	4
cr3	1	-	5	4
cr4	1	7	5	6
cr5	1	8	9	10

g. Merged Flow Table & States Assignment

X1,X2	00	01	11	10
cr1	0	-	-	0
cr2	-	-	0	-
cr3	-	-	-	0
cr4	-	1	1	1
cr5	-	0	0	0

h. Output Table

f. Selected Merge Partitions

$$\begin{aligned}
 S1 &= X1'.X2' & R1 &= cr2.X1.X2 + cr5.X1'.X2 \\
 S2 &= cr1.X1.X2 & R2 &= cr3.X1.X2' + cr5.X1'.X2 \\
 S3 &= cr2.X1.X2' & R3 &= cr4.X1.X2 + X1'.X2' \\
 S4 &= cr3.X2 & R4 &= X1'.X2' \\
 S5 &= cr4'.X1'.X2 & R5 &= X1'.X2'
 \end{aligned}$$

$$T = cr4$$

i. System Functions

Fig. 5-24 : Combination Lock System Design

CHAPTER 6

PNEUMATIC CONTROL SYSTEMS

Pneumatic Cascade
Efficient Valve Implementation
Emergency-Stop Modes

6-1


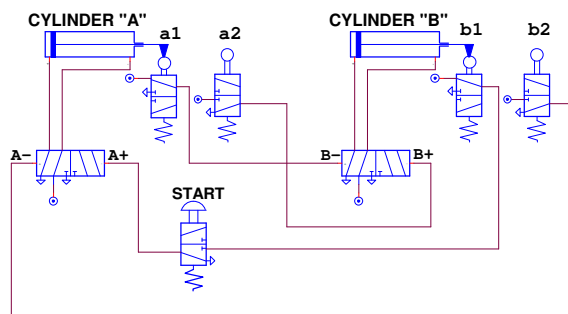


Fig. 6-1 : Intuitive Design for Sequence Start , A+,B+,A-,B-

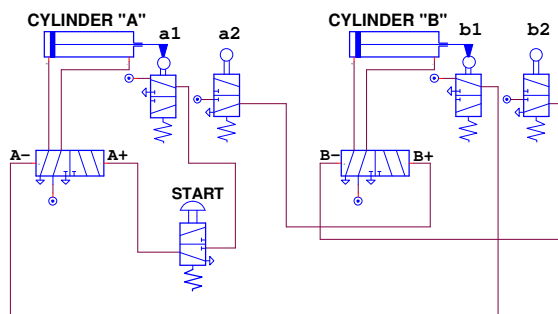

START (A+) Conflicts With A- Actuation (by b1)
More Conflicting States

Fig. 6-2 : Sequence Start , A+,B+,B-,A-

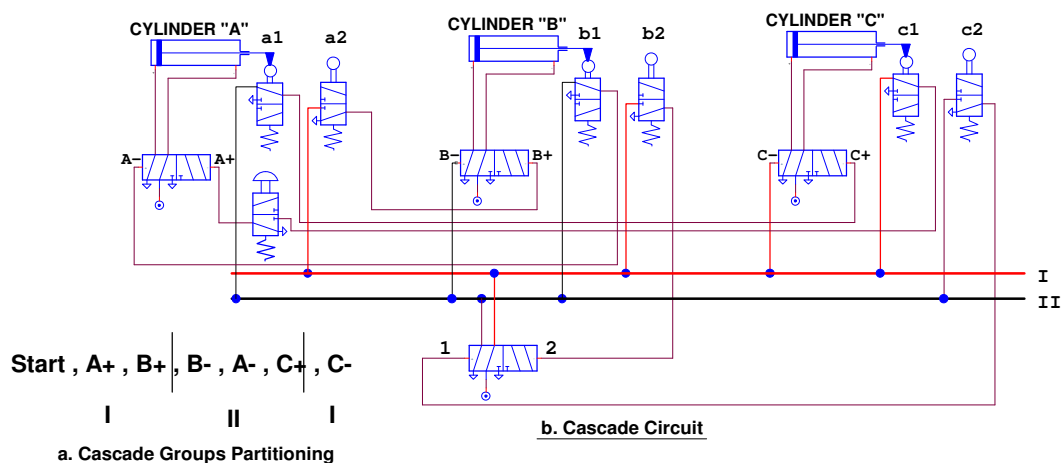


Fig. 6-3 : Cascade Design for Sequence Start , A+,B+,B-,A-,C+,C-

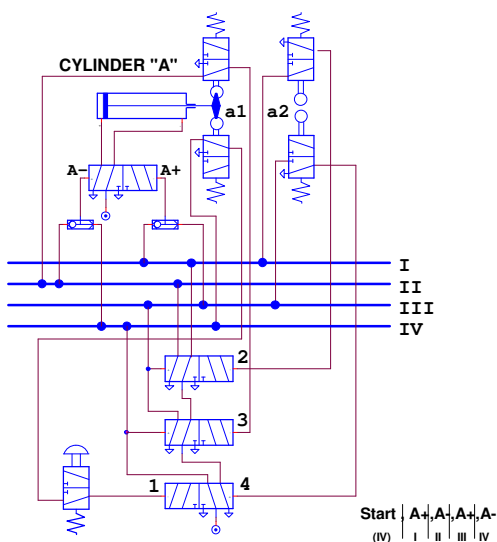


Fig. 6-4 : Cascade System for Sequence Start , A+,A-,A+,A- (Cascade)

 


Fig. 6-5: Multiple Limit Valves Replacement

6-2

Pure pneumatic control system

Simplicity and reliability

Limited to control cylinders with actuation valves that satisfy the following restrictions :

- * Valves do not have return springs
- * Valves are operated pneumatically (no solenoids)

Group Partitioning differences between pneumatic and relays cascade are :

- * There is always an active group, even when not operating (START is also included within a group)
- * Last Group may be merged with first group, provided that groups do not conflict

Fig. 6-6 : Pneumatic Cascade Basic Concept


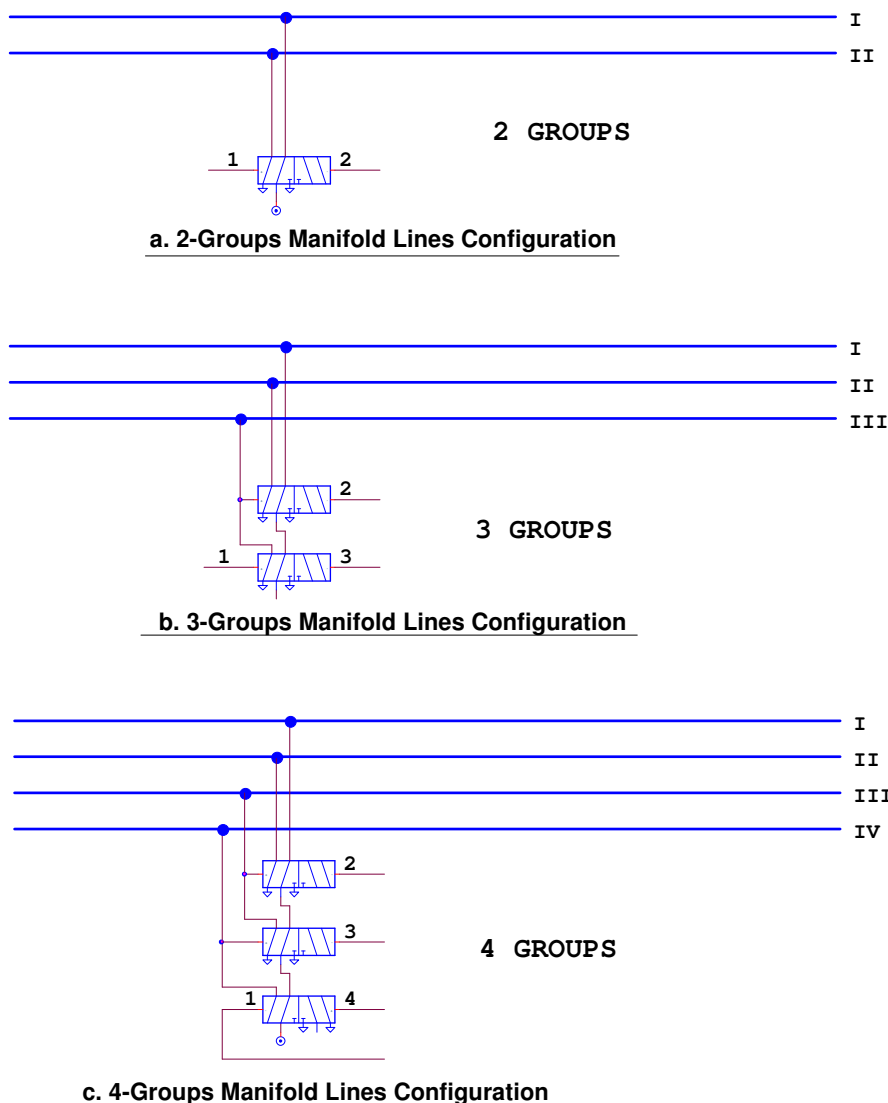



Fig. 6-7 : Pneumatic Cascade Group Configurations

 

a. Process Sequence Definition


b. Sequence Groups Partitioning

 1. cylinder actuated by valves without return springs.
2. A set of two limit valves.




c. Single-Cycle Cylinder Requirement

 1. cylinder actuated by valves without return springs
2. Two sets of two limit valves.
3. A two-input OR gate for each valve control.




d. Two-Cycle Cylinder Requirement

 1. System consists of 3 cylinders, each equipped with limit-valves
2. Cylinders "A" and "C" perform single cycle (each), and require a single set of limit valves.
3. Cylinder "B" performs two cycles, and requires two sets of limit-valves, and OR valves.
4. A START valve is also required.




e. System Cylinders Requirements

Fig. 6-8 : Pneumatic Cascade Design Process Steps

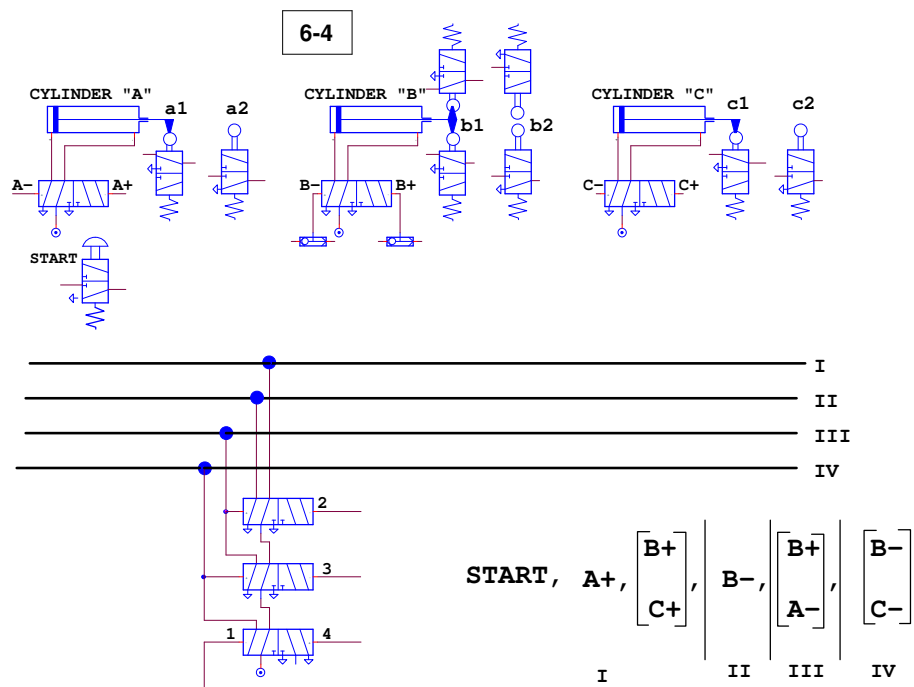

f. System Components

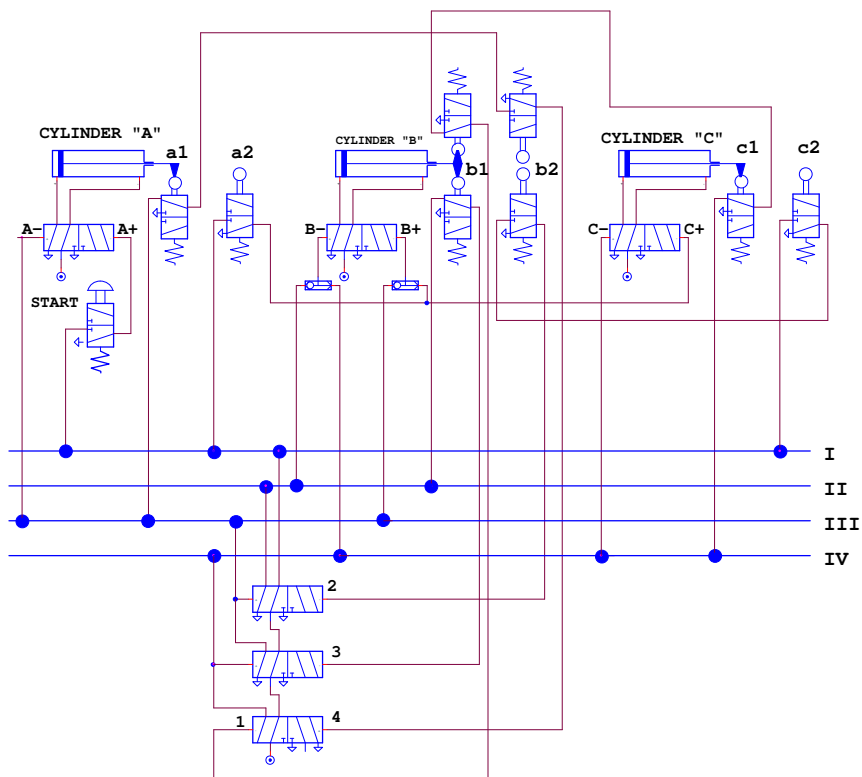

g. Complete System

Fig. 6-8 : Pneumatic Cascade Design Process Steps

(Cont'd)

6-5

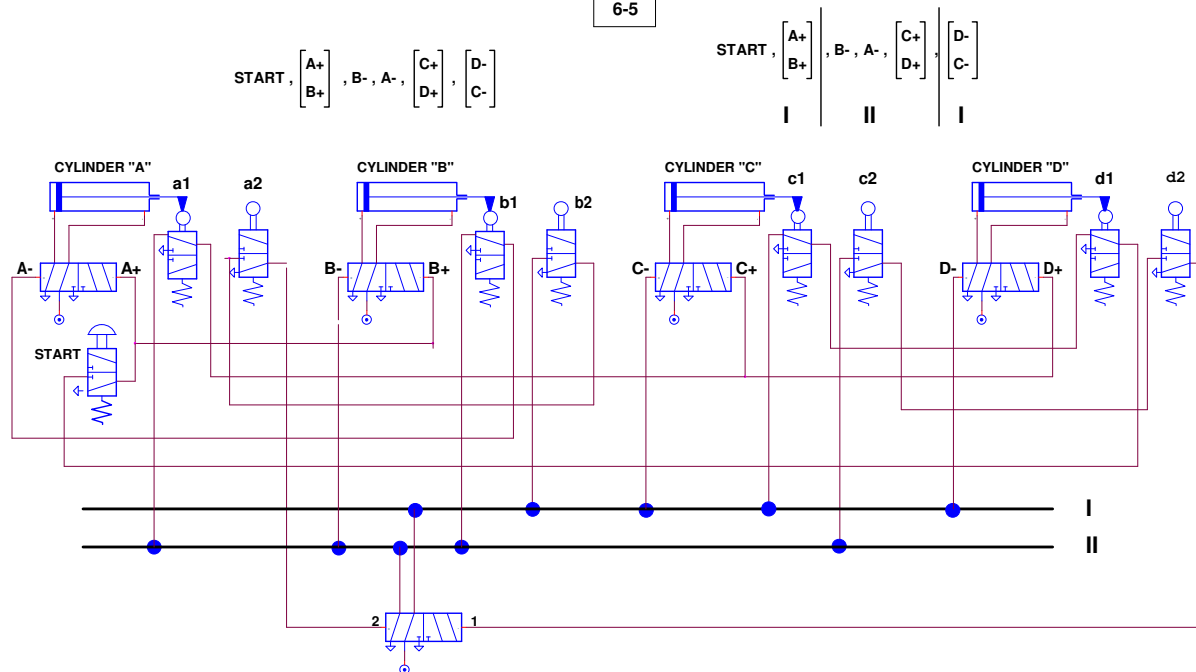


Fig. 6-9 : Pneumatic Cascade Example 1

(from semester exam September 2002)

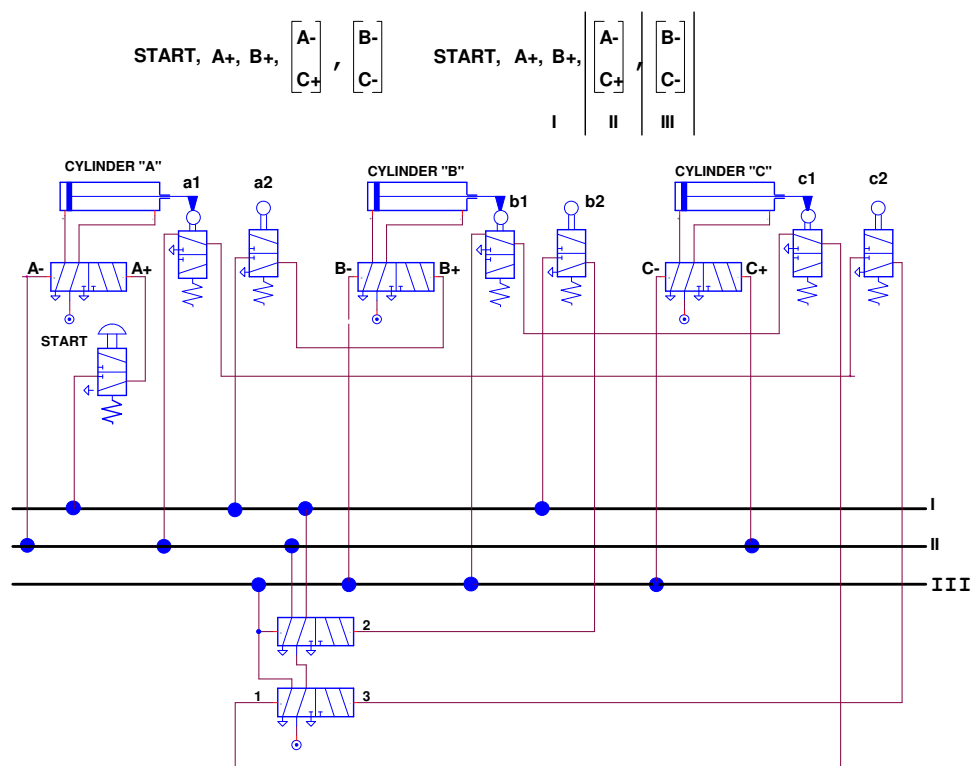


Fig. 6-10 : Pneumatic Cascade Example 2

(from semester exam July 2002)

Efficient Use of Directional-Control Valves in Fluid-Logic Circuits

Various types of directional-control valves have been systematically analyzed to determine the logic output functions obtained for different input-signal combinations. It was found that a surprisingly large variety of fairly complex logic functions can be obtained with a single valve. The results are summarised in five tables which include 186 (i.e. all the significant) input-signal combinations. Several examples are presented, illustrating how the tables can be used to implement given fluid-logic functions with a minimum number of valves. It thus becomes possible to exploit the logic capacity of these valves to their fullest extent, which can result in considerable reduction in the number of valves.

D.W. Pessen
Associate Professor
Dept of Mechanical Engineering,
Technion - Israel Institute of Technology,
Haifa, Israel
Mem ASME

 


Fig. 7-19 : Examples of Complex Functions

- a. 3/2 Valve , Single Output Function
- b. Two Separate Output Function, 2 Input Variables
- c. Two Separate Output Function, 3 Input Variables
- d. Two Separate Output Function, 4/5 Input Variables
- e. Two Separate Flip-Flop Output Function


a. Function Search Order

1	YES
2	NOT
3	AND
4	OR
5	INHIBITION
6	IMPLICATION
7	SELECTOR


b. Tables List

Fig. 6-12 : Function Tables Arrangement

Fig. 6-11 : Function Tables Background

 

a. Valves Pins Assignment

 

Line No.	Function Name	Boolean Function	P	2	3
1	YES	$T = A$	A	1	0
2	NOT	$T = A'$	A	0	1
3	AND	$T = AB$	B	A	0
4	AND	$T = AB$	B	A	B
5	OR	$T = A+B$	B	1	A
6	OR	$T = A+B$	B	B	A
7	INHIBITION	$T = AB'$	B	0	A
8	IMPLICATION	$T = A+B'$	B	A	1
9	SELECTOR	$T = AC+BC'$	C	A	B

b. 3/2 Valve Connections yielding Single Output Function

Fig. 6-13 : 3/2 Valve Connections yielding Single Output Function and Valves Pins Assignment

Note : Use of shuttle valves is usually less expensive.

6-7

No.	Function Names	Output 1	Output 2	5/2 Valve	6/2 Valve	5/3 Valve
10	YES/NOT	T2=A	T1=A'	P 2 3 4	P 2 3 4 5	P1 P2 2 3 4
12	YES/AND	T2=B	T1=AB	A 0 1 0	B A 0 1 0	
13	YES/OR	T2=B	T1=A+B		B 1 A 1 0	
14	YES/INHIBITION	T1=B	T2=AB'	B 1 0 A		
16	YES/IMPLICATION	T2=B	T1=A+B'	B A 1 0		
18	NOT/AND	T2=B'	T1=AB	B A 0 1		
21	NOT/OR	T1=B'	T2=A+B	B 0 1 A		
24	NOT/INHIBITION	T1=B'	T2=AB'		B 0 1 0 A	
25	NOT/IMPLICATION	T1=B'	T2=A+B'		B 0 1 A 1	
26	AND/OR	T2=AB	T1=A+B	B 1 A 0		
27	AND/OR	T2=AB	T1=A+B	B B A 0		
36	AND/INHIBITION	T2=AB	T1=AB'	B 0 A 0		
42	AND/IMPLICATION	T1=AB	T2=A+B'		B A 0 A 1	B A A 0 1
43	AND/IMPLICATION	T1=AB	T2=A+B'			A B A 1 0
45	OR/INHIBITION	T1=A+B	T2=AB'			
46	OR/INHIBITION	T1=A+B	T2=AB'		B 1 A 0 A	
47	OR/INHIBITION	T1=A+B	T2=AB'		B B A 0 A	
48	OR/IMPLICATION	T2=A+B	T1=A+B'	B A 1 A		
54	INHIBITION/INHIBITION	T1=A'B	T2=AB'			A B 0 1 0
55	INHIBITION/IMPLICATION	T1=AB'	T2=A+B'	B 0 A 1		
58	IMPLICATION/IMPLICATION	T1=A+B'	T2=A'+B			A B 1 0 1

: Valve Connections Yielding Two Separate Outputs, Two Variables

Fig. 6-14

6-8

No.	FUNCTION NAME	BOOLEAN FUNCTION 1	BOOLEAN FUNCTION 2	Valve 5/2 P 2 3 4	Valve 6/2 P 2 3 4 5	Valve 5/3 P1 P2 2 3 4
59	YES/SELECTOR	T2=C	T1=AC+BC'		C A B 1 0	
60	NOT/SELECTOR	T2=C'	T1=AC+BC'		C A B 0 1	
61	AND/OR	T1=AB	T2=B+C	B A B C		
66	AND/AND	T1=AC	T2=BC		C A 0 B 0	
70	AND/INHIBITION	T1=AC	T2=BC'	C A 0 B		
73	AND/IMPLICATION	T1=AC	T2=B+C'		C A 0 B 1	
75	AND/SELECTOR	T2=BC	T1=AC+BC'	C A B 0		
79	AND/SELECTOR	T2=AC	T1=AC+BC'		C A B A 0	
81	OR/OR	T1=B+C	T2=A+C		C 1 B 1 A	
84	OR/OR	T1=B+C	T2=A+C		C C B C A	
85	OR/INHIBITION	T1=B+C	T2=AC'		C 1 B 0 A	
86	OR/INHIBITION	T1=B+C	T2=AC'		C C B 0 A	
87	OR/IMPLICATION	T2=A+C	T1=B+C'	C B 1 A		
90	OR/SELECTOR	T1=A+C	T2=AC+BC'	C 1 A B		
91	OR/SELECTOR	T1=A+C	T2=AC+BC'	C C A B		
94	OR/SELECTOR	T1=B+C	T2=AC+BC'		C 1 B A B	
95	OR/SELECTOR	T1=B+C	T2=AC+BC'		C C B A B	
96	INHIBITION/INHIBITION	T1=AC'	T2=BC'		C 0 A 0 B	
97	INHIBITION/INHIBITION	T1=AB'C	T2=ABC'			B C 0 A 0
99	INHIBITION/IMPLICATION	T1=AC'	T2=B+C'		C 0 A B 1	
100	INHIBITION/IMPLICATION	T1=AB'C	T2=A+B'+C			B C 0 A 1
101	INHIBITION/SELECTOR	T1=AC'	T2=AC+BC'	C 0 A B		
103	INHIBITION/SELECTOR	T1=BC'	T2=AC+BC'		C 0 B A B	
104	IMPLICATION/IMPLICATION	T1=A+C'	T2=B+C'		C A 1 B 1	
105	IMPLICATION/IMPLICATION	T1=A+B+C'	T2=A+B'+C			B C 1 A 1
107	IMPLICATION/SELECTOR	T2=B+C'	T1=AC+BC'	C A B 1		
109	IMPLICATION/SELECTOR	T2=A+C'	T1=AC+BC'		C A B A 1	
110	SELECTOR/SELECTOR	T2=AC+BC'	T1=AC'+BC	C A B A		
112	AND+AND/AND+AND	T1=AB+AC	T2=AC+BC			C A A B C
113	AND+AND/AND+	T1=AB+AC	T2=A+BC			C A A B A
114	AND+AND/INHIBITION	T1=AB+AC	T2=A'BC			C A A B 0
115	AND+AND/IMPLICATION	T1=AB+AC	T2=A+B+C'			C A A B 1
117	AND+INHIBITION/AND+INHIBITION ...	T1=AB+AC'	T2=AB'+AC			B C A 0 A
118	AND+INHIBITION/INHIBITION+	T1=AB+AC'	T2=A+BC'			B C A B A
119	AND+INHIBITION/OR	T1=AB+AC'	T2=B+C			B C A B C
120	AND+INHIBITION/AND	T1=AB+AC'	T2=BC			B C A 0 B
121	AND+INHIBITION/INHIBITION	T1=AB+AC'	T2=BC'			B C A B 0
122	AND+INHIBITION/IMPLICATION	T1=AB+AC'	T2=B'+C			B C A 0 1
127	AND+/AND+	T1=A+BC	T2=C+AB			A C A B C
128	AND+/INHIBITION	T1=A+BC	T2=ABC'			A C A B 0
129	AND+/IMPLICATION	T1=A+BC	T2=A'+B+C			A C A B 1
131	INHIBITION+/INHIBITION+	T1=A+BC'	T2=A+B'C			C B A 1 A
132	INHIBITION+/OR	T1=A+BC'	T2=B+C			C B A 1 B
133	INHIBITION+/AND	T1=A+BC'	T2=BC			C B A B C
134	INHIBITION+/INHIBITION+	T1=A+BC'	T2=B'C			C B A 1 0
135	INHIBITION+/IMPLICATION	T1=A+BC'	T2=B+C'			C B A B 1

Fig 6-15 : Valve Connections Yielding 2 Separate Output Functions, 3 Variables

6-9

No.	Function Names	Output 1	Output 2	5/2 Valve P 2 3 4	6/2 Valve P 2 3 4 5	5/3 Valve P1 P2 2 3 4
	5 VARIABLES					
140		$T1 = AE + BE'$	$T2 = CE + DE'$			
141		$T1 = AB + AC' + B'CD$	$T2 = CE + B'E + BC'D$		E A B C D	B C A D E
142	AND/SELECTOR	$T2 = CD$	$T1 = AD + BD'$		D A B C 0	
143	AND/SELECTOR	$T2 = CD$	$T1 = AD + BD'$		D A B C D	
144	OR/SELECTOR	$T2 = C + D$	$T1 = AD + BD'$		D A B 1 C	
145	OR/SELECTOR	$T2 = C + D$	$T1 = AD + BD'$		D A B D C	
146	INHIBITION/SELECTOR	$T2 = CD'$	$T1 = AD + BD'$		D A B 0 C	
147	IMPLICATION/SELECTOR	$T2 = C + D'$	$T1 = AD + BD'$		D A B C 1	
148	SELECTOR/SELECTOR	$T1 = AD + BD'$	$T2 = BD + CD'$	D A B C	D A B C B	
149	SELECTOR/SELECTOR	$T1 = AD + BD'$	$T2 = CD + BD'$		D A B C A	
150	SELECTOR/SELECTOR	$T1 = AD + BD'$	$T2 = CD + AD'$		D A B C A	
151	SELECTOR/SELECTOR	$T1 = AD + BD'$	$T2 = AD + CD'$		D A B A C	
152	AND+INHIBITION/AND+INHIBITION	$T1 = AB + AC'$	$T2 = CD + B'D$			B C A 0 D
153	AND+INHIBITION/INHIBITION+	$T1 = A + B'C$	$T2 = CD + B'D$			B C A C D
154	INHIBITION+/INHIBITION+	$T1 = A + B'C$	$T2 = D + BC'$			B C A 1 0
155		$T1 = AB + AC' + B'CD$	$T2 = C + BD$			B C A D C
156		$T1 = AB + AC' + B'CD$	$T2 = BC + BD$			B C A D B
157		$T1 = AB + AC' + B'CD$	$T2 = BC'D$			B C A D 0
158		$T1 = AB + AC' + B'CD$	$T2 = B' + C + D$			B C A D 1
159		$T1 = AB + AC' + B'CD$	$T2 = AB' + AC + B'CD$			B C A D A
160		$T1 = AB + AC' + B'CD$	$T2 = D$			B C A D D

: Valve Connections Yielding Two Separate Outputs, 4-5 Variables

Fig. 6-16

6-10

No.	Output 1	Output 2	3/2 Valve 2 3	5/2 Valve 2 3 4
<u>No Input Variables</u>				
161	T=y		1 0	
162	T1=y'	T2=y		0 1 0
163	T1=y	T2=y'		1 0 1
<u>One Input Variables</u>				
164	T=Ay		A 0	
165	T=Ay'		0 A	
166	T1=Ay'	T2=Ay		0 A 0
167	T1=Ay	T2=Ay'		A 0 A
168	T1=Ay	T2=y'		A 0 1
169	T1=y	T2=Ay'		1 0 A
170	T=A+y'		A 1	
171	T=A+y		1 A	
172	T1=A+y	T2=A+y'		1 A 1
173	T1=A+y'	T2=A+y		A 1 A
174	T1=A+y'	T2=y		A 1 0
175	T1=y'	T2=A+y		0 1 A
176	T1=Ay'	T2=A+y'		0 A 1
177	T1=A+y	T2=Ay		1 A 0
<u>Two Input Variables</u>				
178	T1=Ay	T2=By'		A 0 B
179	T1=A+y'	T2=B+y		A 1 B
180	T1=Ay+By'		A B	
181	T1=Ay+By'	T2=By		A B 0
182	T1=Ay+By'	T2=B+y'		A B 1
183	T1=Ay'	T2=Ay+By'		0 A B
184	T1=A+y	T2=Ay+By'		1 A B
185	T1=Ay+By'	T2=By+Ay'		A B A
<u>Three Input Variables</u>				
186	T1=Ay+By'	T2=By+Cy'		A B C

Fig. 6-17 : Valve Connections Yielding Flip-Flop Output Functions


 


Fig. 6-18 : Example 1


6-11

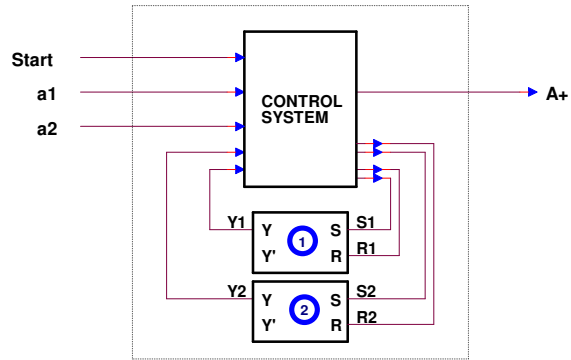

d. System Solution Block Diagram
(Huffman Method Realization)

START,A+,A-,A+,A-

a. Process Sequence

 

b. System Block Diagram

$$S1 = \text{Start}.a1.y2' \quad R1 = a1.y2$$

$$S2 = a2.y1 \quad R2 = a2.y1'$$


$$A+ = y1.y2' + y1'.y2$$

$$A- = a2$$

C. Huffman Method Solution

- * Start , a1, a2 are external signals
- * y1 ,y2 are outputs of internal flip-flops
- * S1,R1,S2,R2 are Set/Reset of those flip-flops
- * Functions that contain only external variables are to be searched in first 4 tables
- * Function that contain internal variables (y) are to be searchedfirst in fifth table
- * In current system, all functions contain internal variables, so they are to be searched in fifth table

e. Design Considerations

 

f. System Valve Circuit

Fig. 6-19 : Example 2

START,A+,B+,B-,A-,B+,B-

6-12

a. Process Sequence

a1b1	a2b1	a2b2	a1b2	A+	A-	B+	B-
1	2	-	-	1	0	0	-
-	2	3	-	-	0	1	0
-	4	3	-	-	0	0	1
5	4	-	-	0	1	0	-
5	-	-	6	0	-	1	0
1	-	-	6	0	-	0	1


b. Primitive Flow Table

{1,2,6} {3,4,5}

d. Selected Option

y	b1	b2
0	1 2 3 6	
1	5 4 3 6	
	a1 a2 a1	

e. Merged Flow Table & States Assignment

 

c. Merge Diagram

y	b1	b2
0	0 0 1 0	
1	- - - 0	
	a1 a2 a1	

$$S = a2.b2$$

y	b1	b2
0	- - 0 -	
1	0 0 0 1	
	a1 a2 a1	

$$R = a1.b2$$

f. Exitation Functions

y	b1	b2
0	1 - 0 0	
1	0 0 - 0	
	a1 a2 a1	

$$A+ = \text{Start}.b1.y'$$

y	b1	b2
0	0 0 0 -	
1	- 1 0 -	
	a1 a2 a1	

$$A- = b1.y$$


y	b1	b2
0	0 1 - 0	
1	1 0 0 -	
	a1 a2 a1	

$$B+ = a2.y' + a1.y$$

y	b1	b2
0	- 0 - 1	
1	0 - 1 -	
	a1 a2 a1	

$$B- = b2$$

g. Output Functions

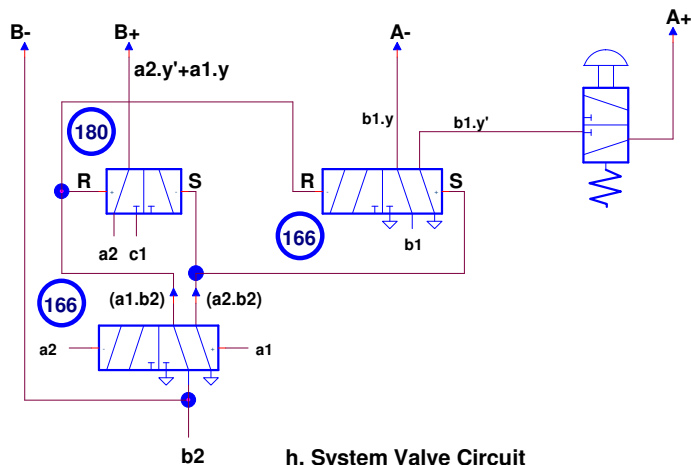


h. System Valve Circuit

Fig. 6-20 : Solution for Sequence START,A+,B+,B-,A-,B+,B-


EMERGENCY STOP

Stop process due to emergency condition
Easy accessible buttons
Safety continuation Restart (Continue)
Different modes
Add-on

a. Target & Definition

 

b. Single STOP-RESTART button

 

c. Separate STOP/RESTART buttons

Fig. 6-21 : STOP-RESTART Single/Separate Buttons

 


Fig. 6-22 : STOP-RESTART With Multiple Remote-Control STOP Buttons


 



Fig. 6-23 : Electric STOP-RESTART System With Multiple Remote-Control STOP Buttons

No Change Cylinder at rest must remain at rest. Cylinder in motion must complete its stroke, and remain at rest.
No Motion Cylinder at rest must remain at rest. Cylinder in motion must be disconnected from pressure and move until stopped by friction (or end stroke).
Lock Piston Cylinder at rest must remain at rest. Cylinder in motion must be locked at its current position.
Safety Position Cylinder must be moved to its either (+) or (-) position, which been pre-definrd as "Safety Position".
No-Change/No-Motion Combination of No-Change and No-Motion modes.
No-Change/Lock-Piston Combination of No-Change and Lock-Piston modes.
No-Change/Safety-Position Combination of No-Change and Safety-Position modes.


Fig. 6-24 : Emergency Stop Modes Definition

 


a. No-Change Mode Pneumatic Actuation

 

b. No-Change Mode Electric Actuation

 

c. No-Motion Mode Pneumatic Actuation

 

d. No-Motion Mode Electric Actuation

Fig. 6-25 : No-Change & No-Motion Circuits

 


Fig. 6-26 : "Lock-Piston" Mode Circuit

 


Fig. 6-29 : "No-Change/No-Motion" Mode Circuit

 


Fig. 6-27 : "Safety-Position" Mode Circuit
(Applied to an Individual Cylinder)

 


Fig. 6-30 : Karnaugh Maps for
"No-Change/Safety-Position" Circuit

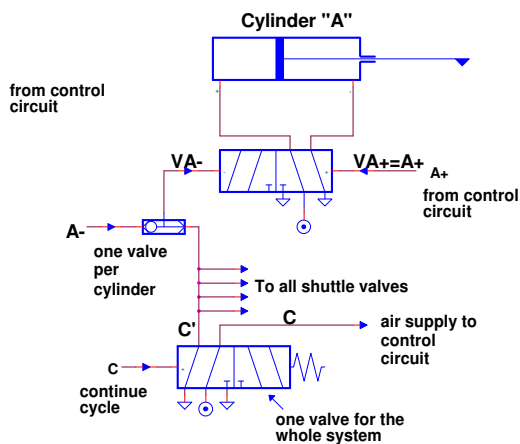


Fig. 6-28 : "Safety-Position" Mode Circuit
(Applied to Entire System)

 


Fig. 6-31 : "No-Change/Safety-Position" Mode Circuit

CHAPTER 7

HARDWARE PROGRAMMERS

Drum Programmer

Programmable Counter 1/n

Programmable Counter 2/n

 


Fig. 7-1 : Drum programmer. (Courtesy of Amerace Corp.)

7-2


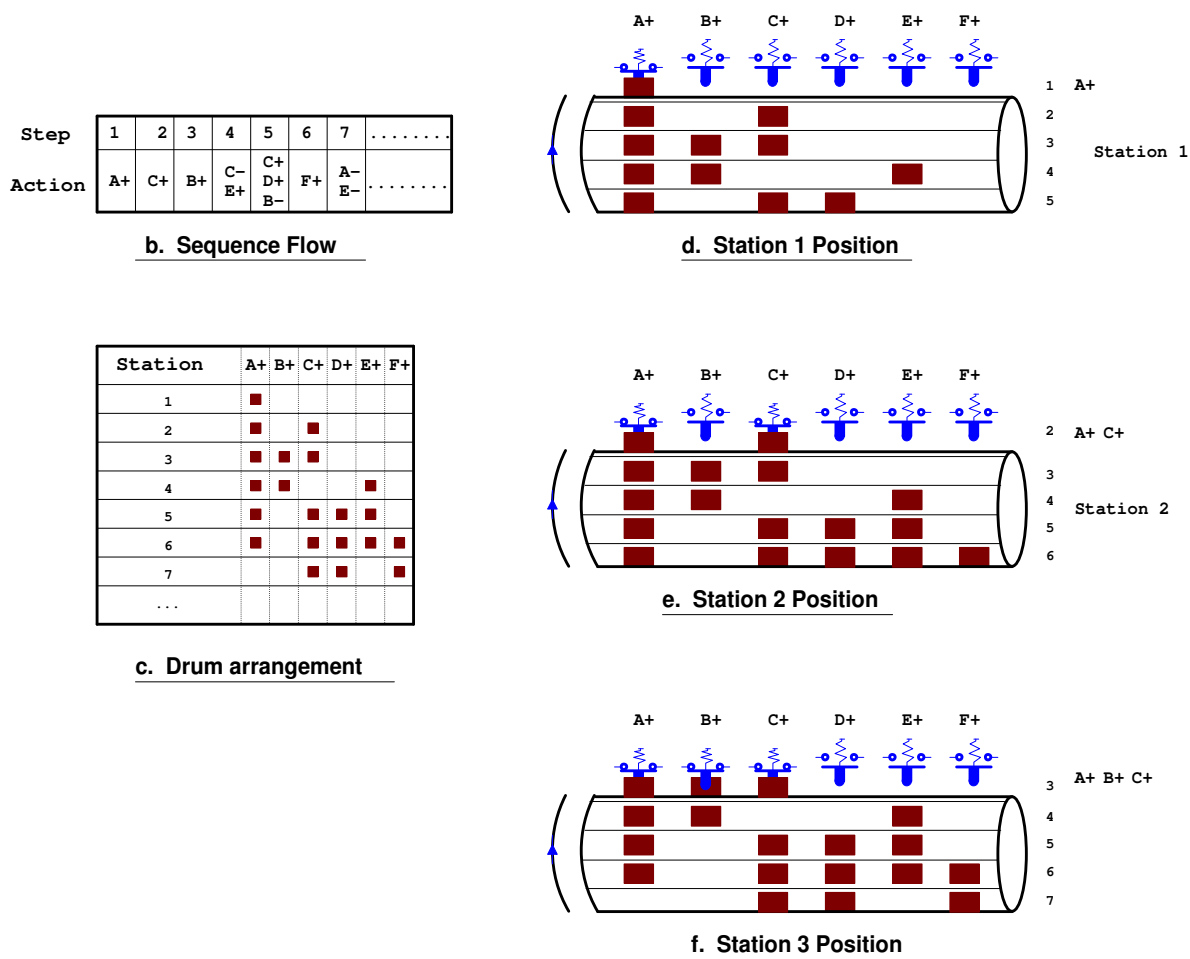


Fig. 7-2 : Drum Programmer Action

 

START, A+, B+, B-, C+, C-, D+, A-, $\begin{bmatrix} E+ \\ F+ \end{bmatrix}$, F-, F+, F-, F+, $\begin{bmatrix} D- \\ E- \\ F- \end{bmatrix}$

Step	Desired Event	Signal to Advance	Switches									
			Connected to									
			A+	B+	C+	D+	D-	E+	E-	F+	F-	Motor
1	/	Start										
2	A+	a2	X									
3	B+	b2	X	X								
4	B-	b1	X									
5	C+	c2	X		X							
6	C-	c1	X									
7	D+	d2	X			X						
8	A-	a1										
9	E+ F+	e2 f2						X		X		
10	F-	f1									X	
11	F+	f2								X		
12	F-	f1									X	
13	F+	f2								X		
14	D- E- F-	d1 e1 f1					X		X		X	
15-24	Go Home	/										X

Fig. 7-3 : Drum Programmer Solution

7-3

MATRIX BOARDS

 


Fig. 7-4 : Boards

 


Fig. 7-5 : Matrix Board

PROGRAMMABLE COUNTERS (SEQUENCERS)

 


Fig. 7-6 : Schematic Representation of Programmable Counter

 


Fig. 7-7 : Programmable Counter With Single-Cycle START mode

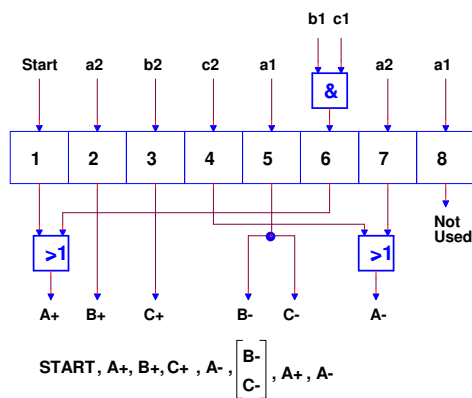


Fig. 7-8 : Programmable Counter Circuit for a Sequence, Implementing Actuating Valves Without Return Springs (1/n)

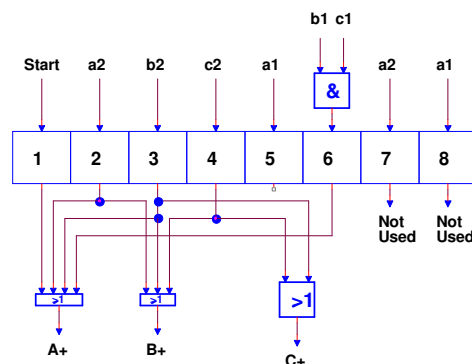


Fig. 7-9 : Programmable Counter Circuit for Sequence of Fig 7-8, While Actuating Valves Have Return Springs (1/n)

7-4

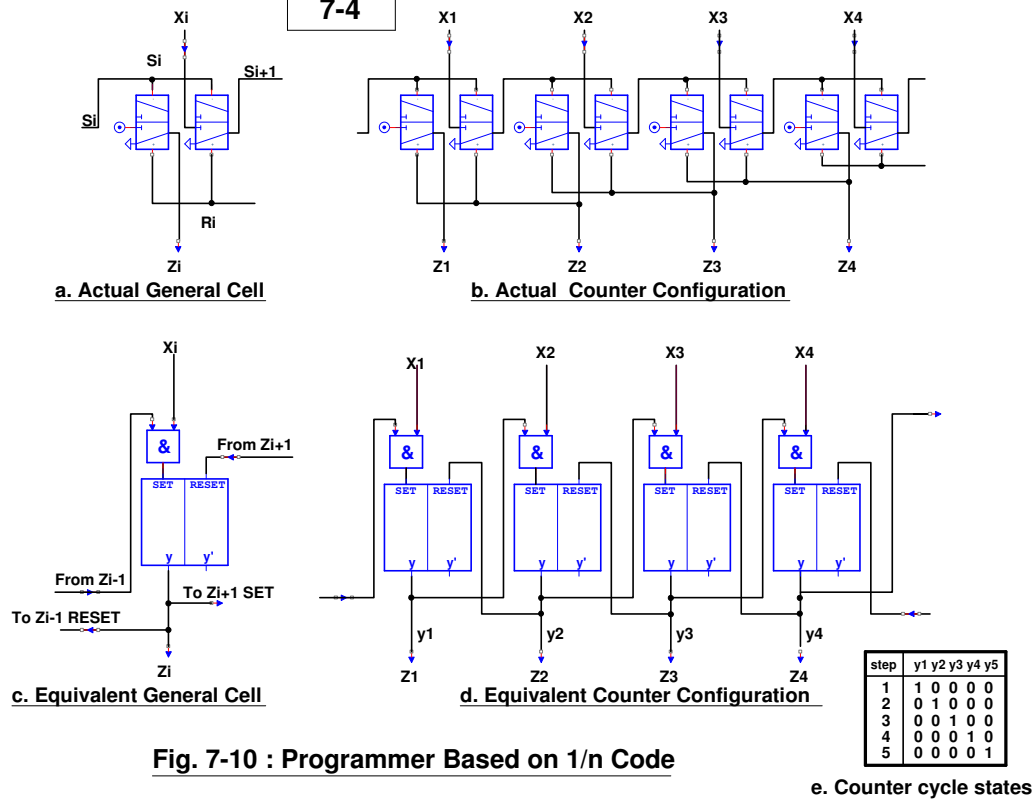


Fig. 7-10 : Programmer Based on 1/n Code

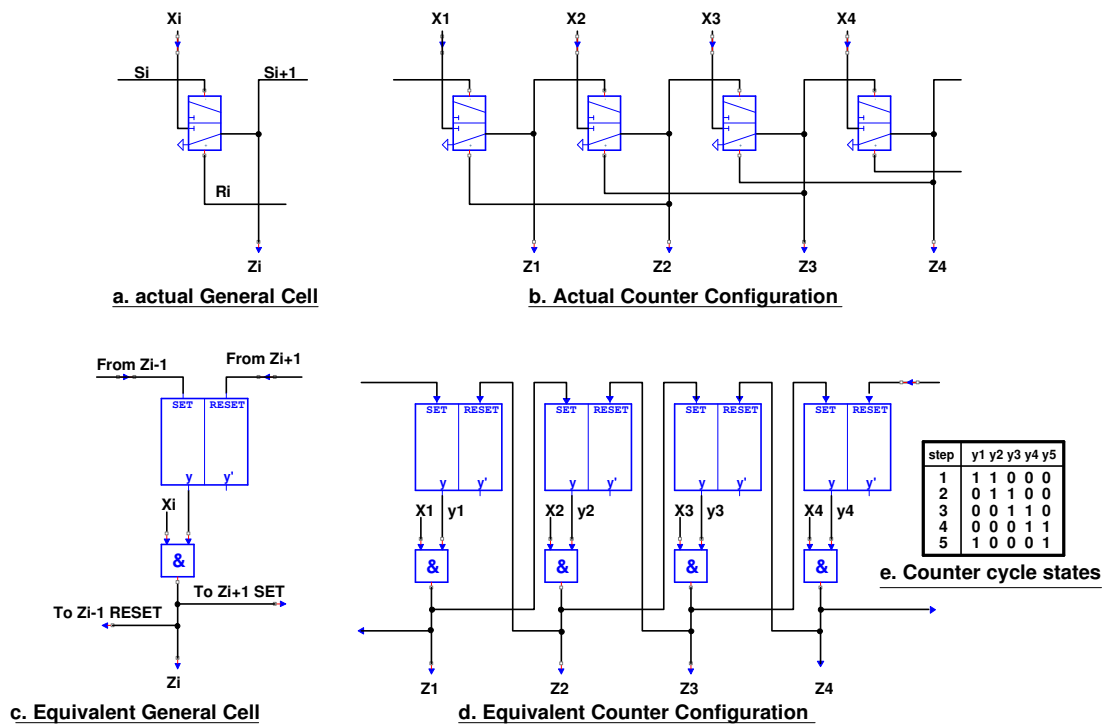


Fig. 7-11 : Programmer Based on 2/n Code

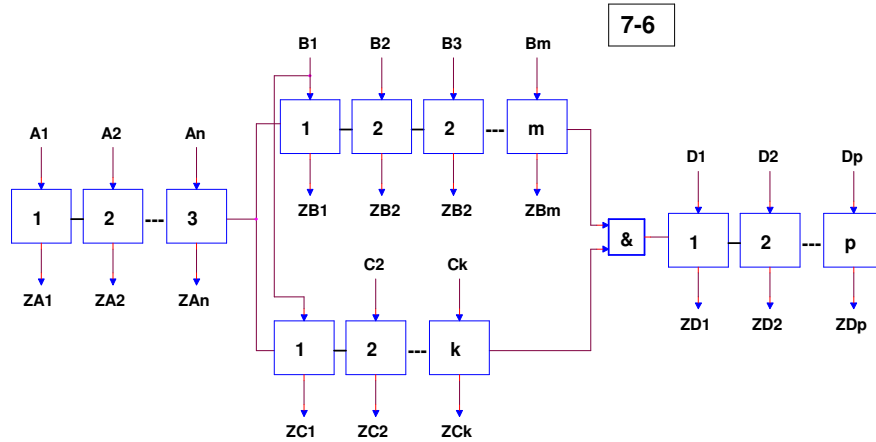


Fig. 7-15 : 1/n Programmer for Two Simultaneous Parallel Paths

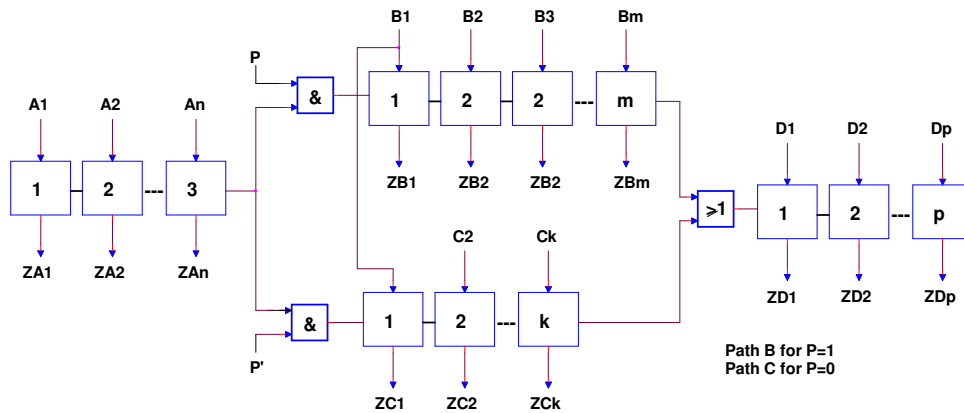


Fig. 7-16 : 1/n Programmer for Two Alternative Parallel Paths (Parallel)

 


Fig. 7-17 : 1/n Programmer for Program With Skip Steps Option

 


Fig. 7-18 : 1/n Programmer for Program With Repeated Steps Option

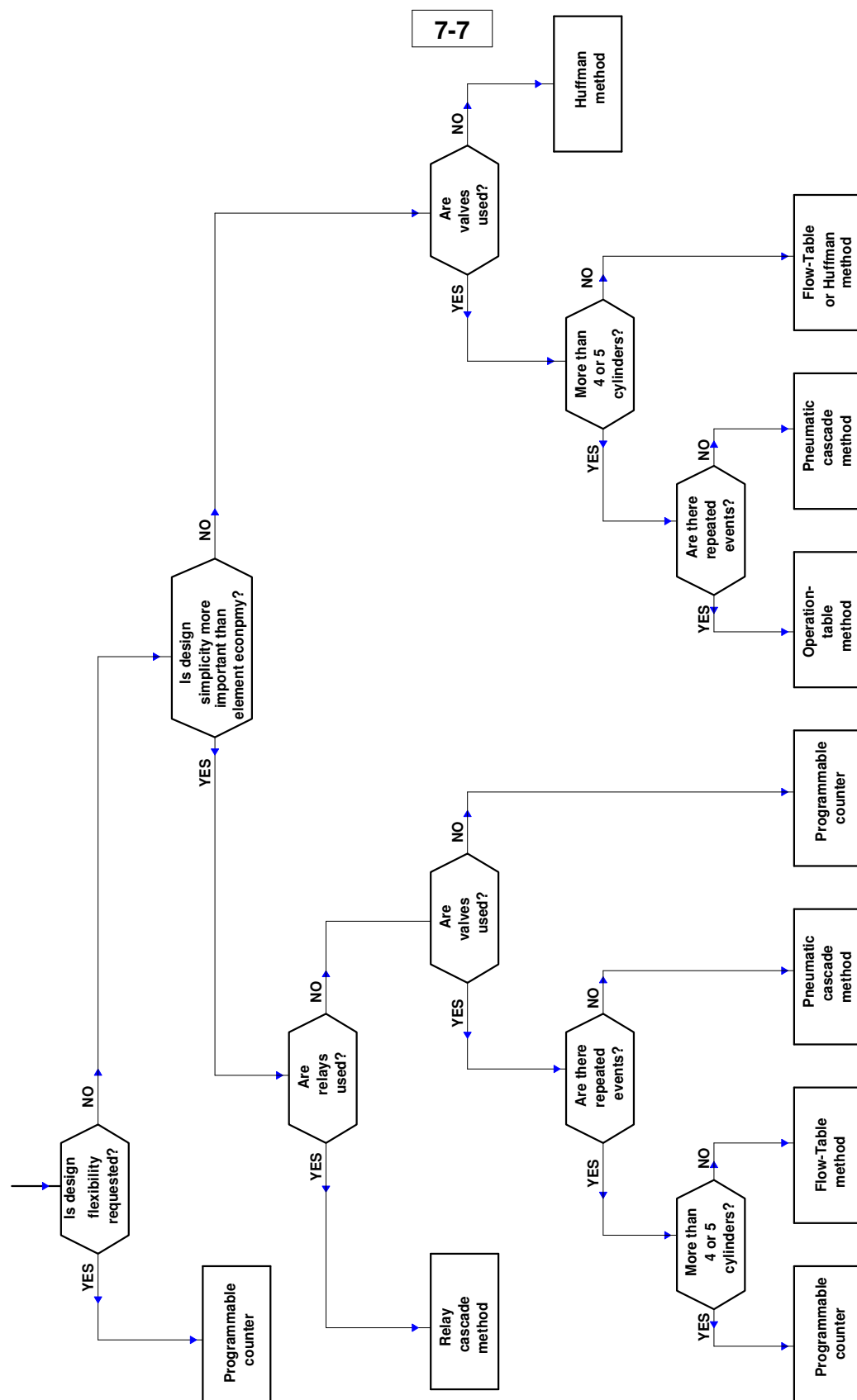


Fig. 7-19 : Flow Chart for Selecting Sequence-Control System Design Method

CHAPTER 8

MISCELLANEOUS SWITCHING ELEMENTS AND SYSTEMS

Timers Modes

Timers Construction

Pulse Shapers

Flip-Flop Types

Up/Down Counters

Shift Registers Implementation

Schmitt Trigger

Binary Codes

Error Detection

Encoders

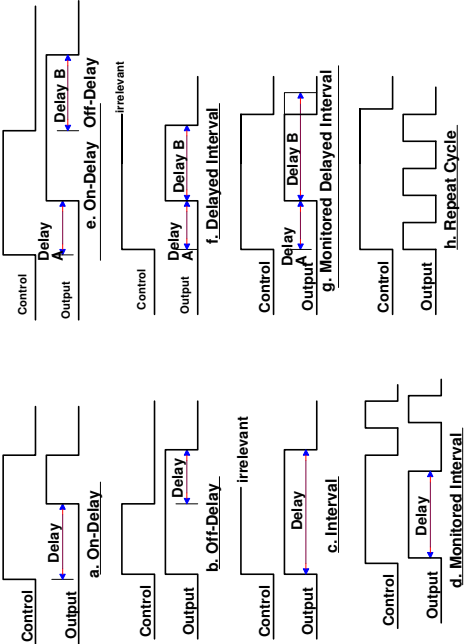


Fig. 8-1 : Sequence Chart of Common Timer Modes

 


Fig. 8-5 : Pneumatic "On-Delay" Timer Using Bias Pressure

 


Fig. 8-6 : Implement "On-Delay" Timer for Automatic Cylinder Retraction (Interval Delay)

 


Fig. 8-7 : Sequence Chart for a Pulse Shaper (Monostable, One-Shot)

 


Fig. 8-8 : Relay Pulse Shaper

 


Fig. 8-9 : Pneumatic Pulse Shaper

 


Fig. 8-2 : Pneumatic "On-Delay" Timer

 


Fig. 8-3 : Pneumatic "Off-Delay" Timer

 


Fig. 8-4 : Pneumatic "On-Delay Off-Delay" Timer

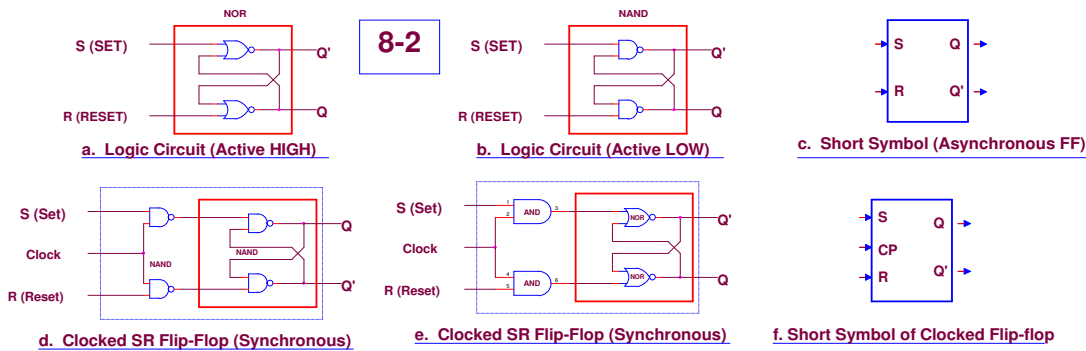


Fig. 8-10 : Basic Set-Reset Flip-Flop (SR)

 


Fig. 8-11 : Toggle Flip-Flop (T)

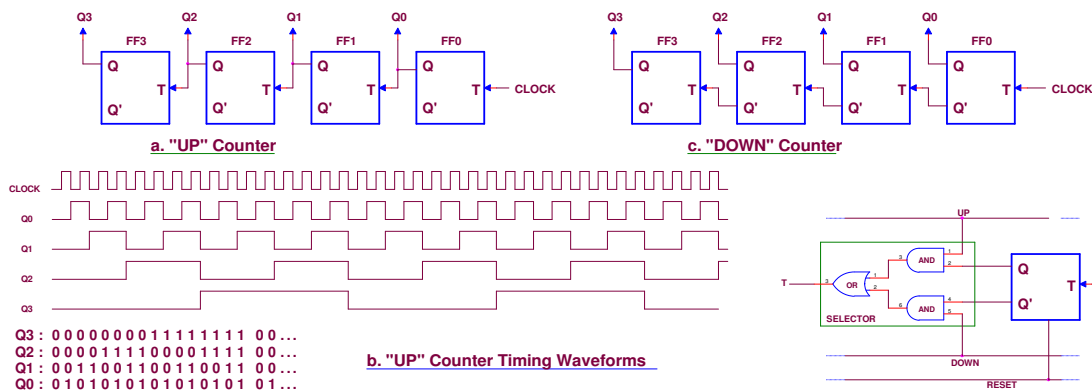


Fig. 8-12 : T Flip-Flop Implementation - Counters
(Flip-Flops are Triggered on High-to-Low Transition at T)

d. "UP/DOWN" Selector


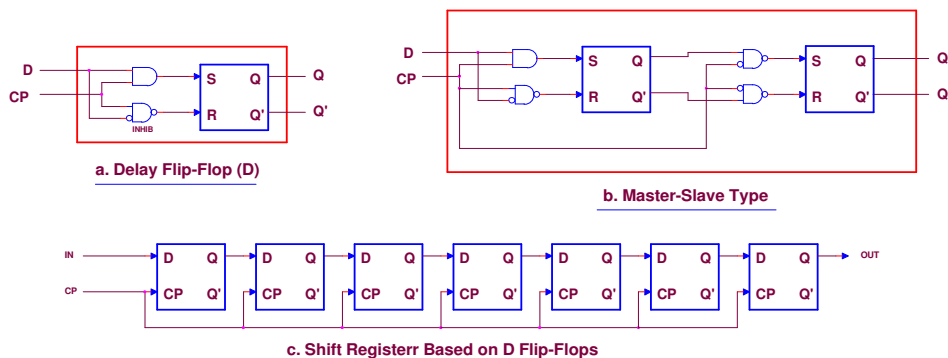


Fig. 8-13 : D Flip-Flop Implementation - Shift Register

8-3

 

a. "UP" Counter


 
 
 
 
 


Fig. 8-14 : Up-Counter Hardware Sequence

8-4

 

c. "DOWN" Counter

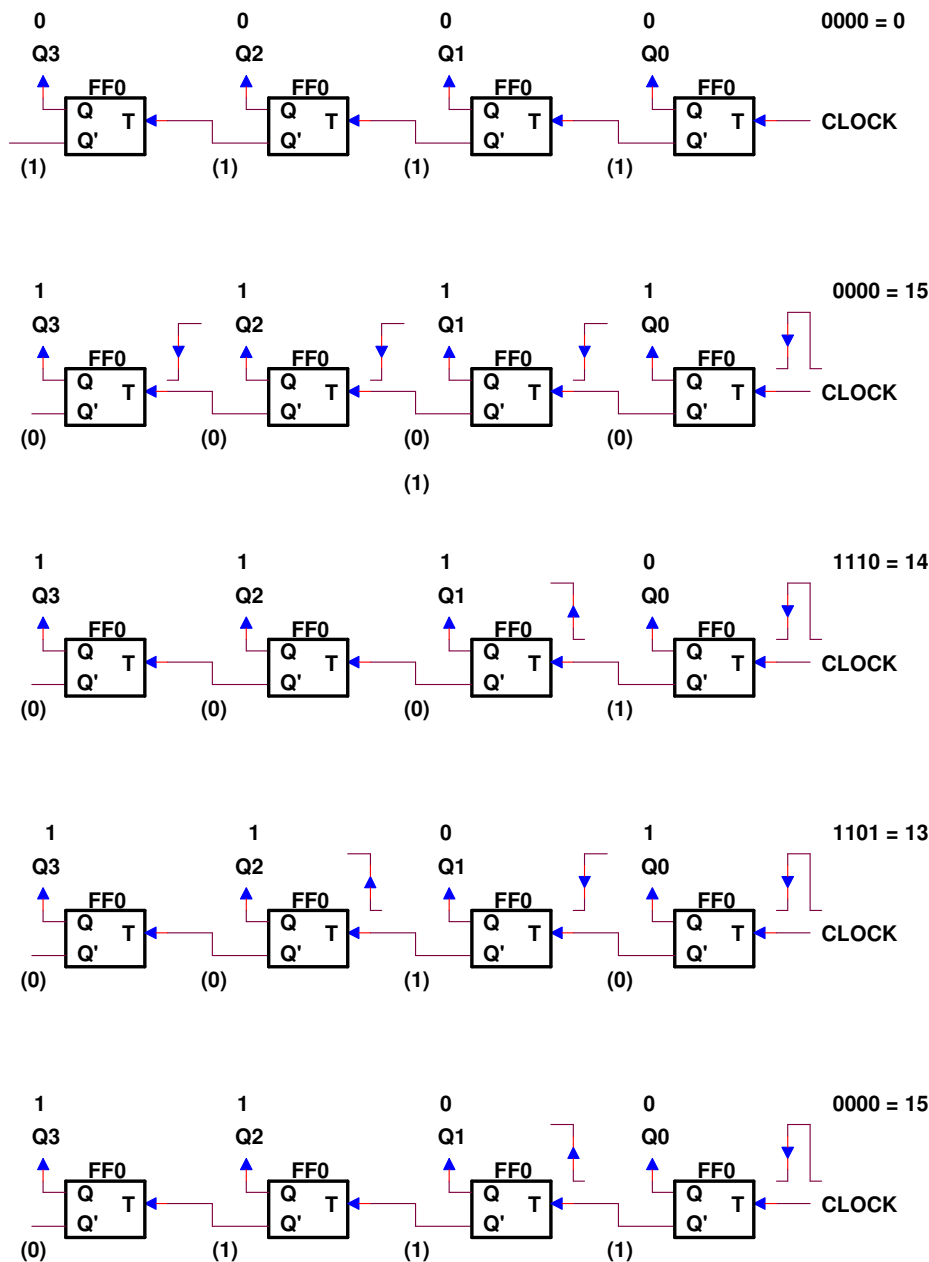


Fig. 8-15 : Down-Counter Hardware Sequence

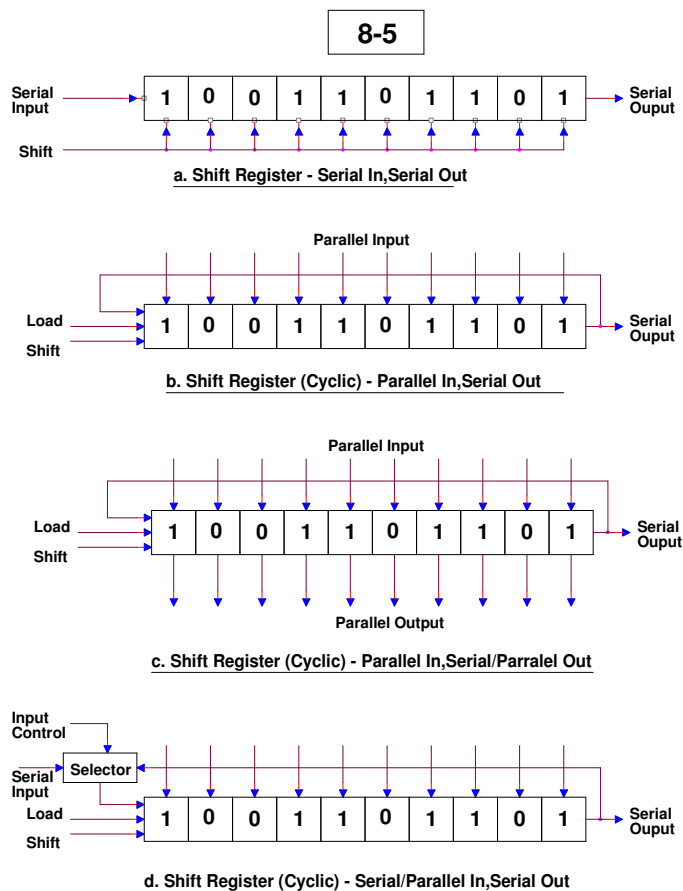


Fig. 8-16 : 10 Stages Shift Registers


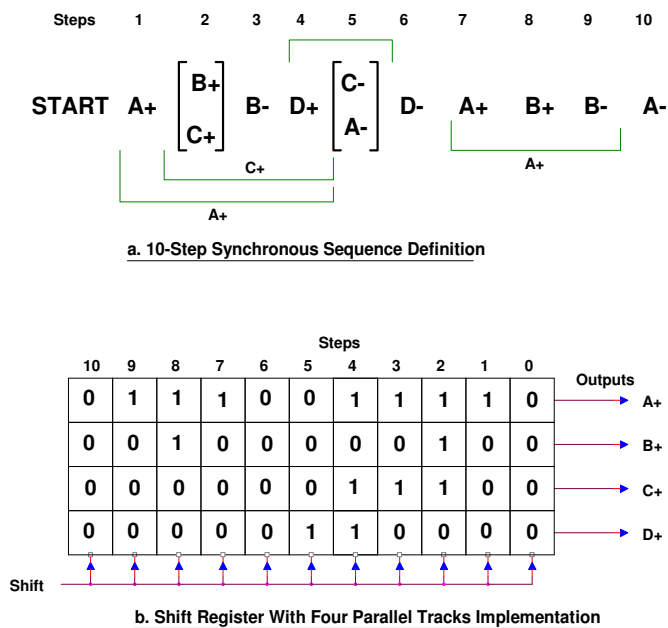


Fig. 8-17 : Implementation of Multi Track Shift Register for Operating Synchronous Sequence


8-6

 

a. Typical Gate I/O




b. Correct Input Signal

 


c. Noisy Input Signal

Fig. 8-18 : Response of Standard Gate

 


a. Hysteresis I/O Graph

 


b. Typical Response

Fig. 8-19: Schmitt-Trigger Response

 

a. Electronic Schmitt Gate

 

b. Response of Schmitt Trigger Gate

Fig. 8-20: Standard/Schmitt Response to Fuzzy Waveform

8-7

Decimal Value	Natural Binary Code	Reflected Cyclic Code
0	0 0 0 0	0 0 0 0
1	0 0 0 1	0 0 0 1
2	0 0 1 0	0 0 1 1
3	0 0 1 1	0 0 1 0
4	0 1 0 0	0 1 1 0
5	0 1 0 1	0 1 1 1
6	0 1 1 0	0 1 0 1
7	0 1 1 1	0 1 0 0
8	1 0 0 0	1 1 0 0
9	1 0 0 1	1 1 0 1
10	1 0 1 0	1 1 1 1
11	1 0 1 1	1 1 1 0
12	1 1 0 0	1 0 1 0
13	1 1 0 1	1 0 1 1
14	1 1 1 0	1 0 0 1
15	1 1 1 1	1 0 0 0

Fig. 8-21: Comparison Between Natural-Binary and Reflected-Cyclic Code

 


Fig. 8-22: Use of Karnaugh Map to Obtain Cyclic Codes

1	1	1	1
1	1	1	0
1	1	0	0
1	1	0	1
1	0	0	1
1	0	0	0
1	0	1	0
1	0	1	1
0	0	1	1
0	0	1	0
0	0	0	0
0	0	0	1
0	1	0	1
0	1	0	0
1	0	1	1
1	0	1	1
0	0	1	1
0	0	1	1

Fig. 8-23: Reflected Cyclic Code for 6 Numbers

Fig. 8-24: Construction of "Reflected" Cyclic Code

8-8

Weight Number	8	4	2	1
0	0	0	0	0
1	0	0	0	1
2	0	0	1	0
3	0	0	1	1
4	0	1	0	0
5	0	1	0	1
6	0	1	1	0
7	0	1	1	1
8	1	0	0	0
9	1	0	0	1
10	1	0	1	0
11	1	0	1	1
12	1	1	0	0
13	1	1	0	1
14	1	1	1	0
15	1	1	1	1

a. Natural Code
(No Parity)

P = Parity Bit

Weight Number	8	4	2	1	P
0	0	0	0	0	0
1	0	0	0	1	1
2	0	0	1	0	1
3	0	0	1	1	0
4	0	1	0	0	1
5	0	1	0	1	0
6	0	1	1	0	0
7	0	1	1	1	1
8	1	0	0	0	1
9	1	0	0	1	0
10	1	0	1	0	0
11	1	0	1	1	1
12	1	1	0	0	0
13	1	1	0	1	1
14	1	1	1	0	1
15	1	1	1	1	0

b. Natural Code With Binary Parity Bit
(Even Parity)

Fig. 8-25: Truth Tables for Natural Code

Weight Number	8	4	2	1	P
0	0	0	0	0	0
1	0	0	0	1	1
2	0	0	1	0	1
3	0	0	1	1	0
4	0	1	0	0	1
5	0	1	0	1	0
6	0	1	1	0	0
7	0	1	1	1	1
8	1	0	0	0	1
9	1	0	0	1	0


a. Weighted BCD Code

Weight Number	7	4	2	1	P
0	1	1	0	0	0
1	0	0	0	1	1
2	0	0	1	0	1
3	0	0	1	1	0
4	0	1	0	0	1
5	0	1	0	1	0
6	0	1	1	0	0
7	1	0	0	0	1
8	1	0	0	1	0
9	1	0	1	0	0

b. 2-out-of-5 BCD Code

Fig. 8-26: Truth Tables for BCD Code
(With Even Parity bit)

8-9

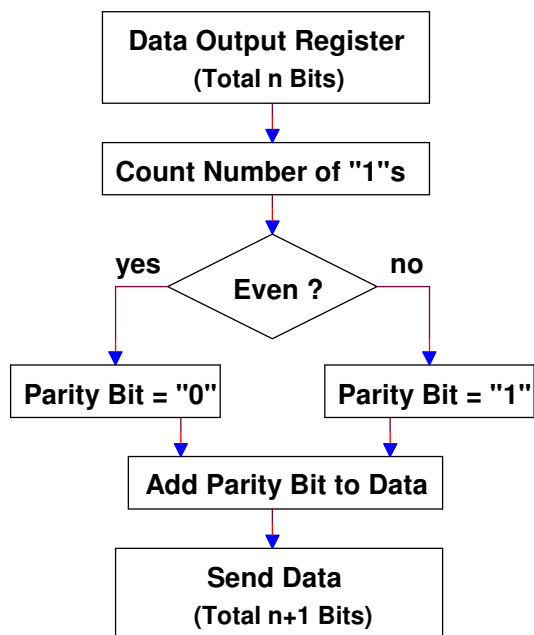

Error Detection Not Available

a. Natural Code

Detect ODD numbers of Errors

b. Single Parity Bit



Correct Single Error &
Detect 2 Errors

c. Multiple Parity Bits

Fig 8-27 : Common Modes

Fig 8-28: Parity Check Process

8-10

  

100 E WRONG
110 G OK
101 F OK
111 H WRONG



c. Sections Border Problem

b. Encoder Photo-Cells

a. Encoder Plate

Fig. 8-29: Binary 8-Sections Encoder

Absolute Coordinates

  

110 G OK
100 F OK



c. Border Problem Solved

b. Encoder Photo-Cells

a. Encoder Plate

Fig. 8-30: Typical 8-Sections Encoder

Absolute Coordinates

  

c. Incremental Encoder Output

b. Encoder Photo-Cells

a. Encoder Plate

No Sense for Direction

Fig. 8-31: Single Output Incremental Encoder

8-11

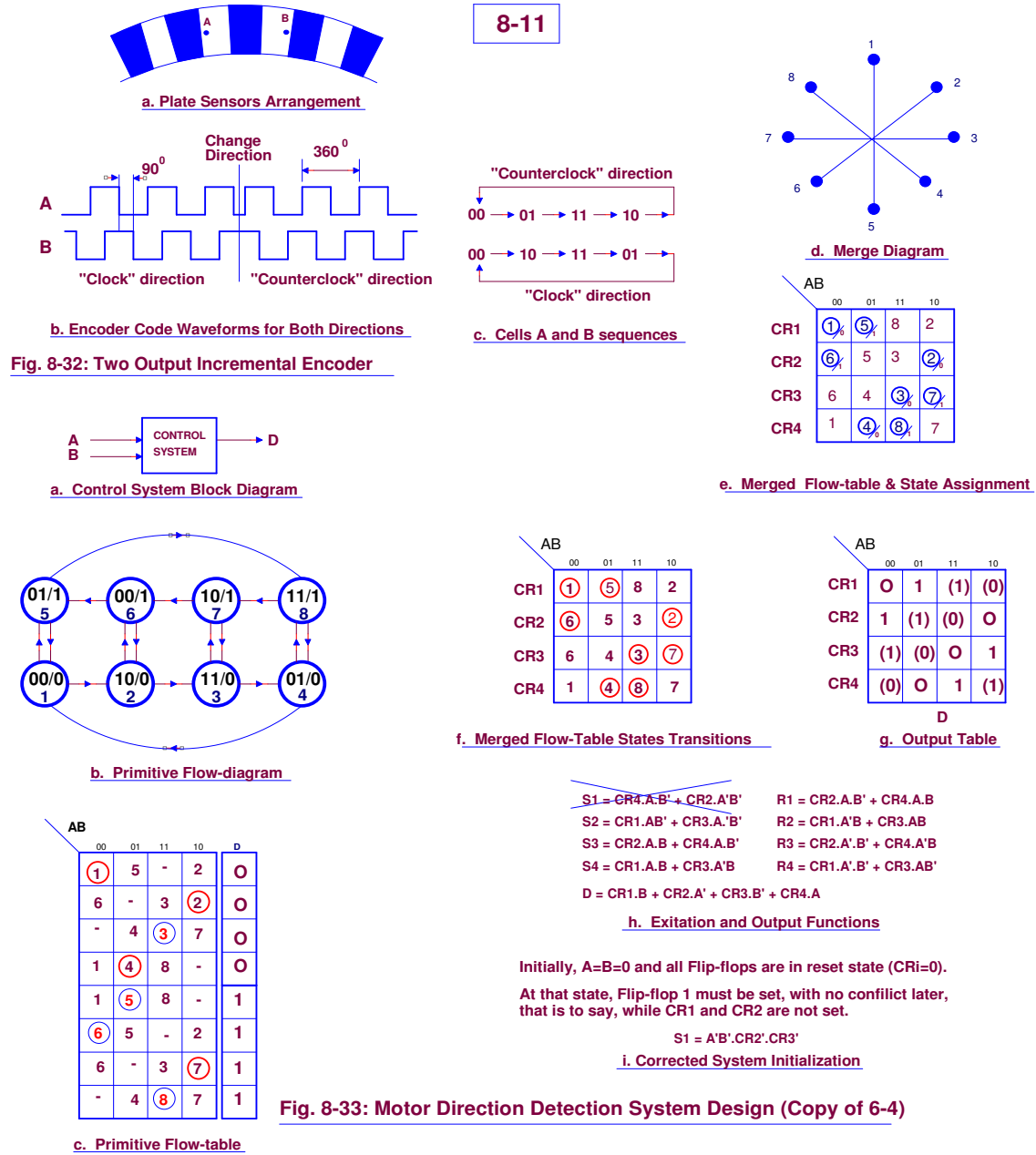


Fig. 8-33: Motor Direction Detection System Design (Copy of 6-4)

 


Fig. 8-34: Simplified Block Diagram of a Closed Loop NC System (One Control Axis)



Fig. 8-35: Block Diagram of an Open-Loop NC System (One Control Axis)

CHAPTER 9

ITERATIVE SYSTEMS

Iterative Binary Adder
Iterative Design Samples
Binary Numbers Comparator
Cyclic Codes Converters

9-1

X1	X0	Y1	Y0	Z2	Z1	Z0
0	0	0	0	0	0	0
0	0	0	1	0	0	1
0	0	1	0	0	1	0
0	0	1	1	0	1	1
0	1	0	0	0	0	1
0	1	0	1	0	1	0
0	1	1	0	0	1	1
0	1	1	1	1	0	0
1	0	0	0	0	1	0
1	0	0	1	0	1	1
1	0	1	0	1	0	0
1	0	1	1	1	0	1
1	1	0	0	0	1	1
1	1	0	1	1	0	0
1	1	1	0	1	0	1
1	1	1	1	1	1	0

a. Truth Table

$$Z2 = X1.Y1 + X1.X0.Y0 + X0.Y1.Y0$$

$$Z1 = X1'X0.Y1'Y0 + X1.X0.Y1.Y0 + X1.Y1'Y0' + X1.X0'Y1' + X1'Y1.Y0' + X1'X0'Y1$$

$$Z0 = X0.Y0' + X0'Y0$$

b. Sum Output Minimized Functions

- * 3-Bit Numbers Adder requires 6-Variable Map
- * 4-Bit Numbers Adder requires 8-Variable Map
- * 32-Bit Numbers Adder requires 64-Variable Map
- * Karnaugh Map Methode Is Limited to 4-Bit Numbers

c. Karnaugh Map Methose Limitation

Fig. 9-1 : Adder for 2-Bit Numbers


 


Fig. 9-2 : Iterative Adder Block Diagram

 


a. General Cell (FA) Flow Chart

Ci	Xi	Yi	Ci+1	Si
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

$$Si = (Xi) \text{ xor } (Yi) \text{ xor } (Ci)$$

$$Ci+1 = Xi.Yi + Ci (Xi + Yi)$$

b. FA Truth Table

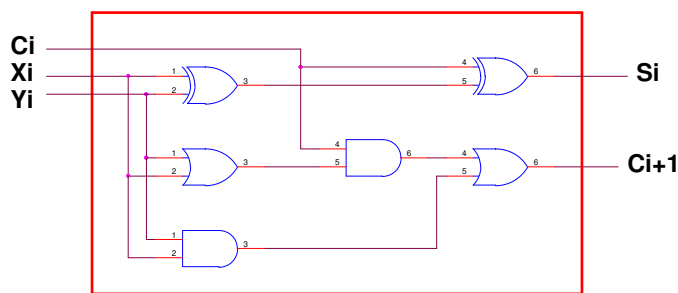

c. FA Logic Circuit

Fig. 9-3 : Iterative Binary Adder Design

9-2


DESIGN OF A PARITY CHECKER

Checker detects if number of "1" in a binary vector, is odd or even.


It produces a single output line P, where :

P=1 denotes odd parity
P=0 denotes even parity


a. Requirements Definition

 

b. Simplified Block Diagram

 

c. Iterative Block Diagram

 


d. General Cell Flow Chart

Pi-1	Xi	Pi
0	0	0
0	1	1
1	0	1
1	1	0

e. General Cell Truth Table

$$P_i = P_{i-1}.X_i' + P_{i-1}'.X_i = P_{i-1} \text{ xor } X_i$$

f. General Cell Function

 

g. General Cell Logic Circuit

Fig. 9-4: Iterative Parity Checker


DESIGN OF 2-OUT-OF-5 CHECKER

A specific code consists of vectors that contain exactly two "1"s, and all other bits are "0".


(11000000, 00101000, 01000001 etc).

Design a circuit that checks vectors and announces Z=1 when detected vector been found valid.


a. Requirements Definition

 

b. Simplified Block Diagram

 

c. General Cell Flow Chart

 

d. Iterative Block Diagram

Ai-1	Bi-1	Ci-1	Di-1	Xi	Ai	Bi	Ci	Di
1	-	-	-	0	1	0	0	0
1	-	-	-	1	0	1	0	0
-	1	-	-	0	0	1	0	0
-	1	-	-	1	0	0	1	0
-	-	1	-	0	0	0	1	0
-	-	1	-	1	0	0	0	1
-	-	-	1	0	0	0	0	1
-	-	-	1	1	0	0	0	1

e. General Cell Truth Table

$$\begin{aligned} A_i &= A_{i-1}.X_i' \\ B_i &= A_{i-1}.X_i + B_{i-1}.X_i' \\ C_i &= B_{i-1}.X_i + C_{i-1}.X_i' \\ D_i &= C_{i-1}.X_i + D_{i-1} \end{aligned}$$

f. General Cell Function

Fig. 9-5 : Iterative 2-Out-of-n Checker

DESIGN OF A BINARY COMPARATOR

Comparator compares 2 binary numbers X,Y (of equal length), and produces 3 output signals:

Line A : A=1 if $X>Y$

Line B : B=1 if $X=Y$


Line C : C=1 if $X<Y$

Design refers to positive numbers of $n+1$ bits, where n may vary according to case.


a. Requirements Definition



b. Simplified Block Diagram

 

c. Iterative Block Diagram

 

d. General Cell Flow Chart

$$A_i = A_{i-1} + B_{i-1} \cdot X_i \cdot Y_i'$$


$$B_i = B_{i-1}(X_i \cdot Y_i + X_i' \cdot Y_i') = B_{i-1}(X_i \text{ xor } Y_i)$$

$$C_i = C_{i-1} + B_{i-1} \cdot X_i \cdot Y_i$$

f. General Cell Functions

A_{i-1}	B_{i-1}	C_{i-1}	X_i	Y_i	A_i	B_i	C_i
1	0	0	-	-	1	0	0
0	0	1	-	-	0	0	1
0	1	0	0	0	0	1	0
0	1	0	0	1	0	0	1
0	1	0	1	0	1	0	0
0	1	0	1	1	0	1	0

e. General Cell Truth Table

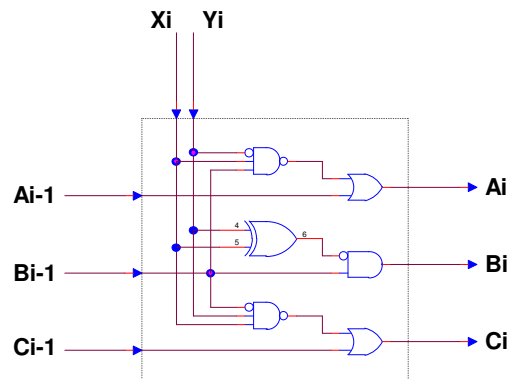

g. General Cell Logic Circuit

Fig. 9-6 : Iterative Binary Numbers Comparator

Decimal Value	Natural Binary Code	Reflected Cyclic Code
0	0 0 0 0	0 0 0 0
1	0 0 0 1	0 0 0 1
2	0 0 1 0	0 0 1 1
3	0 0 1 1	0 0 1 0
4	0 1 0 0	0 1 1 0
5	0 1 0 1	0 1 1 1
6	0 1 1 0	0 1 0 1
7	0 1 1 1	0 1 0 0
8	1 0 0 0	1 1 0 0
9	1 0 0 1	1 1 0 1
10	1 0 1 0	1 1 1 1
11	1 0 1 1	1 1 1 0
12	1 1 0 0	1 0 1 0
13	1 1 0 1	1 0 1 1
14	1 1 1 0	1 0 0 1
15	1 1 1 1	1 0 0 0

Fig. 9-7 : Comparison Between Natural-Binary and Reflected-Cyclic Code

 


Fig. 9-8 : Iterative Circuit for Translating Natural-Binary into Reflected-Cyclic Code

 


Fig. 9-9 : Iterative Circuit for Translating Reflected-Cyclic into Natural-Binary Code

N(i)	N(i-1)	C(i-1)
0	0	0
0	1	1
1	0	1
1	1	0

$$C(i-1) = N(i) \oplus N(i-1)$$

$$N(i-1) = N(i) \oplus C(i-1)$$

Fig. 9-10 : Truth Table for Translating Natural-Binary into Reflected-Cyclic Code

CHAPTER 10


MULTI VARIABLES KARNAUGHT MAPS

5-Variables Map

6-Variables Map

7-Variables Map

8-Variables Map

 

a. 3-D Representation

b. Flat Representation

Fig. 10-1 : Three-Dimensional Five-Variable Karnaugh Map, and Its Development

10-1


 


Fig. 10-2 : Optional Construction of Five-Variable Karnaugh Map (Not Recommended)

 

b. Karnaugh Map

$$T = A'B'C'D' + A'BDE' + A'B'CDE' + AB'C'D' + A'BC'DE + ABCDE + ABCD'E$$


with impossible conditions : $A'B'CD=1$ $ACDE=1$

a. Original Function

$$T = B'C'D' + A'BC'D + CDE' + ABCE$$

c. Simplified Function

Fig. 10-3 : 5-Variable Minimization Exercise (With Solution)

 

b. Karnaugh Map


$$T = A'B'C'E' + A'B'CD' + ABC'DE' + AB'C'E' + AB'CD'E' + B'C'D'E' + A'B'C'DE + CD'E$$

a. Original Function


T =

c. Simplified Function

Fig. 10-4 : 5-Variable Minimization Exercise (Without Solution)

 


a. 3-D Representation

 

b. Flat Representation

Fig. 10-5 : Three-Dimensional six-Variable Karnaugh Map, and Its Development

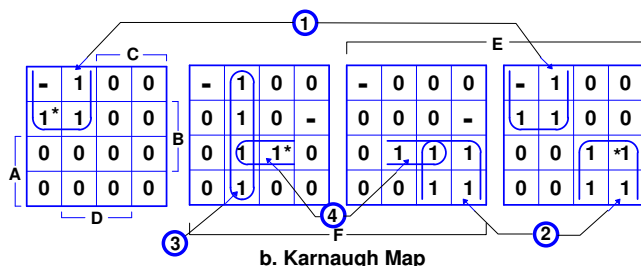

b. Karnaugh Map

$$T = A'BC'F' + AB'C'DE'F + ABDF + ACDE + ACD'E' + A'C'DE' + A'C'DEF'$$

with impossible conditions :
 $A'B'C'D=1$ $A'BCD'F=1$

a. Original Function

$$T = A'C'F' + ACE + C'DE'F + ABDF$$

c. Simplified Function

Fig. 10-6 : 6-Variable Minimization Exercise (With Solution)

10-2

 


Fig. 10-7 : Seven-Variable Karnaugh Map, and Its Development

$$T = A'C'D'G' + ABCF + B'D'FG + A'C'EF'$$

b. Simplified Function

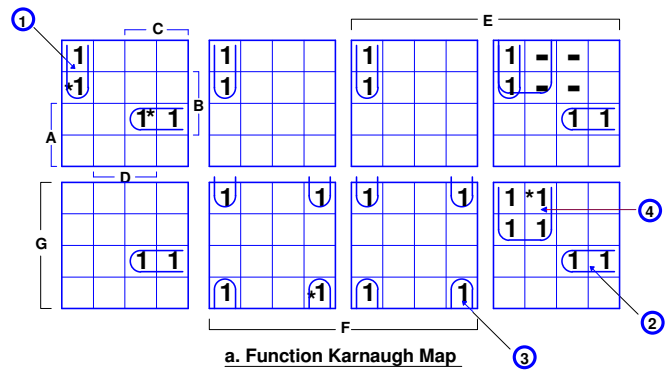


Fig. 10-8 : 7-Variable Minimization Exercise (With Solution)

 


Fig. 10-9 : Eight-Variable Karnaugh Map, and Its Development

	Number of Variables in The Function							
Size of Cell	2	3	4	5	6	7	8	
Single Square	2	3	4	5	6	7	8	
2-Square Cell	1	2	3	4	5	6	7	
4-Square Cell		1	2	3	4	5	6	
8-Square Cell			1	2	3	4	5	
16-Square Cell				1	2	3	4	
32-Square Cell					1	2	3	
64-Square Cell						1	2	
128-Square Cell							1	

Fig. 10-11 : Number of Variables Required to Define Certain Cell Address

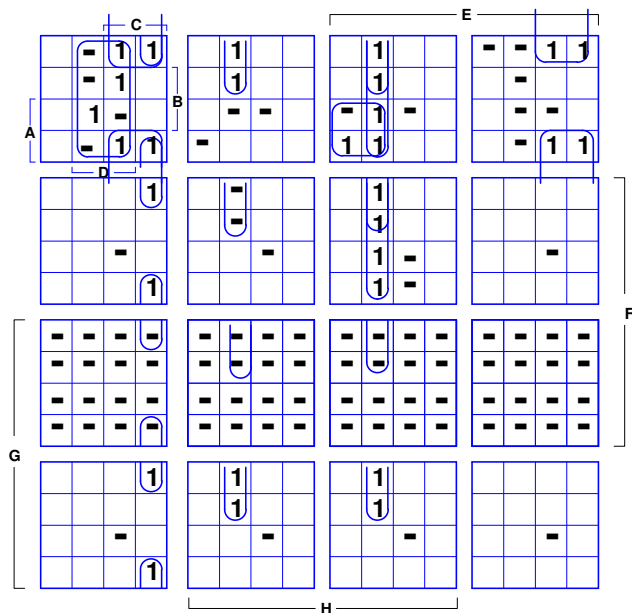


Fig. 10-10 : 8-Variable Minimization Exercise

10-3

Semi-Karnaugh Maps

T.B.D.

CHAPTER 11

PNEUMATIC FLOW-TABLE METHODE

 


Fig. 11-2 : Two Steering Valves providing 3 addresses


 


Fig. 11-3 : Three Steering Valves providing 4 addresses

 

START,A+,A-,A+,A-,A+,A-

a. Process sequence

a1	a2	A+	A-
①		1	
	②		1
③		1	
	④		1
⑤		1	
	⑥		1

b. Flow Table

a1	a2	A+	A-
y1' ① R3		1	
	y3' ② S1 R2		1
y1.y2' ③ S3 R4		1	
	y3.y4' ④ S2		1
y1.y2 ⑤ S4		1	
	y3.y4 ⑥ R1		1

c. Complete Flow Table

S1 = a2.y3' S2 = a2.y3.y4' S3 = a1.y1.y2' S4 = a1.y1.y2
R1 = a2.y3.y4 R2 = a2.y3' R3 = a1.y1' R4 = a1.y1.y2'

A+ = a1.y1'.Start+a1.y1.y2'+a1.y1.y2 = a1.y1'.Start+a1.y1
A- = a2.y3'+a2.y3.y4'+a2.y3.y4 = a2.y3'+a2.y3 = a2

d. Exitation and Output Functions

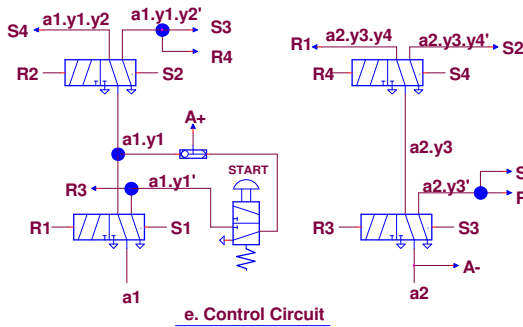


Fig. 11-4 : Pneumatic Flow-Table Design for sequences START,A+,A-,A+,A-,A+,A-

START,A+,B+,A-,B-, $\begin{bmatrix} A+ \\ B+ \end{bmatrix}$,A-,B-

a. Process sequence

a1.b1	a2.b1	a2.b2	a1.b2	A+	A-	B+	B-
y1' ①				1			
	① R2					1	
		y2' ③ R3			1		
			y3' ④ S1				1
y1 ⑤ s2				1		1	
		y2 ⑥ S3			1		
			y3 ⑦ R1				1

b. Complete Flow Table

S1 = a1.b2.y3' S2 = a1.b1.y1 S3 = a2.b2.y2
R1 = a1.b2.y3 R2 = a2.b1 R3 = a2.b2.y2'

A+ = a1.b1.y1'.Start+a1.b1.y1 = a1.b1.Start+a1.b1.y1
A- = a2.b2.y2'+a2.b2.y2 = a2.b2
B+ = a2.b1+a1.b1.y1
B- = a1.b2.y3'+a1.b2.y3 = a1.b2

c. Exitation and Output Functions

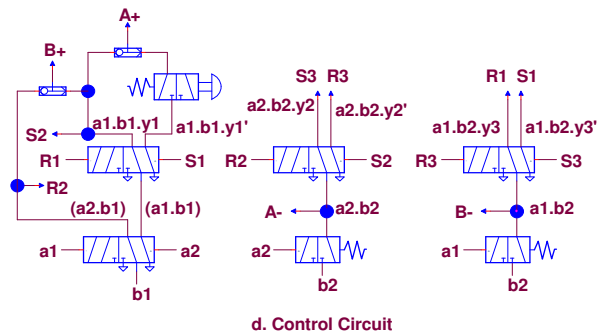


Fig. 11-5 : Pneumatic Flow-Table Design for Sequence START,A+,B+,A-,B-, $\begin{bmatrix} A+ \\ B+ \end{bmatrix}$,A-,B-


11-2

START,A+,B+,B-,C+,B+,B-,C-,A-

a. Process sequence

a1.b1.c1 (a1)	a2.b1.c1	a2.b2.c1 (b2.c1)	a2.b1.c2 (b1.c2)	a2.b2.c2 (b2.c2)	A+ A-	B+ B-	C+ C-
① R1					1		
	y1' ②					1	
		③ S1 R2					1
	y1.y2' ④ R3						1
			y3' ⑤			1	
				⑥ S3			1
			y3 ⑦ S2				1
	y1.y2 ⑧				1		

b. Complete Flow Table

 


c. Simplifying Input Map

a1 b1 c1 → a1
a2 b2 c1 → b2 a1
a2 b1 c2 → b1 c2
a2 b2 c2 → b2 c2

S1 = b2.c1 S2 = b1.c2.y3 S3 = b2.c2
R1 = a1 R2 = b2.c1 R3 = a2.b1.c1.y1.y2'
A+ = a1.START A- = a2.b1.c1.y1.y2
B+ = a2.b1.c1.y1'+b1.c2.y3' B- = b2.c1+b2.c2 = (b2)
C+ = a2.b1.c1.y1.y2' C- = b1.c2.y3

d. Exitation and Output Functions

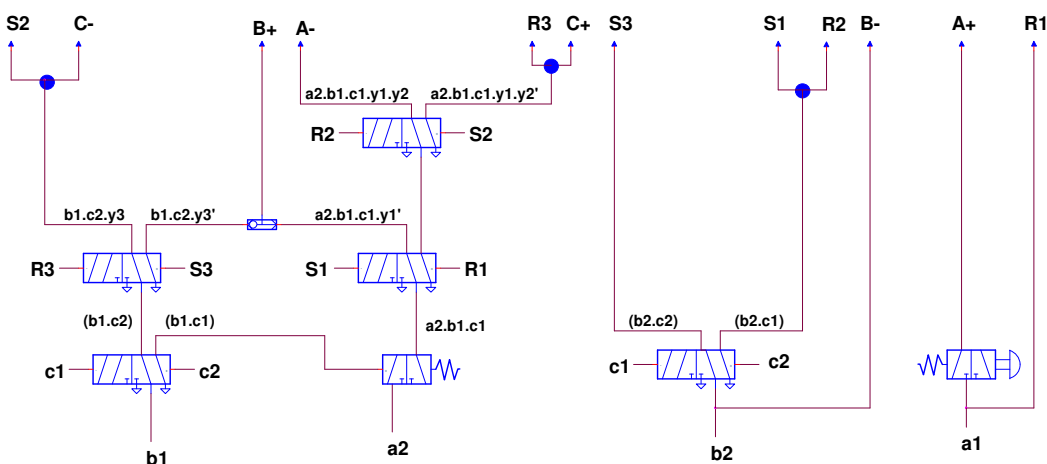

e. Control Circuit

Fig. 11-6 : Pneumatic Flow-Table Design for Sequence START,A+,B+,B-,C+,B+,B-,C-,A-

CHAPTER 12

MOTION ACTUATORS

Linear and Angular Motion

Electrical Linear Actuators

Electrical Rotary Actuators

Fluid-power Linear Actuators

Fluid-power Rotating Actuators

Boolean Functions Standard Formats

12-1

 


Fig. 11-3 : Eight types of
Pneumatic rotary actuators

Chapter 1 : MOTION ACTUATORS

 


Fig. 11-2 : Force-stroke curve for
Typical 1/2" diameter solenoid

 


Fig. 11-1 : Solenoid

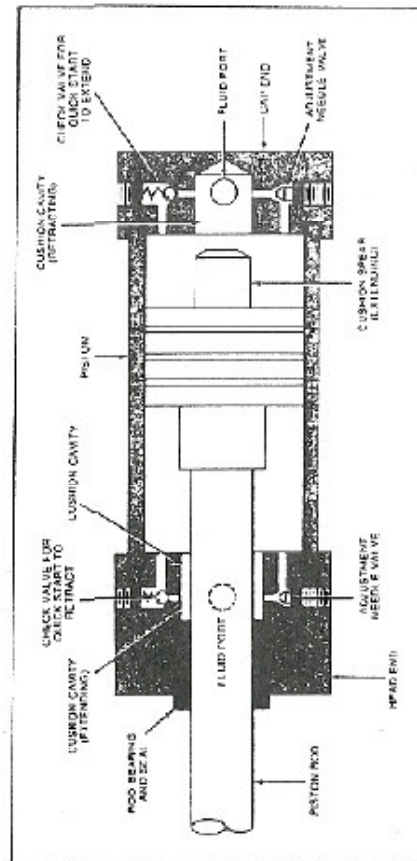


Fig. 11-4 : Pneumatic cylinder
With air cushions

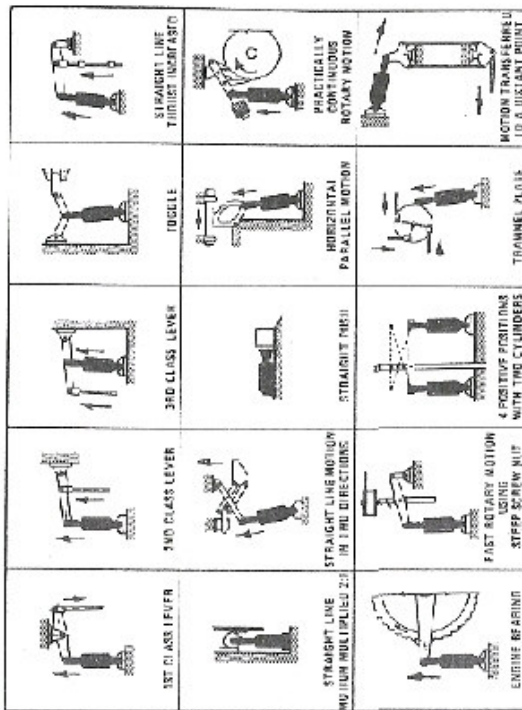


Fig. 12-6 : Fifteen ways of using cylinders

 


Fig. 12-5 : Basic cylinder types


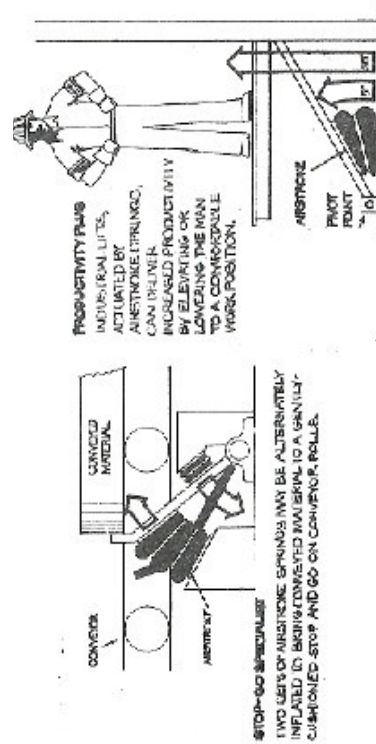


Fig. 12-7 : Two application of "airstroke"
Actuator (Firestonr)

 

**Fig. 12-8 : Eight types of
Pneumatic rotary actuators**

 


Fig. 3—Reversible vane-type air motor. To reverse direction of rotation, inlet line is moved from one port to the other.

Fig. 12-9 : Air motor

CHAPTER 13

SENSORS

Electric Position Sensors

Contacts Symbols

Photoelectric Sensors

Reed Switches

Proximity Sensors

Pressure, Flow and Level Switches

Pneumatic Limit Valves

Back-Pressure Sensors

13-1

 


Fig. 13-1 : Common actuation methods for Limit Switches
(a) Overtravel plunger
(b) Lever roller
(c) Pin Plunger
(d) Lever

 


Fig. 13-2 : Common contact arrangements

	NO (SPST)	NC (SPST)	Change over (SPDT)
Normal position (non-actuated)			
Actuated position			

Fig. 13-3 : Limit-switch symbols for different contact configurations

 


Fig. 13-4 : SPDT switch with (a) break-before-make (BBM) contacts, and (b) make-before-break (MBB) contacts

 


Fig. 13-5 : SPDT Three operating modes of photoelectric sensor –

- (a) through beam
- (b) reflection from target
- (c) retroreflection

Fig. 13-11 : Use of magnetic proximity sensor
To measure rotational velocity

 


Fig. 13-6 : Methods for actuating Reed switches


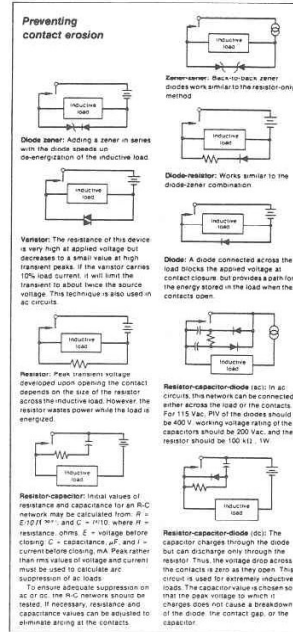


Fig. 13-8 : Arc suppression method for protecting relay & switch controls

 

Air Cylinder Controls Magnetic Reed Switch

An SPST magnetic reed switch slides in a track on an air cylinder to operate relays, solenoids, timers, and other electrical equipment. A permanent magnet attached to the piston activates the switch. Six bore sizes are available from 1 1/16 to 2 1/2 in. with strokes to 32 in.

Fig. 13-7 : Use of reed switch to sense piston position


 



Fig. 13-9 : Proximity sensor

 

With an unbroken bit, the Mark III output contacts are closed allowing regular operation.

If the bit is broken, the Mark III sensor detects the damage and signals "No Go".

 If a bent bit smashes the Mark III sensor, the machine is turned off.



With the part in proper position, the Mark III output contacts are closed allowing regular operation.

With the part in an irregular position, the Mark III sensor detects the damage and signals "No Go".

If the sensor is broken or the cable is open or shorted, the Mark III turns off the machine.

Fig. 13-10 : Proximity sensor application

 


Fig. 2-11: Use of magnetic proximity sensor to measure rotational velocity

13-3

 


Fig. 13-12 : Four basic types of pressure switches

 


Fig. 13-15 : Two flow switches (based on reed switch)

 


Fig. 13-13 : pressure switch (diagram and Step acts on a limit)

 


Fig. 13-14 : Level switch (based On reed switch)

 


Fig. 13-16 : Symbols for various sensor switches (normally-open contacts)

 


Fig. 13-17 : Sensor switch - (a) without dead band (b) With dead band (hysteresis)

 


Fig. 13-18 :

Pneumatic limit valves and their fluid-power symbols:

(a) a 3/2 valve, and (b) a 5/2 valve.
(Spool Type)

 


Fig. 13-19 :

3/2 limit valve
(Poppet Type)

13-4

 


Fig. 13-20 : Flapper-Nozzle system used as back-pressure

 


Fig. 13-21 : Back-pressure sensor with overtravel rotation

Fig. 13-21 : Back-pressure sensor with overtravel rotation


 


Fig. 13-22 : Detecting liquid level of power level using back-pressure sensor (bubble tube)

 

Fig. 13-23 : Annular back-pressure (a) output pressure P_0 low



(b) sensor P_0 high

 


Fig. 13-24 : Interruptable-jet sensor

 


Fig. 13-25 : Interruptable-jet sensor (insensitive to dirt)


 


Fig. 13-26 : Interruptable-jet sensor (with remote actuation)

 

As illustrated in Fig. 4-12 the properties of sound waves extend the usefulness of the ultrasonic-type sensor: the reflex method of sensing can detect objects on a conveyor line or a sound curtain can detect the presence of a person entering a hazardous area.

Fig. 13-27 : Ultrasonic sensor, and several applications

 


Fig. 2-28: Spring Sensor (AIR LOGIC CO.)

CHAPTER 14

FRAFCET METHODE

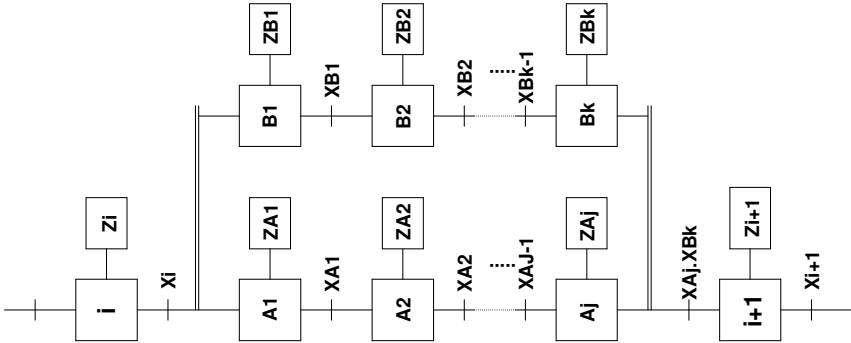


Fig. 14-3 : GRAFCET for Simultaneous Parallel Paths

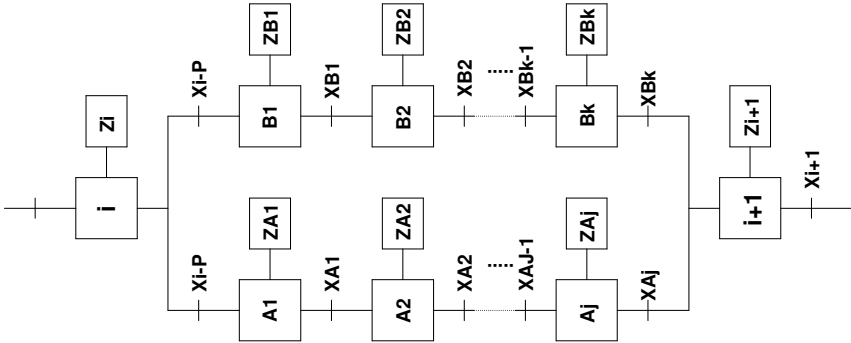


Fig. 14-2 : GRAFCET for Alternate Parallel Paths

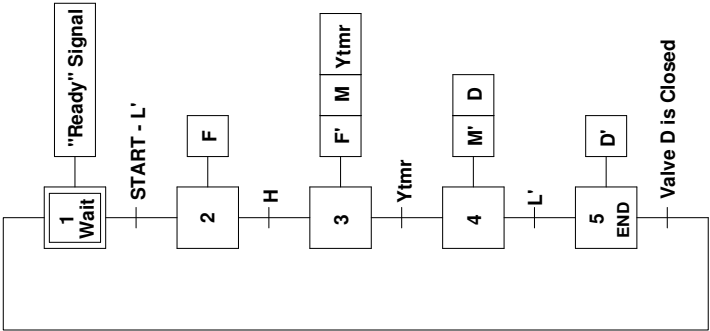


Fig. 14-1 : GRAFCET for Automated Mixing System (Fig. 5-11)

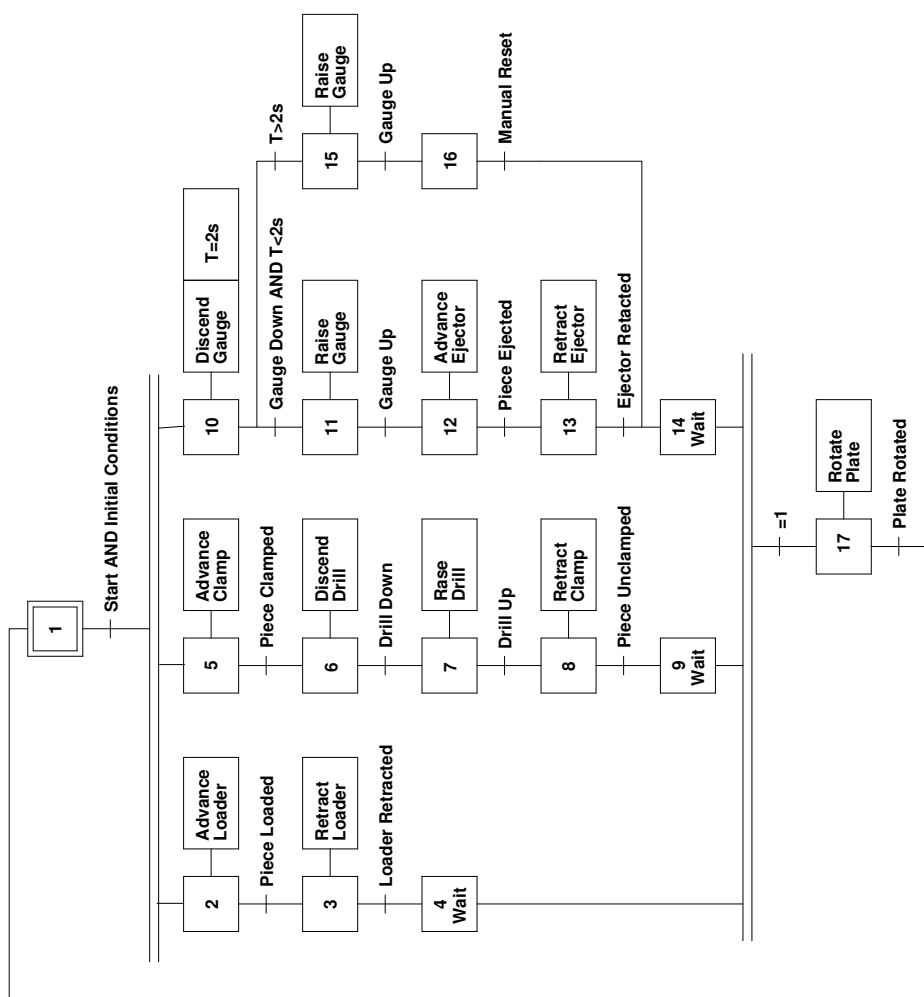


Fig. 14-4 : GRAFCET for Drilling Station
(From Telemechanique TSX T607 Manual)

