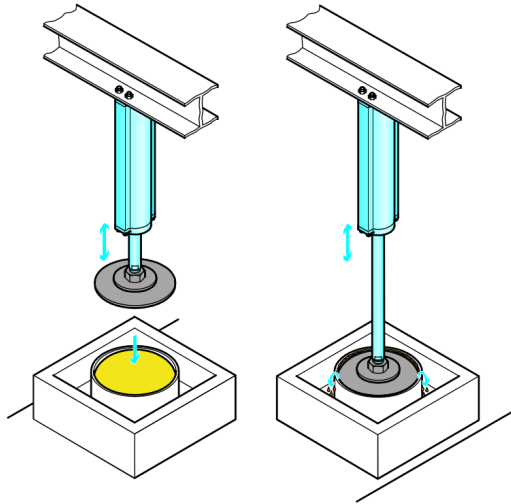


Logic control of electro-pneumatic systems

Kjartan Halvorsen


October 20, 2020

Cheese pressing example, sequence A+A-




From FESTO Didactic


They Relay

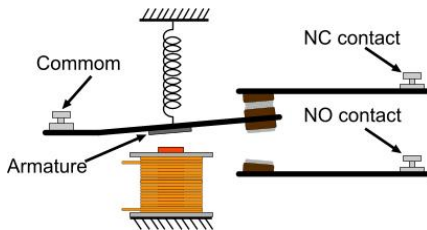

From pcbheaven.com

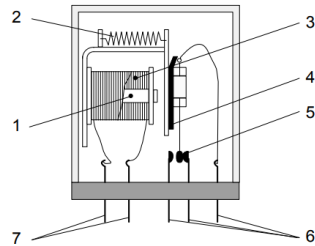

From FESTO didactic

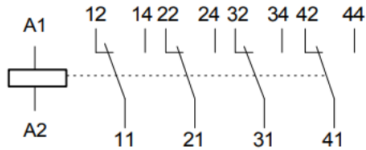

From FESTO didactic




From FESTO didactic


Other key components

Sources: FESTO didactic, electroschematics.com, automation-insights.blog


Limit switch

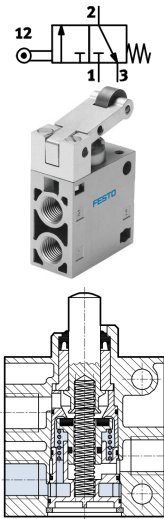

Solenoid valve

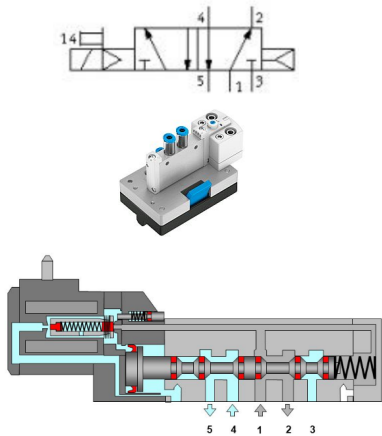


Proximity sensor

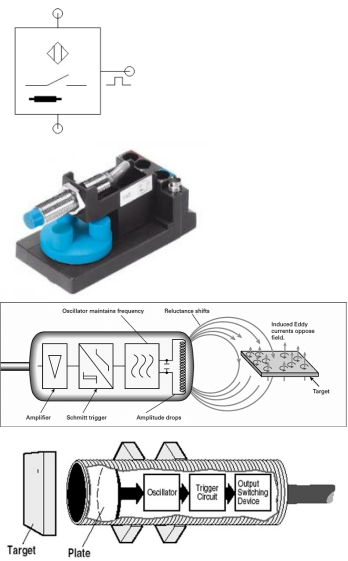

A logic control loop

controller = logic circuit

plant = pneumatic system

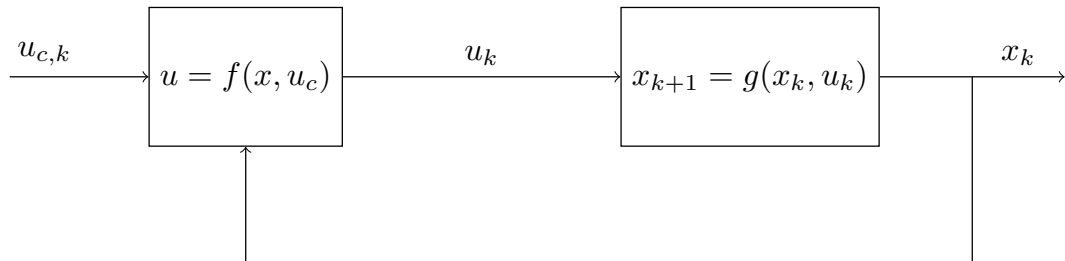

Cheese pressing example - Variables

Activating solenoid UA+ extends the cylinder, activating UA- retracts the cylinder.

State variable

$$x = \begin{cases} 0 & \text{Cylinder retracted} \\ 1 & \text{Cylinder extended} \end{cases}$$


Control signal

$$u = \begin{bmatrix} u_1 \\ u_2 \end{bmatrix},$$

with

$$u_1 = \begin{cases} 0 & \text{Don't activate UA+} \\ 1 & \text{Activate UA+} \end{cases}$$
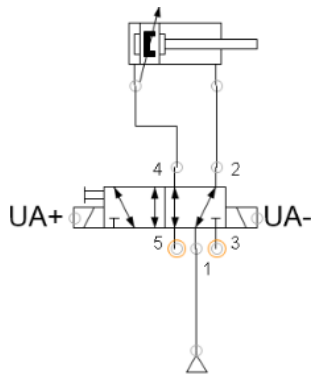
$$u_2 = \begin{cases} 0 & \text{Don't activate UA-} \\ 1 & \text{Activate UA-} \end{cases}$$



Command signal

$$u_c = \begin{cases} 0 & \text{Button unpushed} \\ 1 & \text{Button pushed} \end{cases}.$$

Cheese pressing example - Plant dynamics and control law

Activating solenoid UA+ extends the cylinder, activating UA- retracts the cylinder.

Plant dynamics $x_{k+1} = g(x_k, u_k)$

$u_{1,k}$	$u_{2,k}$	state	
		x_k	x_{k+1}
0	0	0	0
0	1	0	0
1	0	0	1
(1)	(1)	(0)	(0)
0	0	1	1
0	1	1	0
1	0	1	1
(1)	(1)	(1)	(1)

Control law $u_k = f(x, u_c)$

x	u_c	u_1	u_2
0	0	0	1
1	0	0	1
0	1	1	0
1	1	0	1

$u_1 =$


$u_2 =$

Cheese pressing example - implementing the control law


+24V



u_1 0V

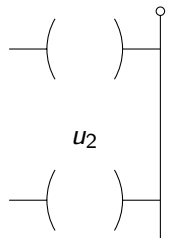


normally open

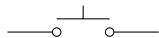


normally open



normally open

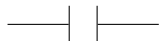

normally closed

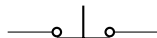


normally closed




normally closed



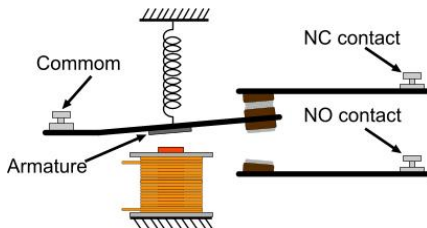
Intermezzo - An electrical circuit with memory



From pcbheaven.com

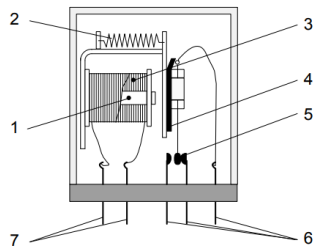

From FESTO didactic

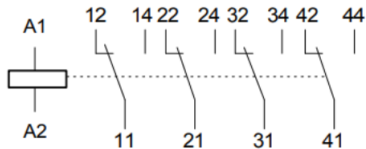


From FESTO didactic



From FESTO didactic

Intermezzo - An electrical circuit with memory


Latching circuit

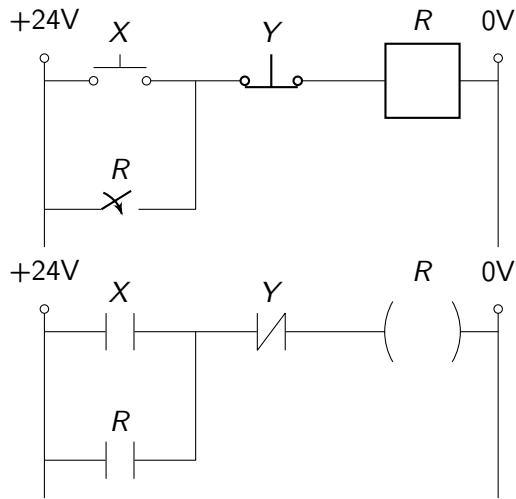


Truth table

X	Y	R_k	R_{k+1}
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	


The lab assignment

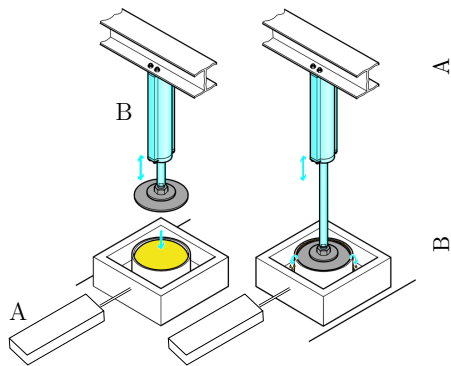


controller = logic circuit

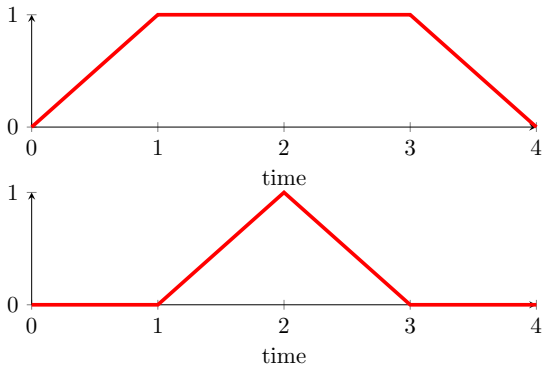


plant = pneumatic system

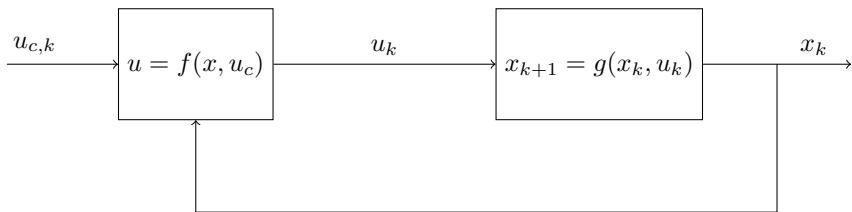

Implementing the sequence $A+B+B-A-$

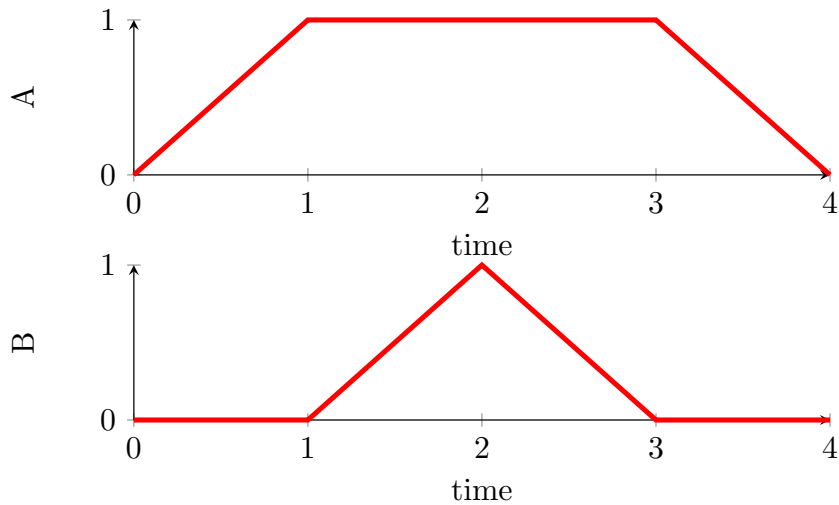

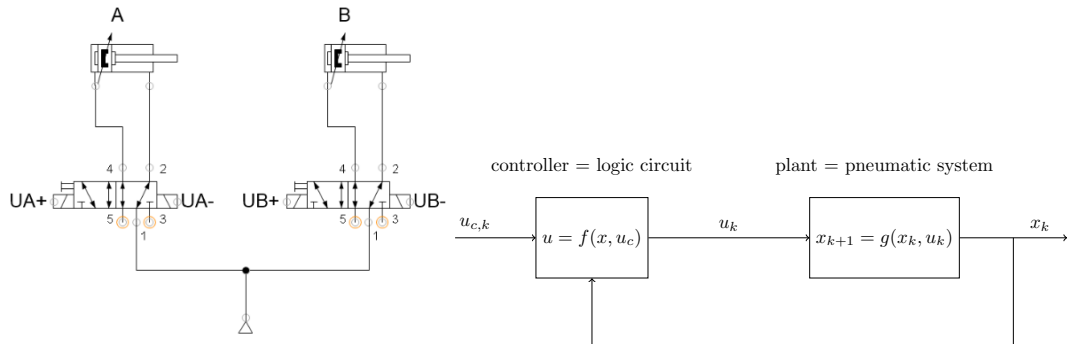Implementing the sequence $A+B+B-A-$, control signal



Control signal


$$u = [u_{A+} \quad u_{A-} \quad u_{B+} \quad u_{B-}]^T,$$

with

$$u_{A+} = \begin{cases} 0 & \text{Solenoid extending A is not activated} \\ 1 & \text{Solenoid extending A is activated} \end{cases}, \quad \text{and similar for B}$$


Implementing the sequence A+B+B-A-, the problem

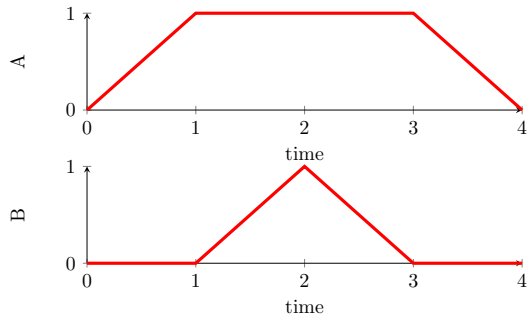The correct control signal (action) is not uniquely defined by the position of the cylinders



controller = logic circuit


plant = pneumatic system

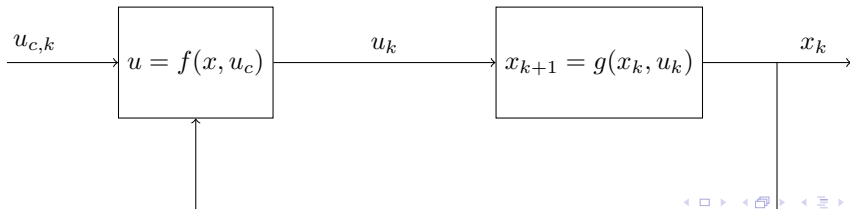

Implementing the sequence $A+B+|B-A-$

Dividing the sequence into groups (a.k.a. cascade method) Each group contains as many steps as possible without repeating a letter.

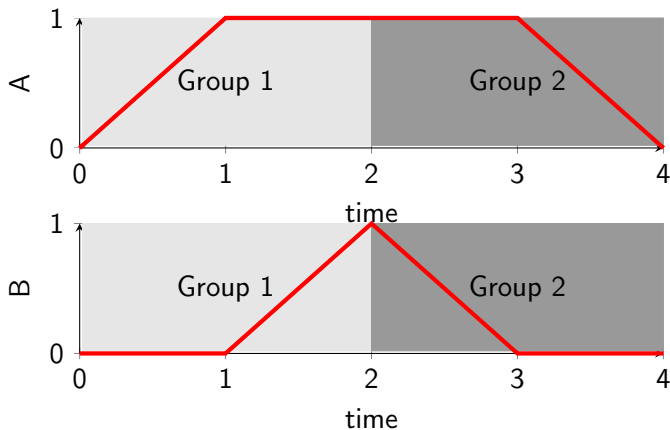
$$\underbrace{A+B+}_{\text{Group 1}} \mid \underbrace{B-A-}_{\text{Group 2}}$$



The cascade method applied to $A+A^-$

The cascade method applied to $A+A-$

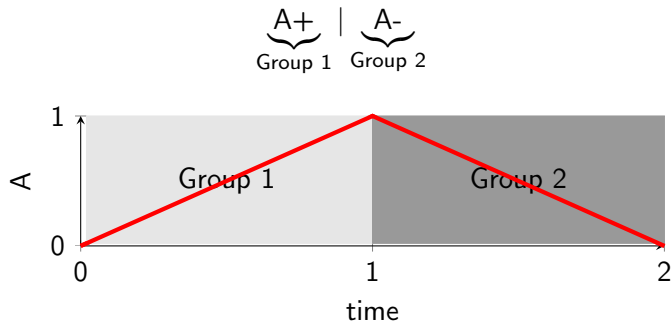
Divide the sequence is to groups, where each group is as long as possible without repeating the same letter.



The cascade method applied to A+A- with delays

Let's add some delays. The process is cyclic and automatic. It takes 4 seconds to replace the mold under the press. The cheese needs to be pressed during 2 seconds before the cylinder retracts.
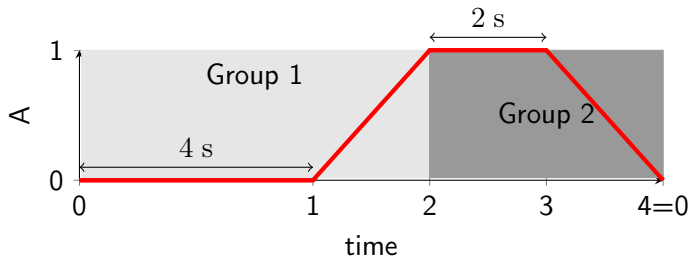
$$\underbrace{T_{4s} A+}_{\text{Group 1}} \mid \underbrace{T_{2s} A-}_{\text{Group 2}}$$



State variables


State variables

$$x = [x_A \quad x_{G1} \quad x_{G2} \quad x_{T4} \quad x_{T2}]^T,$$


where

$$x_A = \begin{cases} 0 & \text{Cylinder A retracted} \\ 1 & \text{Cylinder A extended} \end{cases}$$
$$x_{Gi} = \begin{cases} 0 & \text{Group } i \text{ not active} \\ 1 & \text{Group } i \text{ active} \end{cases}$$
$$x_{Ti} = \begin{cases} 0 & \text{Timer of } i \text{ s not completed} \\ 1 & \text{Timer of } i \text{ s completed} \end{cases}$$


State transitions

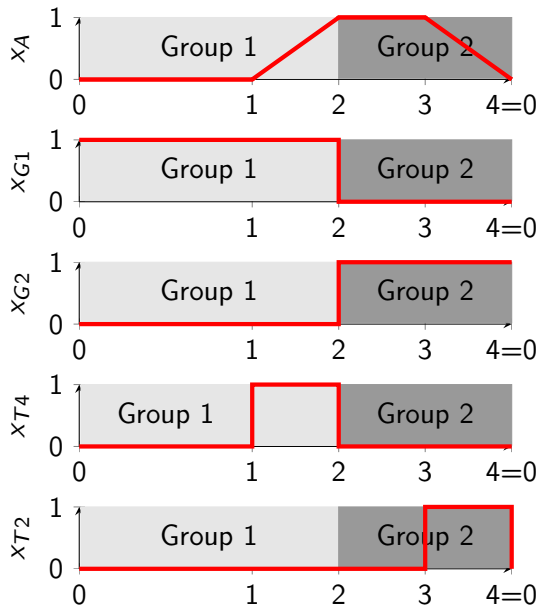


Group transitions

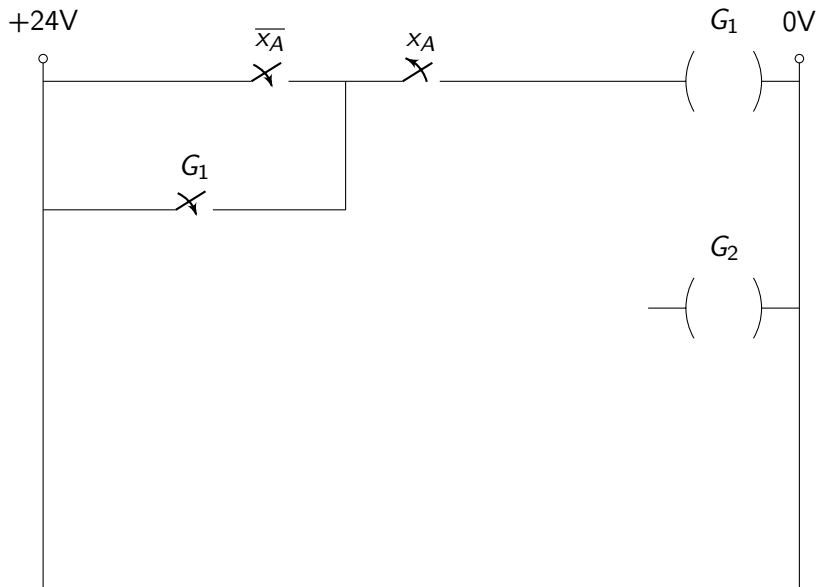

The timers

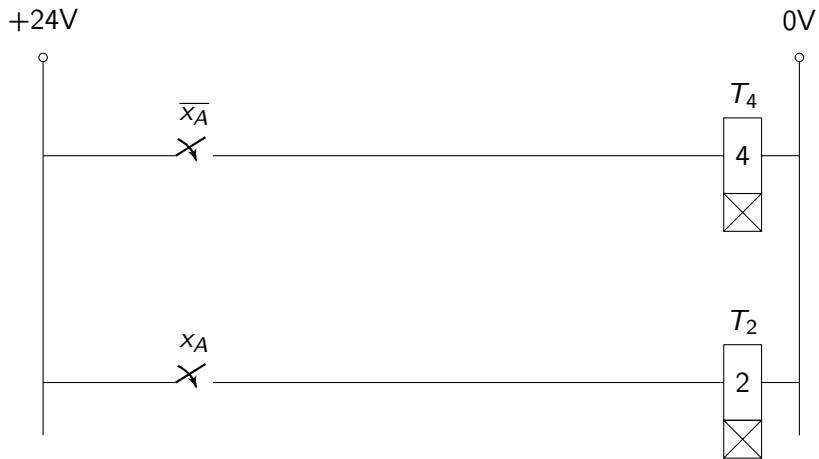

The control law

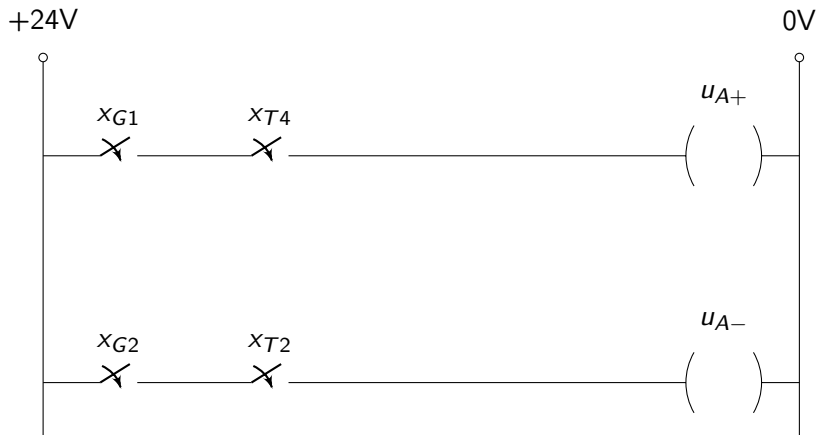

Implementing the sequence $A+B+|B-A-$, state variables

State variables


$$x = [x_A \quad x_B \quad x_{G1} \quad x_{G2}]^T,$$

with

$$x_{\{A,B\}} = \begin{cases} 0 & \text{Cylinder } \{A,B\} \text{ retracted} \\ 1 & \text{Cylinder } \{A,B\} \text{ extended} \end{cases}$$


$$x_{Gi} = \begin{cases} 0 & \text{Group } i \text{ not active} \\ 1 & \text{Group } i \text{ active} \end{cases}$$

State transitions

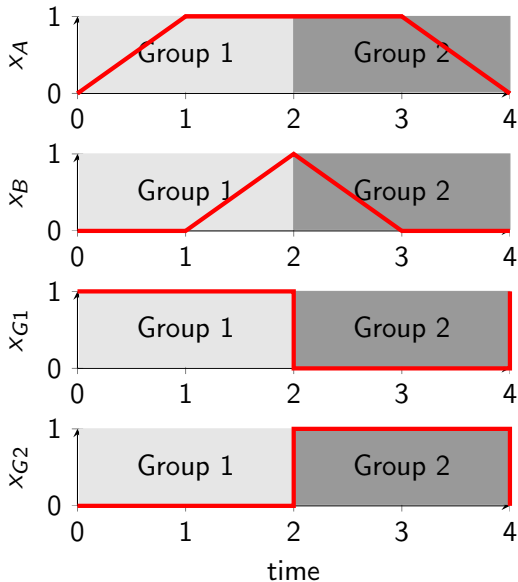

Implementing the sequence $A+B+|B-A-$, control law

State transitions

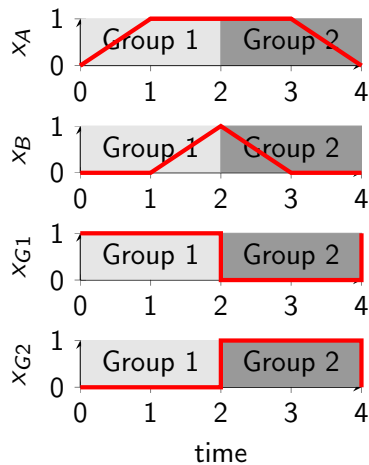

Control law


x_A	x_B	x_{G1}	x_{G2}	u_{A+}	u_{A-}	u_{B+}	u_{B-}
0	0	1	0				
1	0	1	0				
1	1	0	1				
1	0	0	1				

Implementing the control law


+24V



u_{A+} 0V

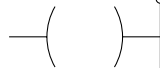


u_{A-}

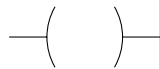



u_{B+}



u_{B-}

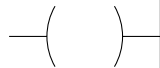

Implementing the group transitions

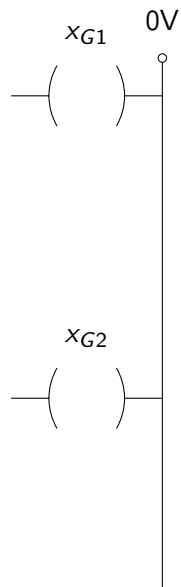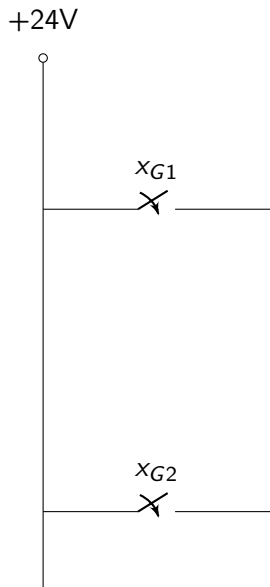

Implementing the proximity sensor circuit

